

Reg. No. _____

Karunya University

(Karunya Institute of Technology and Sciences)

(Declared as Deemed to be University under Sec.3 of the UGC Act, 1956)

End Semester Examination – November/December 2010

Subject Title : DIGITAL ELECTRONICS

Time : 3 hours

Subject Code: EC209

Maximum Marks: 100

Answer ALL questions

PART – A (10 x 1 = 10 MARKS)

1. Write the decimal number -39 as an 8 bit number in sign magnitude form.
2. Express the Boolean expression $Y = AB + B(CD + EF)$ in SOP form.
3. What is the basic function of a comparator?
4. Assign the proper even parity bit for the code 10001010 1.
5. What is an edge triggered flip-flop?
6. What is a register?
7. Define state diagram.
8. Define execution table.
9. What is the bit capacity of a memory that can store 256 bytes of data?
10. What is fan out of a gate?

PART – B (5 x 3 = 15 MARKS)

11. Use the Karnaugh map to minimize the following expression.
$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D} + ABCD$$
12. Draw the logic diagram of a Binary to gray code converters using EX-OR gates.
13. Draw the block diagram and truth table of a 2 bit asynchronous binary counter.
14. Draw the state diagram of a D flip flop.
15. Mention the types of ROM.

PART – C (5 x 15 = 75 MARKS)

16. a. Perform the following operations: (8)
 - i. Convert 100110011010 to octal.
 - ii. Subtract $(84)_{16} - (2A)_{16}$
 - iii. Convert decimal 35 to BCD.
 - iv. Convert binary 10110 to Gray code.
- b. State and prove the DeMorgan's theorems. (7)

(OR)
17. a. Explain with examples the 1's complement and 2's complement method of representing signed numbers. (8)
- b. Use Karnaugh map to simplify the following Boolean expression. (7)
 $Y = \Sigma(1, 2, 4, 6, 7)$
18. a. Implement the Boolean expression $ABC + DE$ using NAND logic gates only. (7)
- b. What is a multiplexer? Describe with logic diagram a 4 x 1 multiplexer. (8)


(OR)
19. a. Explain the function of a full adder. (7)
- b. What is a parallel binary adder? Explain how it can be implemented using full adders. (8)

[P.T.O]

20. a. Describe the basic function of a SR and JK edge triggered flip flops with logic diagrams and truth table. (8)
- b. Implement a asynchronous counter using JK flip flops having a modulus of 12 counting from 0000 to 1011. (7)

(OR)

 21. a. Design a synchronous counter which has the count sequence 001, 010, 101, and 111 using JK flip flops.
22. a. List the main steps involved in synthesis of synchronous sequential circuits. (5)
- b. Synthesize a serial binary adder whose state diagram is as follows. (10)



(OR)

23. A long sequence of pulses enter a 2 input 2 output synchronous sequential circuit which produces an output $Z = 1$ whenever the sequence 1111 occurs (overlapping sequences are accepted). Design the circuit.
24. Describe the basic PAL operation and how SOP expressions can be implemented in it.
- (OR)
25. a. What are the voltage levels of TTL and CMOS logic?
- b. Explain the operation of a TTL and CMOS inverter circuit.