

Reg. No. \_\_\_\_\_

# Karunya University

(Declared as Deemed to be University under Sec.3 of the UGC Act, 1956)  
(Anna University batch)

## End Semester Examination – November / December 2008

Subject Title: **DIGITAL ELECTRONICS**  
Subject Code: **EC209**

Time : **3 hours**  
Maximum Marks: **60**

### Answer ALL questions

#### PART – A (10 x 1 = 10 MARKS)

1. Convert the binary number  $(110100)_2$  into gray code.
2. Explain De-Morgan's theorem.
3. Perform half adder using  $2 \times 4$  multiplexer.
4. \_\_\_\_\_ gate is used for half adder.
5. Name two asynchronous counters.
6. The number of flip-flops required for a Mod-16 ring counter are \_\_\_\_\_.
7. When the circuit is not controlled by the clock, the transition from one state to next occurs whenever there is a change in the input to the circuit at any time and hence this circuit is called as \_\_\_\_\_
8. \_\_\_\_\_ circuits are referred as finite state machine.
9. Fan-in of a logic gate is nothing but the \_\_\_\_\_
10. The fastest logic family is \_\_\_\_\_

#### PART – B (5 x 2 = 10 MARKS)


11. Convert  $(274.2875)_{10}$  to binary.
12. Implement half adder using NAND gates only.
13. Differentiate combinational circuits and sequential circuits.
14. Define state change.
15. Define Propagation delay.

#### PART – C (5 x 8 = 40 MARKS)

16. Simplify the Boolean function  $f(A,B,C,D) = \Sigma(0,2,3,5,6,7,8,9)$  with 10,11,12,13,14,15 as don't cares  
(OR)
17. Simplify and minimize the following four-variable switching function using Quine-McClusky tabulation method.  $f(A,B,C,D) = \Sigma(0,1,2,3,4,6,8,9,10,11)$
18. Design a comparator, which compares the magnitude of two numbers X and Y, each consisting of two bits and giving three outputs  $F_1, F_2, F_3$  such that  
 $F_1 = 1$  if  $X > Y$   
 $F_2 = 1$  if  $X = Y$   
 $F_3 = 1$  if  $X < Y$   
(OR)
19. Realize the function  $\Sigma(0,1,3,5,11,15)$  using multiplexer
20. Explain the working of master slave J-K flip-flop  
(OR)

[P.T.O]

 21. Design a synchronous Mod-5 counter using J-K flip-flop to run through the states 001,010,011,100 and 101 only.
22. Design a sequence detector that produces an output 1 whenever the sequence 101101 is detected  
(OR)
23. Analyse the synchronous sequential circuit shown in figure and draw the state diagram.



24. Implement the following Boolean expression using PLA  

$$Y_1 = ABC' + A'B$$

$$Y_2 = A'B' + AC$$
  
(OR)
25. Explain the operation of TTL Nand gate.