

Reg. No. _____

Karunya University

(Declared as Deemed to be University under Sec.3 of the UGC Act, 1956)

End Semester Examination – November / December 2008

Subject Title: **ELECTRIC CIRCUIT ANALYSIS**

Time : 3 hours

Subject Code: **EE201**

Maximum Marks: 100


Answer ALL questions

PART – A (10 x 1 = 10 MARKS)

1. Write two examples for linear elements.
2. Draw the symbol for a.c voltage source.
3. At resonance the power factor of the circuit is _____.
4. In two watt meter method, if one wattmeter reads zero value and another wattmeter reads some value then the power factor is _____.
5. The regulation value for an ideal Transformer is _____.
6. What is meant by node?
7. Mention any one application of maximum power Transfer Theorem.
8. Minimum number of sources required to apply super position theorem is _____.
9. Time constant value in RL series circuit = ?
10. Draw the Transient response (current) for an RL series circuit.

PART – B (5 x 3 = 15 MARKS)

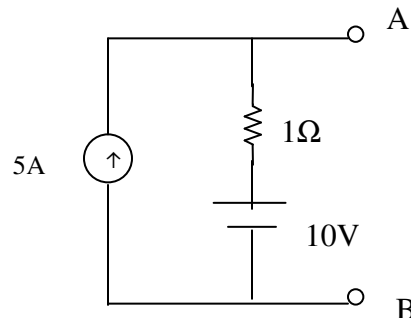
11. Reduce the following to a single source.



12. Define Bandwidth and Q-factor in an RLC series circuit.
13. Define co-efficient of coupling.
14. What is compensation Theorem?
15. Mention any two advantages of Laplace Transformation Technique in circuit Transients.

PART – C (5 x 15 = 75 MARKS)

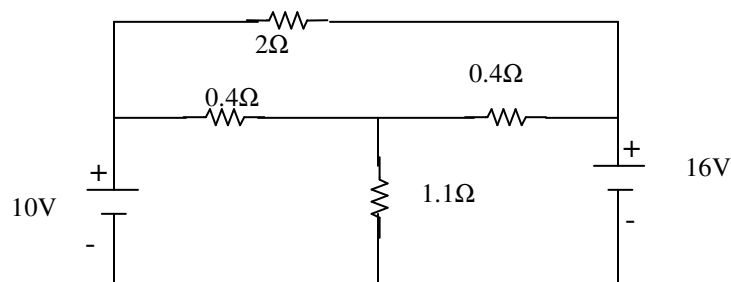16. Find the power delivered by the batteries of figure below.



(OR)


17. a. What is lumped circuit. (2)
- b. Explain the V – I relationships of R,L and C. (8)
- c. Explain current division rule. (5)

18. Derive the relationship among Quality factor, resonant frequency and bandwidth for a series RLC circuit with relevant response.

(OR)


19. Explain the three phase power measurement by two wattmeter method.

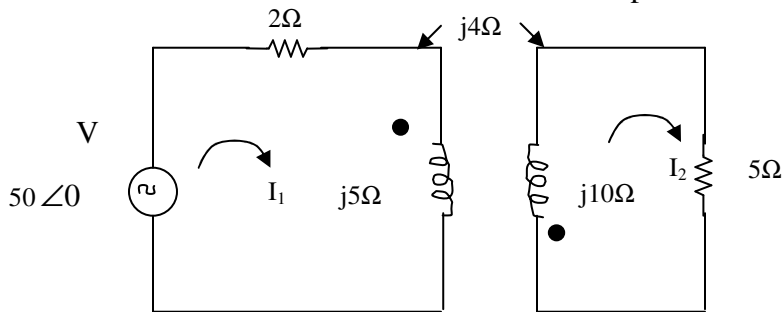20. Calculate the current in the 5 ohm resistor for the coupled circuit shown in fig. below.




(OR)

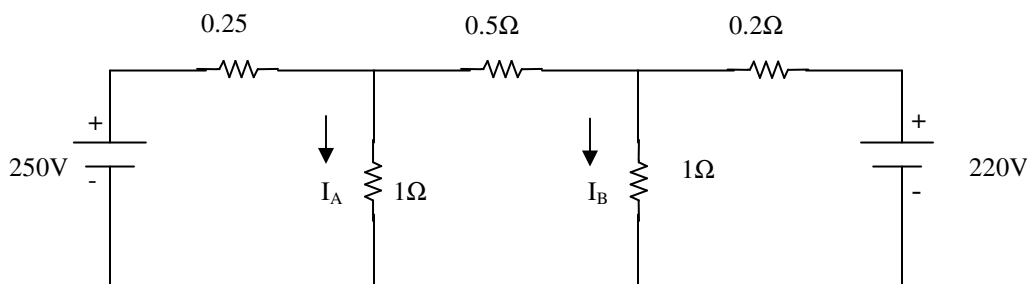21. Find by the nodal method the currents I_A and I_B for the circuit shown in fig. below.




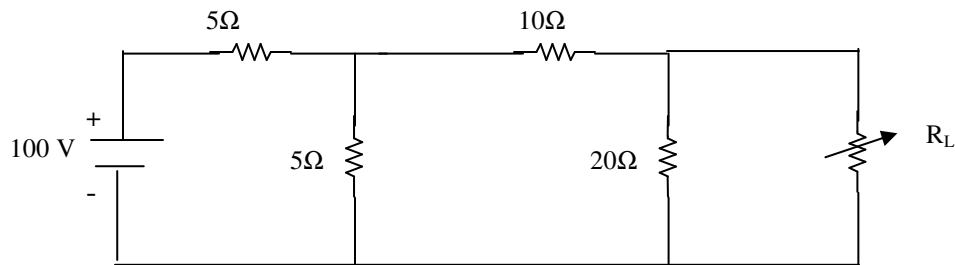22. Find the value of R_L so that maximum power is delivered to the load resistance R_L . Also calculate the Max. power.



(OR)

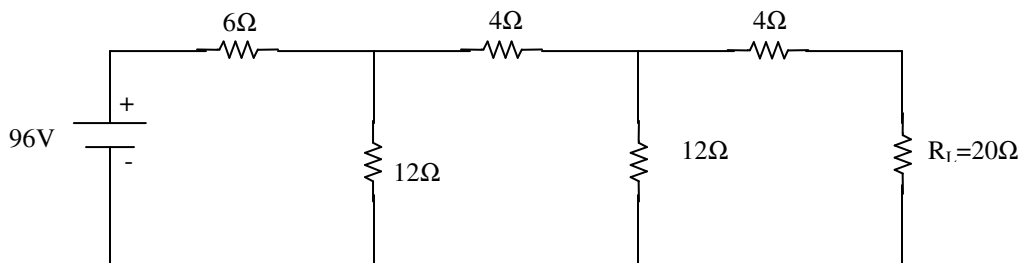23. For the circuit shown in fig. below, find the current in 20Ω load resistor, using Thevenin's theorem.



24. A series R_L circuit with $R = 100\Omega$ and $L = 20$ h has a a.c. voltage of 200 volts applied through a switch at $t = 0$. Find (a) the equation for the transient current and voltage across the elements. (b) the current at $t = 0.5$ secs (c) the time at which $e_R = e_L$.

(OR)

25. The following RC series circuit has an initial charge $Q_0 = 2 \times 10^{-2}$ coloumb as shown. Find the transient current if the switch is closed at $t = 0$.

