



Rajiv Gandhi University of Knowledge Technologies

Weekly Test 3 – Introduction to Electronics

Date: 01-09-2012

Time: 30 Min

Course: E2Sem1_(CSE-ECE)

Max Marks: 10

1. Application of Zener diode is X , Photo diode is Y and LED is Z . Where

- (a) X = Reading of film sound track,
 Y = Reference voltage,
 Z = traffic signal
- (b) X = Reference voltage,
 Y = Reading of film sound track,
 Z = traffic signal
- (c) X = Reading of film sound track,
 Y = traffic signal,
 Z = Reference voltage
- (d) X = traffic signal,
 Y = Reading of film sound track,
 Z = Reference voltage

2. X carriers constitute current in Photodiode with range in Y . Where

- (a) X = Majority, $Y = mA$
- (b) X = Minority, $Y = mA$
- (c) X = Majority, $Y = \mu A$
- (d) X = Minority, $Y = \mu A$

3. $2mA$ current is flowing through source resistance R_s . Find out the value of source resistance R_s . Use concept of linear piecewise diode model.

(Assume $V_{Z_1} = 2V$, $V_{Z_2} = 4V$, Cut-in voltage for $D_1 = 0.2V$, Cut-in voltage for $D_2 = 0.6V$ and forward resistance of D_1 and D_2 is zero ; Refer Figure: 3)

- (a) $6.6k\Omega$
- (b) $8.9k\Omega$
- (c) $7k\Omega$
- (d) None of these

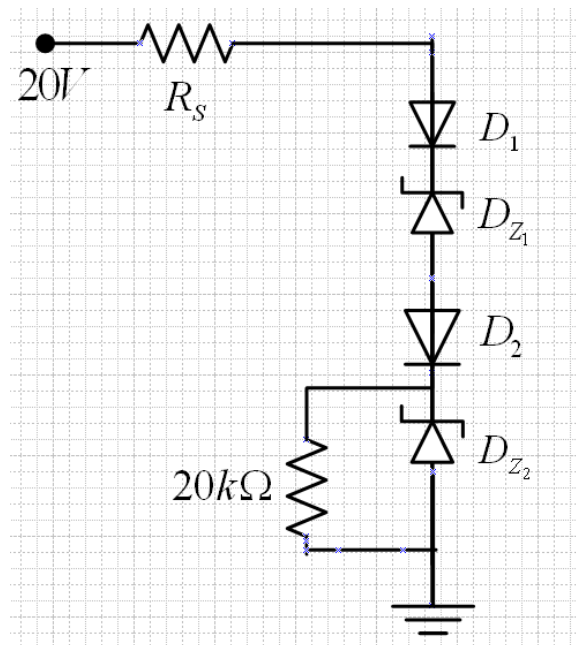


Figure: 3

4. 2mA current is passing through R_1 resistor, find out value of the R_1 . Use concept of linear piecewise diode model.(Use the given assumption in question-3, Refer Figure:4)

- (a) $2.3\text{k}\Omega$
- (b) $1.7\text{k}\Omega$
- (c) $7.7\text{k}\Omega$
- (d) None of these

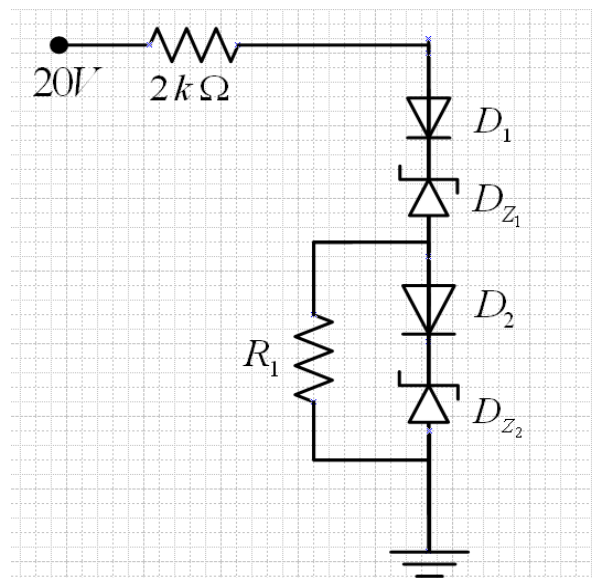


Figure: 4

5. If I is the leakage current, what is the approximate value and direction of the base current. (Assume Emitter and collector region are symmetrical)

- (a) $2I$, flowing from X to Y
- (b) $2I$, flowing from Y to X
- (c) I , flowing from X to Y
- (d) I , flowing from Y to X

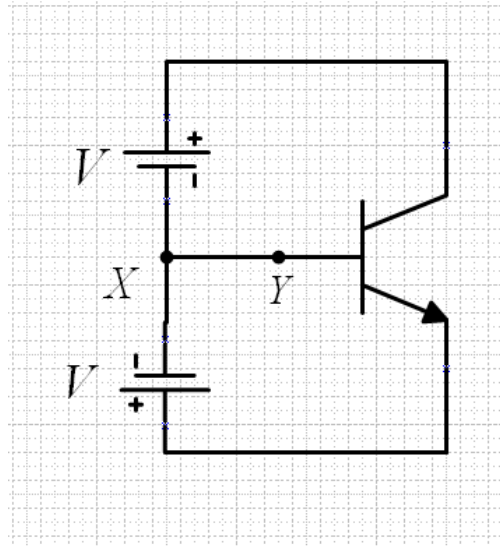


Figure: 5

6. Find out current passes through 4Ω resistor. (Assume voltage drop across base to emitter junction is $0.2V$, assume collector current is nearly equal to emitter current)

- (a) $4.9A$
- (b) $5.1A$
- (c) $2A$
- (d) Data insufficient

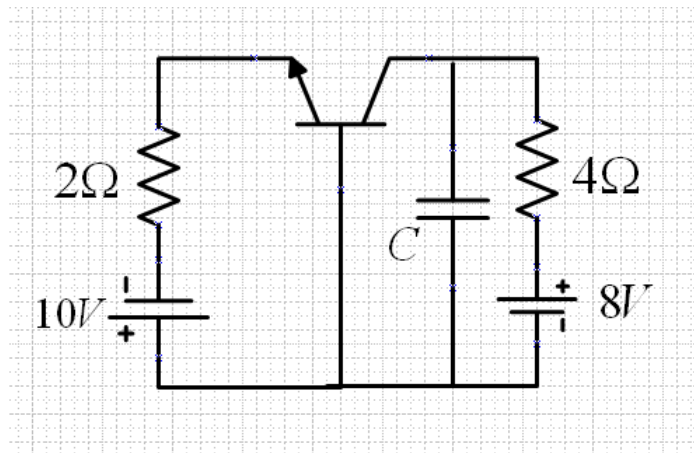


Figure: 6

7. For **npn** bipolar transistor, what is the main stream of current in the base region.

- (a) Drift of holes
- (b) Diffusion of holes
- (c) Drift of electrons
- (d) Diffusion of electrons

8. X is associated with diode and Y is associated with BJT. Where

- (a)** X = Forward resistance, Y = Active region
- (b)** X = Active region, Y = Forward resistance,
- (c)** Both **a** and **b**.
- (d)** Neither **a** nor **b**

9. Consider the following statement for photodiodes:

- 1.** Its dark conductivity is small.
- 2.** With absorption of radiation, equal no. of electrons and holes are produced.

Which of the statement(s) given above is/are correct?

- (a)** **1** only
- (b)** **2** only
- (c)** Both **1** and **2**
- (d)** Neither **1** nor **2**

10. Peak to peak value of the output voltage waveform appeared across the load resistance R_L is depend on which of the following ckt. parameters. Use concept of linear piecewise diode model when zener diodes are in forward bias. (Assume V_m is greater than zener voltages of two zener diodes, and forward resistance of zener diode is zero.; Refer Figure:10)

- (a) Zener voltage of two diodes.
- (b) Cut-in voltage of two diodes.
- (c) Zener voltage of two diodes and load resistance R_L
- (d) Zener voltage of two diodes, source resistance R_s

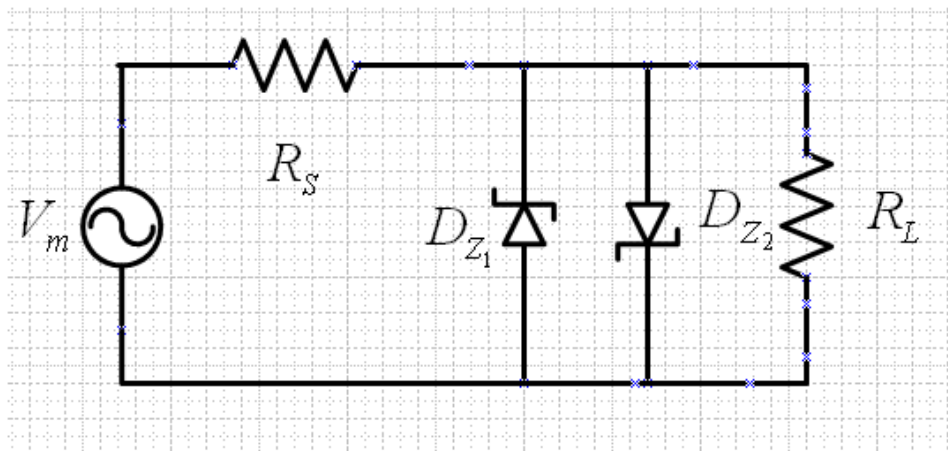


Figure: 10

Introduction to Electronics

Answer Key

1. (b)
2. (d)
3. (a)
4. (a)
5. (b)
6. (a)
7. (d)
8. (a)
9. (c)
10. (b)