



Date: 18-08-2012

Time: 30 Min

Course: E2Sem1\_ECE & CSE

Max Marks: 10

1. Match the following

Column A

- (i) Resistive load
- (ii) Capacitive load
- (iii) Reactive power  $Q > 0$
- (iv) Reactive power  $Q < 0$
- (v) Power factor of a pure inductor

Column B

- (P) positive impedance angle
- (Q) negative impedance angle
- (R) for inductive load
- (S) for capacitive load
- (T) 0
- (U) Unity power factor

(A) (i) – Q, (ii) – P, (iii) – S, (iv) – R, (v) – U

(B) (i) – P, (ii) – Q, (iii) – R, (iv) – S, (v) – T

(C) (i) – U, (ii) – P, (iii) – S, (iv) – R, (v) – T

(D) (i) – U, (ii) – Q, (iii) – R, (iv) – S, (v) – T

2. What is the r.m.s value of 5V symmetric square?


- (A) 5V
- (B) 0 V
- (C) 2.5 V
- (D) 3.75 V

3. What is the resonant frequency of series RL circuit?


- (A)  $f = \frac{1}{2\pi} * L/R$
- (B)  $f = \frac{1}{2\pi} * R/L$
- (C) Can't be determined
- (D)  $R * L$

4. If  $v(t) = V_m \sin(\omega t)$  be the applied voltage to an pure resistive system, which one of the following curve represents the power in an resistor


(A)

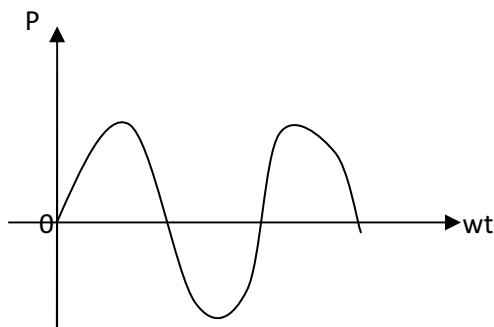


(B)

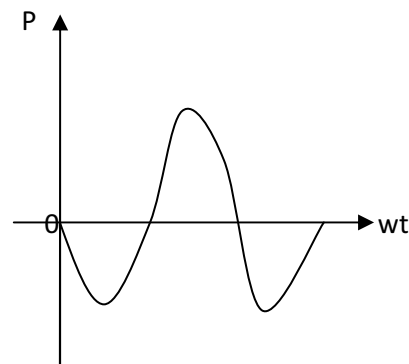

(C)

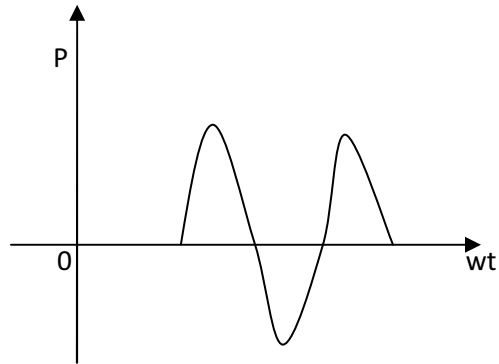


(D)

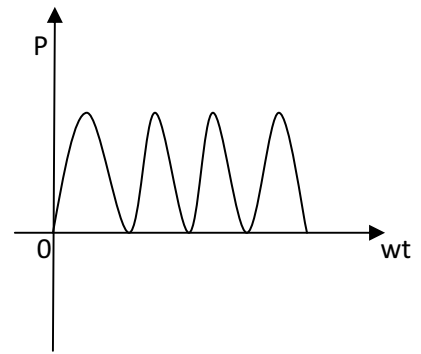

5. What is the power consumed in a  $10\ \Omega$  resistor due to a current source  $i(t) = 2 + 5\cos 2t + 6\cos(2t + 60^\circ)$

- (A) 360 W   (B) 345 W   (C) 455 W   (D) none of the above

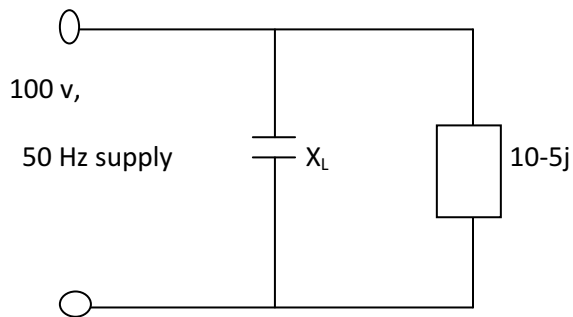6. For the following circuit, calculate the value of inductance that would be required to correct the power factor to unity




(A) 16.91 mH

(B) 15.91 mH

(C) 20.91 mH

(D) None of the above

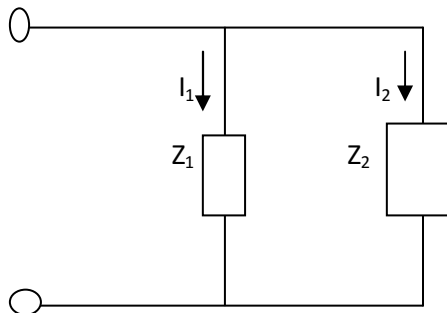7. For the following circuit,  $Z_1$  is an inductor of value ' $L$ ' and  $Z_2$  is a capacitor of value ' $C$ ' then the quality factor is



(A) can't be determined

(B) 1

(C) zero

(D) None of the above

8. In a series R, L, C ckt the power factor at  $f=f_L$  is

- a) 0.707(leading)
- b) 0.707(lagging)
- c) 0.5(lagging)
- d) 1

9. In a parallel R, L, C ckt the power factor at  $f=f_L$  is

- a) 0.707(leading)
- b) 0.707(lagging)
- c) 0.5(lagging)
- d) zero

10. Impedance in a parallel R, L, C at resonance is

- a) maximum
- b) minimum
- c) zero
- d) cant say

Key: 1)B    2)A    3) C    4)D    5) C    6) B    7) D    8)A    9) B    10)A