



## Weekly Test 2 – Introduction to Electronics

**Date:** 25-08-2012


**Time:** 30 Min

**Course:** E2Sem1\_(CSE-ECE)

**Max Marks:** 10

---


1. The ratio of the PIV's of "*centre tap rectifier*" to "*Bridge rectifier*" is.
  - (a) 2
  - (b) 1
  - (c) 0.5
  - (d) None of these
  
2. Find the current through the diode in mA, assume diode is ideal. Refer figure-2.
  - (a) 180
  - (b) 0
  - (c) 200
  - (d) 220

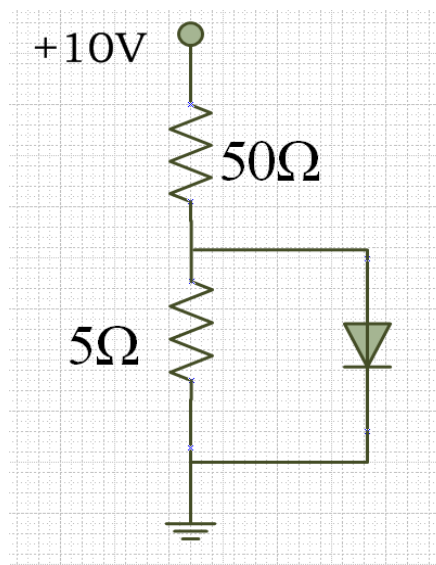

**Figure-2**

**3.** Find the current through the diode under steady state condition. Refer figure-3.

- (a)** 0.6 A
- (b)** 0 A
- (c)** 1 A
- (d)** 2 A

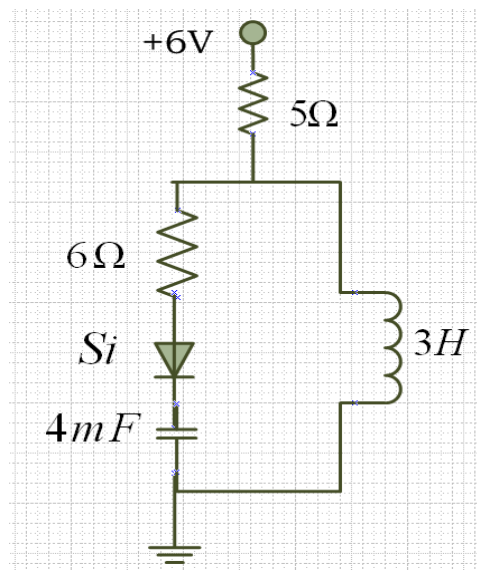

**Figure-3**

4. A HWR supplies 50V DC to a load of  $800\Omega$ , forward resistance of diode is  $25\Omega$ . Find input AC voltage (maximum value) required to achieve the given output.

- (a) 50V
- (b) 100V
- (c) 162V
- (d) 81V

5. Compute the PIV for the diode  $D_1$  in the given circuit. Assume diodes  $D_1$  and  $D_2$  as ideal diodes. Refer figure-5.

- (a) 10V
- (b) -10V
- (c) 0V
- (d) 1V

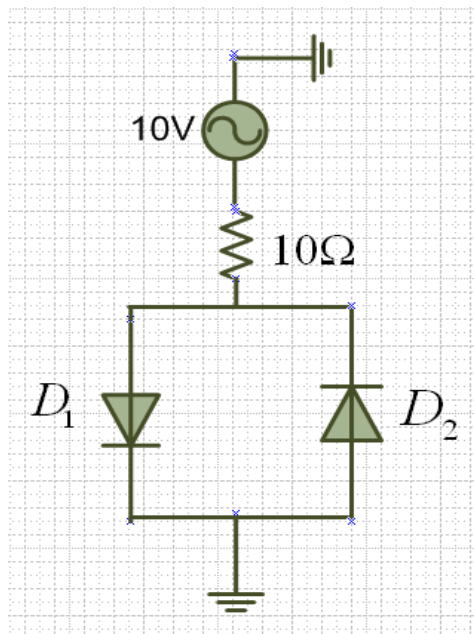


Figure-5

6. Ripple factor can be reduced in case of “*centre tap rectifier*” by which one of the following approach.

- (a) Connecting capacitor in parallel with load resistor
- (b) Connecting inductor in series with load resistor
- (c) Both **a** & **b**
- (d) None of these

7. Zener diode can be mostly used as.

- (a) Voltage regulator
- (b) Photodiode
- (c) Rectifier
- (d) Filter

8. Compute the ratio of RMS value of half wave rectified sinusoidal voltage and Average value of full wave rectified sinusoidal voltage.

- (a)  $\pi/4$
- (b)  $\pi/2\sqrt{2}$
- (c)  $\pi/2$
- (d)  $\pi/\sqrt{2}$

9. Which waveform has highest ripple factor.

- (a) Pure sinusoidal waveform
- (b) Triangular waveform
- (c) Square waveform
- (d) Full wave rectified sinusoidal waveform

10. Find the current through the  $2\Omega$  resistor in amperes. Assume all diodes are practical one and have zero forward resistance.

- (a) 0
- (b) 0.3
- (c) 0.9
- (d) 0.35

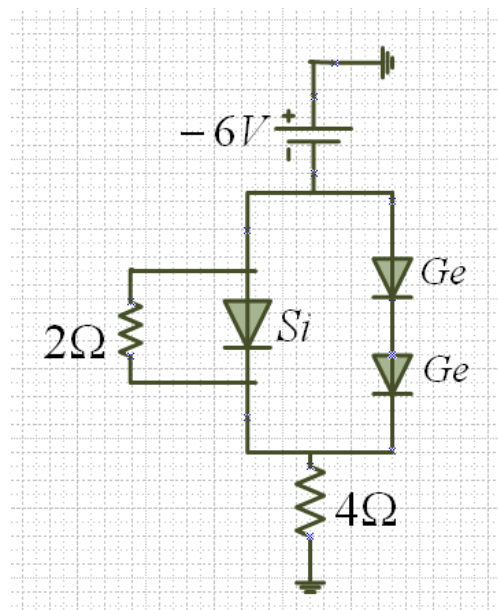


Figure-10

1. (a)
2. (c)
3. (b)
4. (c)
5. (c)
6. (c)
7. (a)
8. (a)
9. (a)
10. (b)