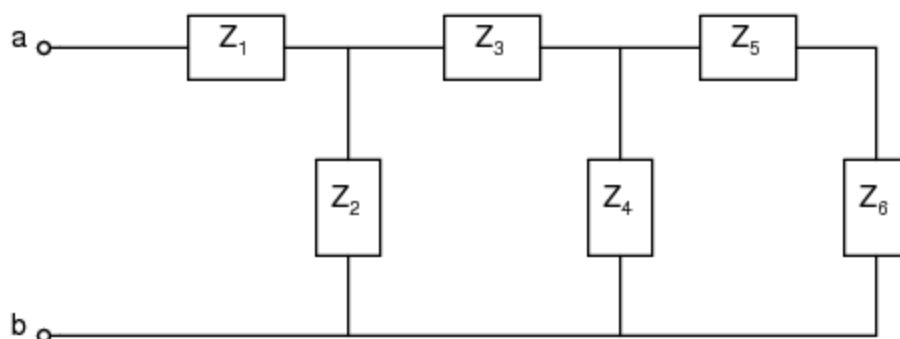




1) Find driving point impedance Z_{ab} for the ckt shown in fig below




a) $Z_1 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_4 + \frac{1}{Z_5 + \frac{1}{Y_6}}}}}$

b) $Z_1 + \frac{1}{Y_2 + \frac{1}{Y_3 + \frac{1}{Y_4 + \frac{1}{Z_5 + \frac{1}{Y_6}}}}}$

c) $Z_1 + \frac{1}{Z_2 + \frac{1}{Z_3 + \frac{1}{Z_4 + \frac{1}{Z_5 + \frac{1}{Z_6}}}}}$

d)None

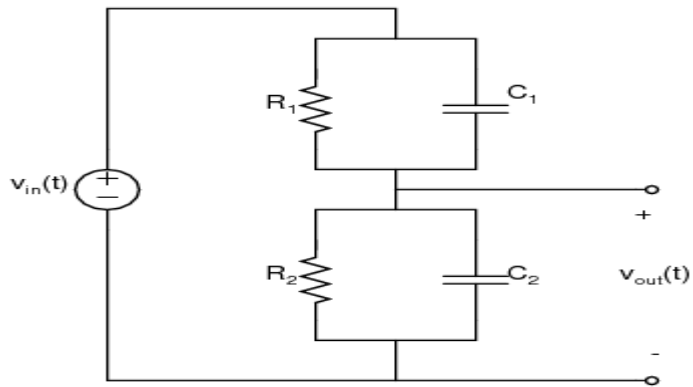2) If $R_1C_1=R_2C_2=\tau$, what is the Transfer function, $H(s)=\frac{V_{out}(s)}{V_{in}(s)}$ for the circuit shown below. Assume all initial conditions are zero.




a) $\frac{R_2\tau s + 1}{R_1(\tau s + 1) + R_2(\tau s + 1)}$

b) $\frac{R_1(\tau s + 1)}{R_1(\tau s + 1) + R_2(\tau s + 1)}$

c) $\frac{R_1}{R_1 + R_2}$

d) $\frac{R_2}{R_1 + R_2}$

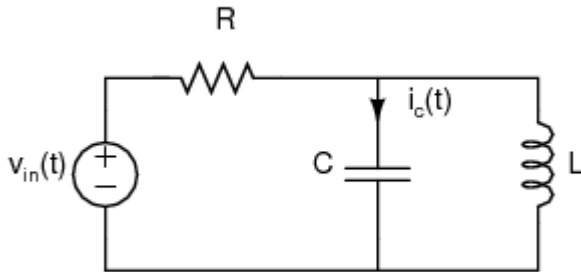3) If $L=1\text{H}$, $C=0.5\text{F}$, $R=\frac{2}{3}\Omega$ and $v_{in}(t)=e^{-t}u(t)$ V then what is $i_c(t)$ for the ckt shown in fig below. Assume all initial conditions are zero



a) $i_c(t) = (6e^{-2t} + 4.5te^{-t} + 1.5e^{-t})u(t)A$

b) $i_c(t) = (6e^{-2t} - 4.5te^{-t} + 1.5te^{-t})u(t)A$

c) $i_c(t) = (6e^{-2t} - 4.5te^{-t} + 1.5e^{-t})u(t)A$

d) $i_c(t) = (6e^{-2t} - 4.5e^{-t} - 1.5te^{-t})u(t)A$


4) If $L=0.25\text{ H}$, $C=0.4\text{ mF}$, $R=10\Omega$ then what is $v_c(t)$, for the circuit shown below. Given $v_c(0^-)=20\text{ V}$ and $i_L(0^-)=4\text{ mA}$

a) $(26.6\cos 200t - 6.6\sin 50t)u(t)\text{ V}$


b) $(-6.6e^{-200t} + 26.6e^{-50t})u(t)\text{ V}$

c) $(26.6e^{-200t} + 6.6e^{-50t})u(t)\text{ V}$

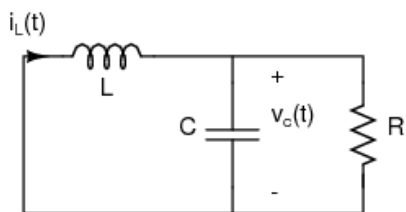d) $(26.6e^{-200t} - 6.6e^{-50t})u(t)\text{ V}$



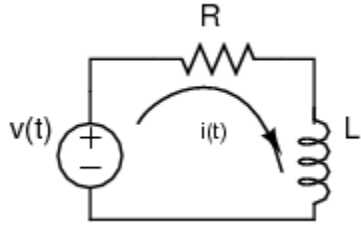5) If $v(t)=e^{-t}$ is a Voltage source connected to a series RL ckt as shown in fig below. Given $R=2\ \Omega$, $L=1\ \text{H}$. Find the current $i(t)$. Given the initial current in the inductor is zero.




a) $i(t) = (-e^{-t} - e^{-2t})u(t)$

b) $i(t) = (-e^{-t} + e^{-2t})u(t)$

c) $i(t) = (e^{-t} - e^{-2t})u(t)$

d) None

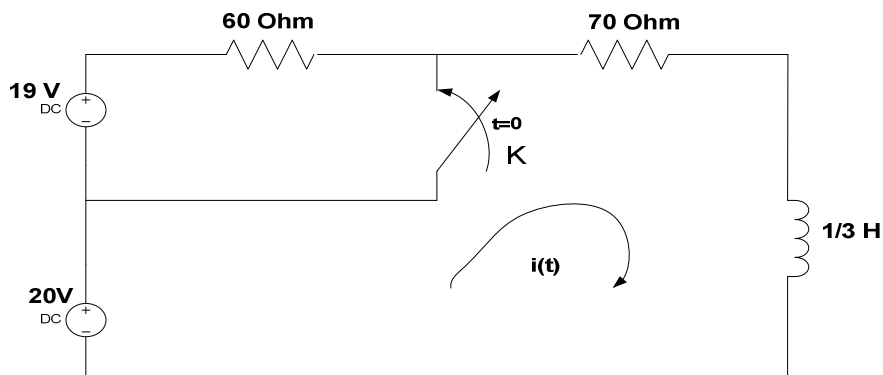6) For the circuit shown below, the switch is kept open until steady state is reached by the network. At $t=0$, switch 'K' is closed. Find $i(t)$.




a) $i(t) = (0.29 + 0.014e^{-210t})u(t)$

b) $i(t) = (0.55 - 0.26e^{-210t})u(t)$

c) $i(t) = (0.55 - 0.28e^{-210t})u(t)$

d) $i(t) = (0.29 - 0.014e^{-210t})u(t)$

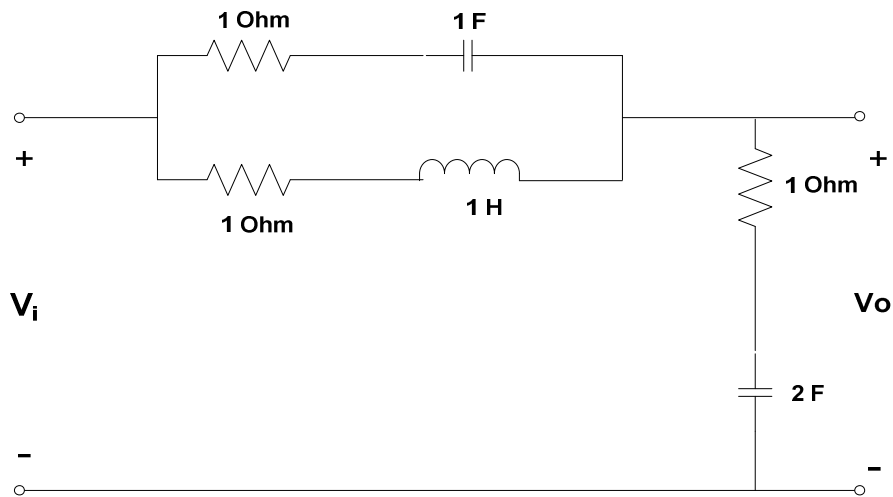7) Find the transfer function $H(s) = V_o(s) / V_i(s)$




a) $\frac{2s+1}{4s+1}$

b) $\frac{4s^2 + 5s + 1}{(2s+1)(s+1)}$

c) $\frac{s+2}{2(s+1)}$

d) $\frac{2s+1}{4(s+1)}$

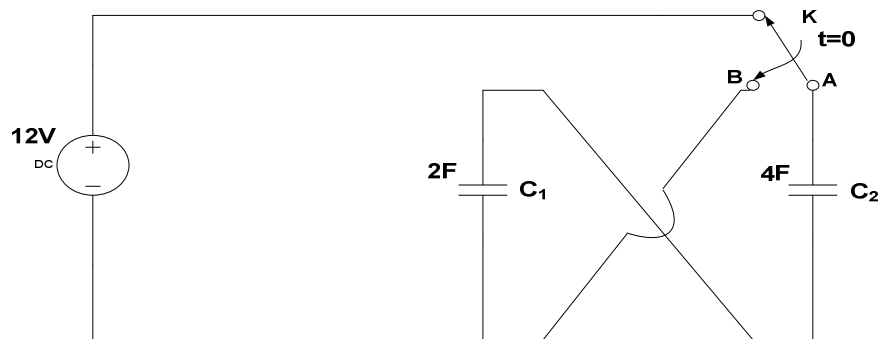8) For the circuit shown below switch moves from position A to position B at $t=0$, using S- domain analysis find $V_{2F}(t)$, $V_{4F}(t)$




- a) 2 V, 2V
- b) $16/3$ V, $16/3$ V
- c) 0 V, 0 V
- d) $-16/3$ V, $16/3$ V


9) Match the following for the graph given below

A. Twigs	(i) 4,5,6,7
B. Links	(ii) 1,2,3,8
	(iii) 1,2,3,4,5
	(iv) 6,7,8

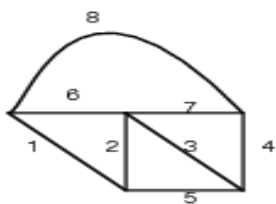- a) A---(i), B----(ii)
- b) A---(iii), B----(iv)
- c) A---(i), B----(iii)
- d) None of the above



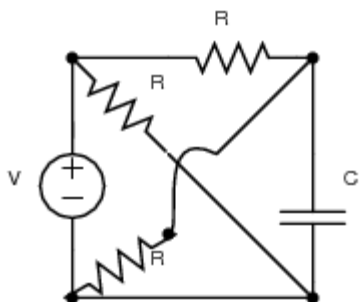10) Determine the number of nodes and branches for the electrical network as shown below



- a) 4 nodes, 6 branches
- b) 3 nodes, 5 branches
- c) 3 nodes, 6 branches
- d) 4 nodes, 5 branches

KEY

- 1)a
- 2)d
- 3)b
- 4)d
- 5)c
- 6)a
- 7)a

8)c

9)a

10)b