

**GATE - 2009**

**Answer Keys**

<b>1</b>	D	<b>2</b>	A	<b>3</b>		<b>4</b>	A	<b>5</b>	A	<b>6</b>	A	<b>7</b>	B
<b>8</b>	D	<b>9</b>	D	<b>10</b>	D	<b>11</b>	D	<b>12</b>	C	<b>13</b>	D	<b>14</b>	C
<b>15</b>	C	<b>16</b>	B	<b>17</b>	B	<b>18</b>	A	<b>19</b>	C	<b>20</b>	A	<b>21</b>	C
<b>22</b>		<b>23</b>	C	<b>24</b>	B	<b>25</b>		<b>26</b>		<b>27</b>	C	<b>28</b>	D
<b>29</b>		<b>30</b>		<b>31</b>	D	<b>32</b>		<b>33</b>	B	<b>34</b>	A	<b>35</b>	B
<b>36</b>	A	<b>37</b>	B	<b>38</b>	A	<b>39</b>	D	<b>40</b>	C	<b>41</b>	C	<b>42</b>	B
<b>43</b>	B	<b>44</b>	A	<b>45</b>		<b>46</b>	C	<b>47</b>		<b>48</b>		<b>49</b>	
<b>50</b>		<b>51</b>	D	<b>52</b>	B	<b>53</b>	A	<b>54</b>	C	<b>55</b>	A	<b>56</b>	
<b>57</b>	D	<b>58</b>	D	<b>59</b>	C	<b>60</b>	A						

1. (D)


$$|e^{j(x+jy)}| = |e^{-y+jx}| = e^{-y} |e^{jx}| = e^{-y} [|\cos x + j \sin x|] = e^{-y}$$

4. (A)

$$\frac{x}{\sqrt{x^2 + y^2 + z^2}}, \frac{y}{\sqrt{x^2 + y^2 + z^2}}, \frac{z}{\sqrt{x^2 + y^2 + z^2}} \Rightarrow (x, y, z)$$

Given  $r=1, \therefore$

6. (A)

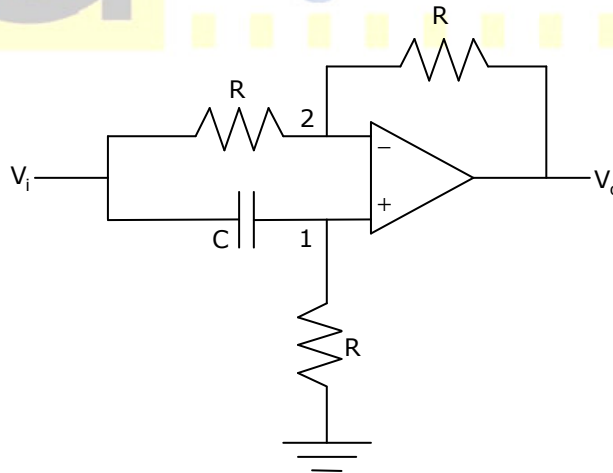

$$V_+ = \left[ \frac{sCR}{1 + sCR} \right] V_i$$

$$V_- = V_+$$

$$\frac{V_i - \frac{sCR V_i}{1 + sCR}}{R} = \frac{sCR}{1 + sCR} \frac{V_i - V_o}{R} \Rightarrow \frac{V_o}{V_i} = \frac{sCR - 1}{sCR + 1}$$

gain = 1, Hence it is APF

7. (B)

It is an AND gate

8. (D)

	PQ		R'P'Q		
RS	00	01	11	10	
00	0	1	0	0	
01	0	1	1	1	
11	1	1	1	0	R'SP
10	0	0	1	0	
					RPQ

9. (C)

JK	Q(t + 1)
00	Q(t)
01	0
10	1
11	Q(t)

10. (C)

$$(1.375)_{10} = (1.011)_2$$

$$0.375 \times 2 = 0.75$$

$$0.75 \times 2 = 1.5$$

$$0.5 \times 2 = 1$$

12. (C)

For  $2\sin(2\pi t)$ ,  $T_1 = \frac{2\pi}{2\pi} = 1\text{s}$

$3\sin(3\pi t)$ ,  $T_2 = \frac{2\pi}{3\pi} = \frac{2}{3}\text{s}$

$\text{LCM}\left(1, \frac{2}{3}\right) = 2\text{ sec}$

13. (D)


$x(t) = \sin t$

$\omega = 1$


$\frac{1}{\sqrt{1+\omega^2}} \angle -\tan^{-1} \omega = \frac{1}{\sqrt{2}} \angle (-\pi/4)$

$\therefore \text{output} = \frac{1}{\sqrt{2}} \sin(t - (\pi/4))$

14. (C)

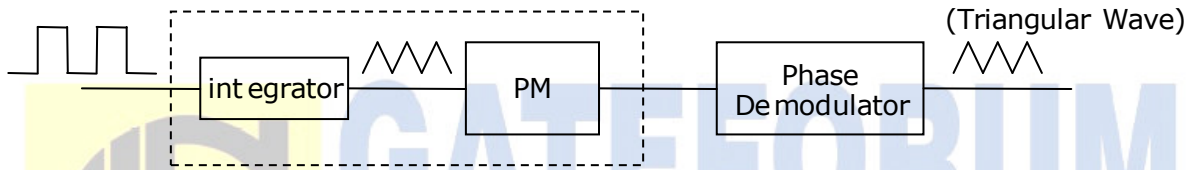

16. (B)

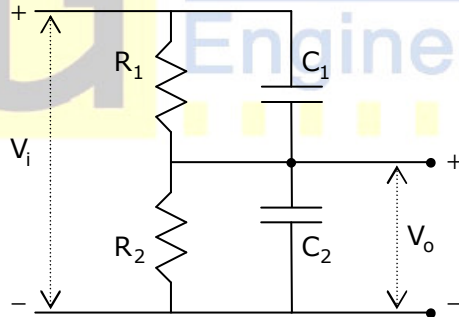

$K = \frac{V_i}{V_o}; C_2 = C_1 [K - 1]; R_2 = \frac{R_1}{K - 1}$

$K = 10$

$R_2 = 1\text{M}\Omega$

$C_2 = 45\text{pF}; C_1 = \frac{45\text{pF}}{9} = 5\text{pF}$

17. (B)

$$I_{fs} = 1\text{mA}; R_m = 100\Omega$$

$$V = 10\text{V}$$

$$V = I_m (R_m + R_s)$$

$$R_s = \frac{V}{I_{fs}} - R_m = \frac{10}{1\text{mA}} - 100 = 10,000 - 100 = 9.9\text{k}\Omega$$

21. (C)

$$\begin{bmatrix} -3 & 0 \\ 0 & -1 \end{bmatrix}$$

Hence eigen values are -3,-1

24. (B)

$$x^3 = j = e^{j\pi/2}$$

$$x = e^{j\pi/6} = \cos 30 + j \sin 30 = \frac{\sqrt{3}}{2} + j \frac{1}{2}$$

28. (D)

$R_L = 2\Omega$ , max power transfer thereon

$$P_{\max} = 6.125\text{W}$$

31. (D)

For thermistor,

$$R_{T_1} = R_{T_2} e^{B \left( \frac{1}{T_1} - \frac{1}{T_2} \right)}$$

For P:  $\beta=3000\text{k}$ , At  $T_2 = 298\text{K}$ ,  $R_{T_2} = 2\text{k}\Omega$

For Q,  $\beta=3000\text{k}$ , AT  $T_2 = 298\text{k}$ ,  $R_{T_2} = 2\text{k}\Omega$

At  $T_1 = 373\text{k}$ ,

$$R_{T_1P} = (2\text{k}) e^{4000 \left[ \frac{1}{373} - \frac{1}{298} \right]} \dots\dots\dots (1)$$

$$R_{T_1Q} = (2\text{k}) e^{3000 \left[ \frac{1}{373} - \frac{1}{298} \right]} \dots\dots\dots (2)$$

$$\frac{\text{Eqn. 1}}{\text{Eqn. 2}} = 0.509$$

33. (B)

By KCL at  $V_i$ ,

$$\frac{V_i}{1\text{k}} = \frac{0 - V_o}{10\text{k}} + \frac{0 - [3.2 - V_o]}{10\text{k}} \Rightarrow V_o = -6.6\text{V}$$

34. (A)

$$\text{Input resistance} = \frac{V_i}{I}$$


$$I = \frac{V_i - 0}{R} + \frac{V_i - V_o}{2R} \quad \text{KCL at node 1.}$$

$$\frac{V_i - 0}{R} = \frac{0 - V_o}{3R} = \frac{-V_o}{3R} \quad \text{KCL at node 2.}$$

$$V_o = -3V_i$$

$$I = \frac{V_i}{R} + \frac{V_i + 3V_i}{2R} = \frac{2V_i}{R} + \frac{V_i}{R} = \frac{3V_i}{R}$$

$$\frac{V_i}{I} = R/3$$

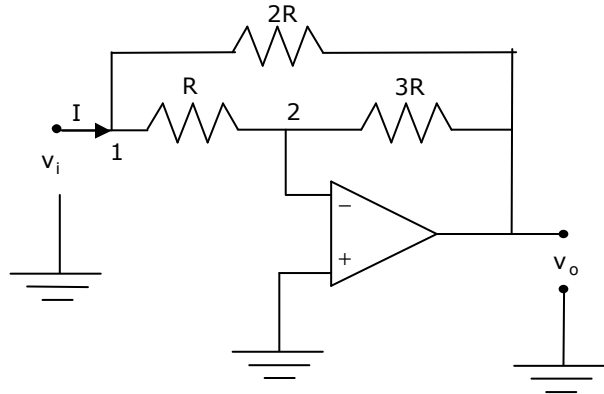

35. (B)

It is a limited circuit

It makes a transition from +5V to -5V.

$$\exists 0(1 - e^{-t/RC}) = 5 \times \frac{4.7}{9.4} = \text{Voltage across bottom } 4.7\text{k}\Omega$$

$$= V_+$$

$$R = 10\text{k}\Omega; C = 1\mu\text{F}; t = 8.7\text{m sec}$$

38. (A)

$$XRAA \rightarrow A = 00H$$

40. (C)


$$3 + 2 \sin t \cos 2t = 3 + [\sin(t+2t) + \sin(t-2t)]$$

$$= 3 + \sin 3t - \sin t$$

It is of  $a + b \sin \theta + c \sin 3\theta$

$$\text{RMS value} = \sqrt{a^2 + \left(\frac{b}{\sqrt{2}}\right)^2 + \left(\frac{c}{\sqrt{2}}\right)^2} = \sqrt{9 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{10}$$

44. (A)

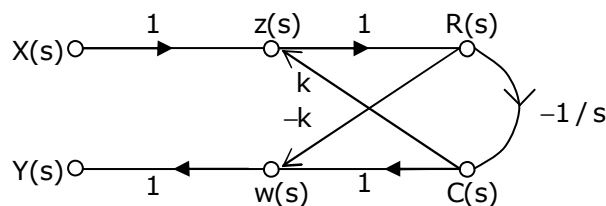

$$Z(s) = kC(s) + X(s)$$

$$W(s) = C(s) - kR(s)$$

$$y(s) = W(s)$$

$$C(s) = \frac{-1}{s} R(s)$$

$$R(s) = Z(s)$$

$$\begin{aligned} \therefore y(s) &= c(s) - kz(s) \\ &= \frac{-1}{s} C(s) - kZ(s) \\ &= -\left[\frac{1+ks}{s}\right] Z(s) = X(s) \end{aligned}$$

$$Z(s) = k\left(-\frac{1}{s}\right)Z(s) + X(s)$$

$$\left(1 + \frac{k}{s}\right)Z(s) = X(s)$$

$$\therefore \frac{Y(s)}{X(s)} = \frac{-(1+ks)}{k+s}$$

46. (B)

Characteristic equation is

$$|sI - F| = 0$$

$$\begin{aligned} \left| \begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} - \begin{pmatrix} 0 & 1 \\ -4 & -2 \end{pmatrix} \right| &= \begin{vmatrix} s & -1 \\ 4 & s+2 \end{vmatrix} = s(s+2) + 4 = 0 \\ &= s^2 + 2s + 4 = 0; \quad \boxed{\xi=0.5} \end{aligned}$$