



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2009
DIGITAL ELECTRONIC CIRCUITS
SEMESTER - 4

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10
- i) Gray code of 1011 (binary) =
- | | | |
|---------|-------------------|--------------------------|
| a) 0101 | b) 1101 | |
| c) 1110 | d) none of these. | <input type="checkbox"/> |
- ii) An example of reflected code is
- | | | |
|---------|------------------|--------------------------|
| a) BCD | b) ASCII | |
| c) GRAY | d) Hamming code. | <input type="checkbox"/> |
- iii) If $(212)_x = (23)_{10}$ where x is base (+ ve integer) then the value of x is
- | | | |
|------|-------|--------------------------|
| a) 2 | b) 3 | |
| c) 4 | d) 5. | <input type="checkbox"/> |
- iv) Excess-3 code 3d representation of $(19)_{10}$ is
- | | | |
|-------------|--------------|--------------------------|
| a) 10011 | b) 00011001 | |
| c) 01001100 | d) 11000100. | <input type="checkbox"/> |
- v) The decimal equivalent of the binary number $(101111.1101)_2$ is
- | | | |
|-----------------------|-----------------------|--------------------------|
| a) $(46.8125)_{10}$ | b) $(47.8125)_{10}$ | |
| c) $(47.8155)_{10}$ | d) $(47.8145)_{10}$ | <input type="checkbox"/> |



GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following questions.

3 × 15 = 45

7. a) Draw and explain the circuit of BCD adder using commercially available adder IC 748-3 and other necessary logic gates. 7

b) Simplify the following using Quine McClusky method :

$$F(W, X, Y, Z) = \sum (0, 1, 2, 5, 8, 14) + \sum d(4, 10, 13). \quad 8$$

8. a) What is CLA adder ? Define the terms 'carry propagate' and 'carry generate'. The propagation delay of EX-OR gate is 20ns and that of OR and AND gate is 10ns. Find the propagation delay of a CLA adder. 2 + 3 + 2

b) "Excess-3 code is self-complementing." Explain the statement and write its application. 4

c) Implement the following function using a 3 × 4 × 2 PLA :

$$F_1(A, B, C) = \sum (3, 5, 6, 7)$$

$$F_2(A, B, C) = \sum (0, 2, 4, 7). \quad 4$$

9. a) With the help of necessary circuit diagram, explain the operation of dual slope ADC. 9

b) A 4-bit binary ladder D/A converter with $R = 10 \text{ k}\Omega$ uses a reference of 5 V. Find the following :

i) Ideal scale factor in V/step

ii) Analog output corresponding to the binary input 0110


iii) Resolution in %

iv) Full scale output

v) Maximum deviation in volts from the best straight line in order to meet standard linearity. 6



 10. a) Design a sequential circuit that implement the following state diagram. Use all D-type F/F for the design. 9



- b) Draw and explain the 4 bit bi-directional Shift Register using mode control (M), when M is logic zero then left shift an right shift for M is logic one. 6
11. Write short notes on any *three* of the following : 3 × 5

- D.C. noise margin and A.C. noise margin
- Hold time and set-up time related to FF
- Parity generator and checker
- Tri-state gates in TTL family
- EPR0M.

END