

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-III Examination December 2009****Subject code: 130901****Subject Name: Circuits and Networks****Date: 19 / 12 / 2009****Time: 11.00 am – 1.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State and explain (i) Thevenin's theorem and (ii) Norton's theorem in brief giving suitable examples. **06**
- (b) What are Y-parameters and Z-parameters? Derive the expression for Z parameters in terms of Y parameters and vice versa. **06**
- (c) How inductor and capacitor will behave at $t = 0$ and at $t = \infty$. Draw equivalent networks. **02**

- Q.2** (a) What is duality? Prepare a list of dual quantities encountered in electrical engineering. Describe the procedure to draw dual of a network. **07**
- (b) Determine the current through 4Ω resistor branch of the network given in **Fig 1**. using mesh analysis **07**

OR

- (b) In the network of **Fig.2** using node analysis find V_2 which results in zero current through 4Ω resistor. **07**

- Q.3** (a) A network with magnetic coupling is shown in **Fig.3**. For the network $M_{12}=0$ Formulate loop equations for this network using KVL. **04**
- (b) Determine the equivalent inductance at terminals A-B for circuit in **Fig.4** **02**
- (c) Explain the rules for source transformation technique. For the network shown in **Fig.5** determine the numerical value of current i_2 using source transformation technique. **08**

OR

- Q.3** (a) State and explain the maximum power transfer theorem. Derive the condition for maximum power transfer to the load for d.c. circuits. **06**
- (b) For the network shown in **Fig.6** determine the value of R_L for maximum power transfer. What will be the value of power transfer under this condition? **08**

- Q.4** (a) For the network shown in **Fig.7** switch K is closed at time $t = 0$ with zero inductor current and zero capacitor voltage. Solve for **10**
- (i) V_1 and V_2 at $t = 0^+$
- (ii) V_1 and V_2 at $t = \infty$
- (iii) dV_1/dt and dV_2/dt at $t = 0^+$
- (iv) d^2V_2/dt^2 at $t = 0^+$
- (b) In the network of **Fig. 8** steady state is reached with switch K open. At $t = 0$ switch K is closed. Find $i(t)$ for the numerical values given. **04**

OR

- Q.4** (a) State the procedure to obtain solution of a network using Laplace transform technique. State its advantages over classical method. **06**
- (b) For the circuit shown in **Fig. 9** obtain the transform of the generator current $I(s)$. **03**

- (c) A series R-L-C circuit having initially zero inductor current and zero capacitor voltage is excited by a 20V d.c. source. Find $i(t)$. Assume $R = 9\Omega$, $L = 1H$ and $C = 0.05F$. 05

- Q.5 (a) What is meant by poles and zeros of network function? State its important features and explain its physical significance. 07
- (b) Obtain ABCD parameters for the network shown in Fig. 10 07

OR

- Q.5 (a) Give the definition of the following: 04
- (i) Graph (ii) Branch (iii) Node (iv) Tree

- (b) Draw the graph for the circuit shown in Fig.11. Prepare the incidence matrix A and partition it into a matrix containing all passive branches A_p and a matrix containing independent current sources branches A_g . Formulate the branch admittance matrix Y_p and hence find node admittance matrix Y_n 10

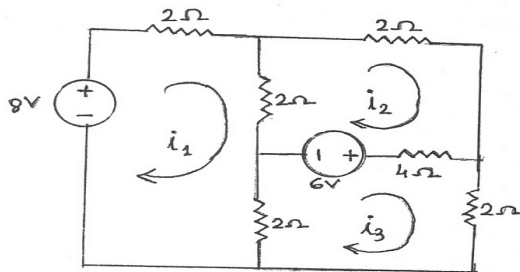


fig. 1

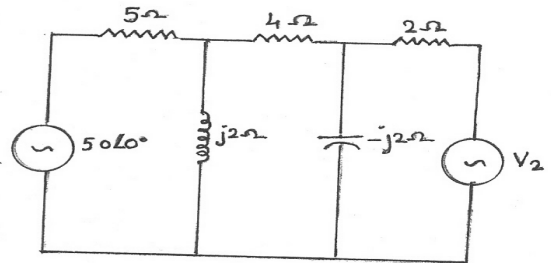


fig. 2

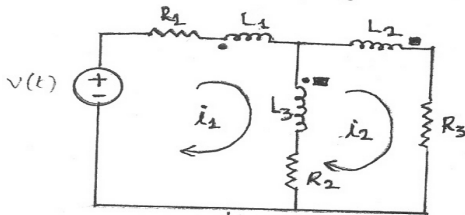


fig. 3

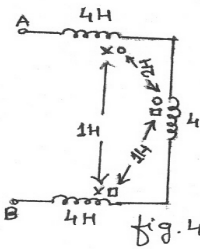


fig. 4

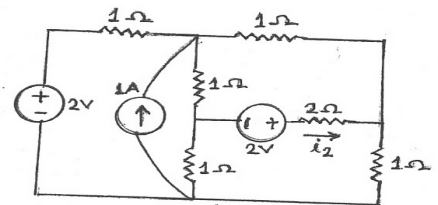


fig. 5

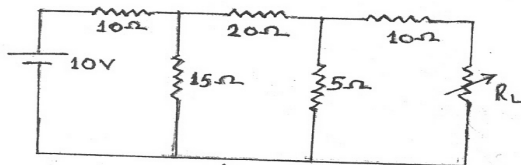


fig. 6

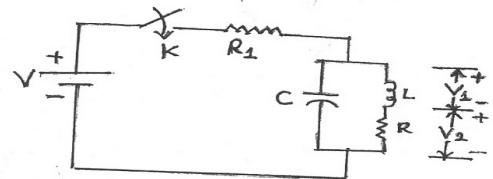


fig. 7

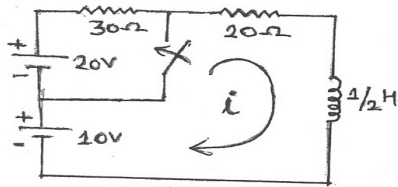


fig. 8

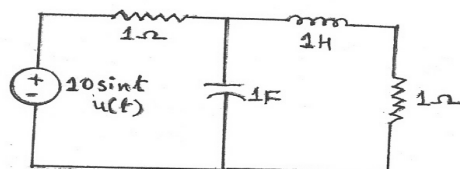


fig. 9

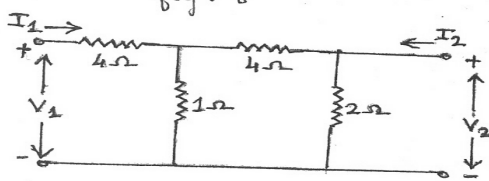


fig. 10

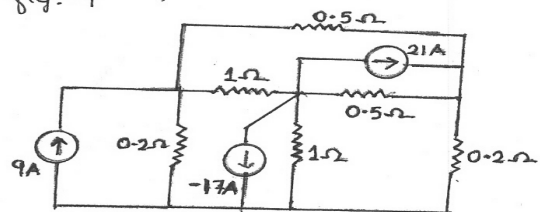


fig. 11