

UNIT-II

3. Explain the laws related to Boolean Algebra. 16(20)
4. (a) Explain the following :
- (i) Sum of product (SOP).
 - (ii) Min term. 6(8)
- (b) Find the De-morgan's equipment of
- $$F = XYZ + XZ + \bar{X}\bar{Y} + YZ$$
- 10(12)
- AND*
OR

UNIT-III

5. Design a full subtracter using 3×8 decoder and OR gate. 16(20)
6. What is Shift register ? What are its types ? List application of shift register. 16(20)

UNIT-IV

7. Discuss the various types of A/D converters and also discuss the advantages and disadvantages of each. 16(20)
8. Discuss the performance criteria of a D/A converter. How these help in selecting a D/A converter ? 16(20)

UNIT-V

(Compulsory Question)

9. Answer the following :
- (a) $A + \bar{A}.B + A.\bar{B} = A + B$.
 - (b) Comparison of Analog Versus Digital.
 - (c) Combinational *versus* Sequential.
 - (d) Advantages of CMOS over Bipolar tech.

4x4 (4x5)

Total No. of Questions - 9]
(2041)

Total Pages : 3

9202

2nd year

B.C.A. Ist Year Examination

DIGITAL ELECTRONICS

Digital Electronics

Paper : BCA-103

(New Syllabus)

Time : Three Hours]

[Max. Marks : { Regular : 80
ICDEOL : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt *five* questions in all, selecting *one* question each from four units. Question No. 9 is compulsory.

UNIT-I

1. Draw the circuit of ECL gate and explain its operation. 16(20)
2. (a) What are Intrinsic and Extrinsic semiconductor ? Explain conductivity in intrinsic semiconductor. 12(15)
- (b) Discuss the working of n-p-n transistor. 4(15)