

(2) 9332

OR

- II. a) Differentiate between the saturated and non-saturated logic. 4(5)
- b) Discuss important characteristics of CMOS digital logic family. 8(10)
- c) What are integrated circuits? 4(5)

Unit - II

III. Write the Boolean expression and truth tables as well as draw the diagrams for the following logic gates:

- a) OR                      b) AND
- c) NOR                     d) NAND       $4 \times 4 = 16 (4 \times 5 = 20)$

OR

- IV. a) Write down 8 basic Boolean laws. 8(10)
- b) What is De-Morgan's theorem? Discuss its duality. 8(10)

Unit - III

- V. a) Draw the circuit diagram of a half adder and explain its working with the help of suitable diagrams. 8(10)
- b) Draw the circuit diagram of a full adder and discuss its working. 8(10)

(3) 9332

OR

- VI. a) What are flip-flops? Explain the working of RSFF and write down its truth table 8(10)
- b) What is a master-slave FF? Discuss its working with the help of a suitable diagram. 8(10)

Unit - IV

- VII. Discuss the working of a R-2R ladder D/A converter 16(20)

OR

- VIII. Explain how can dual slope integrator method be used for A/D conversion? 16(20)

Unit - V

- IX. a) What is a semi conductor?
- b) What is a diode?
- c) What is a NOR gate?
- d) What is a truth table?
- e) What are combinational circuits?
- f) What are sequential circuits?
- g) What is a multiplexer?
- h) What is a decoder?  $8 \times 2 = 16 (8 \times 2.5 = 20)$

+++

[Total No. of Questions - 9]  
(2101)

[Total No. of Printed Pages : 3]

9332

B.C.A. I Year Examination

Digital Electronics

Paper - BCA-103

(New Syllabus)

Time : 3 Hours

Max. Marks :(Regular):80

(ICDEOL): 100

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

**Note :** Attempt **five** questions in all selecting **one** question each from first **four** units. Question no.**IX** is **compulsory**.

**Unit - I**

- I. a) Discuss the concept of energy bands in solids. **8(10)**
- b) What is a pn junction diode? How do they work in forward and reverse bias? Explain with the help of suitable diagrams **8(10)**