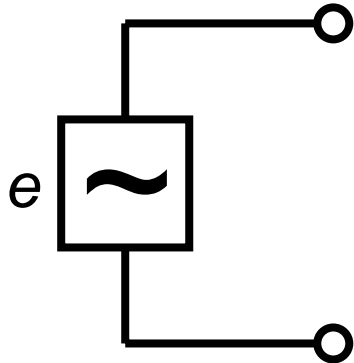


### 3. ALTERNATING CURRENT

#### Main things to learn

- Generation of alternating EMF
- Waveform and parameters
- Average and root-mean-square values
- Phase and phase difference
- Power in a.c. circuits



Source of alternating EMF

$$e = \mathcal{E}_m \sin \omega t$$

$\omega$  - angular frequency (see later)

$e$  - **instantaneous** value of the EMF

$e$  is a function of time  $e(t)$

$\mathcal{E}_m$  - amplitude of alternating EMF

#### General rule about notations



**Instantaneous** values are denoted by **lowercase** letters:  $e$ ,  $u$ ,  $i$

**Amplitudes** are denoted by **uppercase** letters:  $\mathcal{E}$ ,  $U$ ,  $I$

Question:

Why  $\sin \omega t$ , not any other periodic function?

# GENERATION OF ALTERNATING EMF

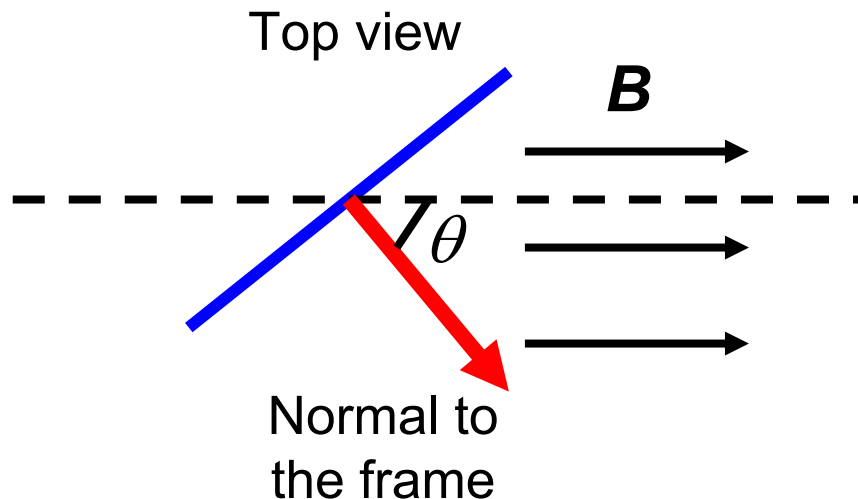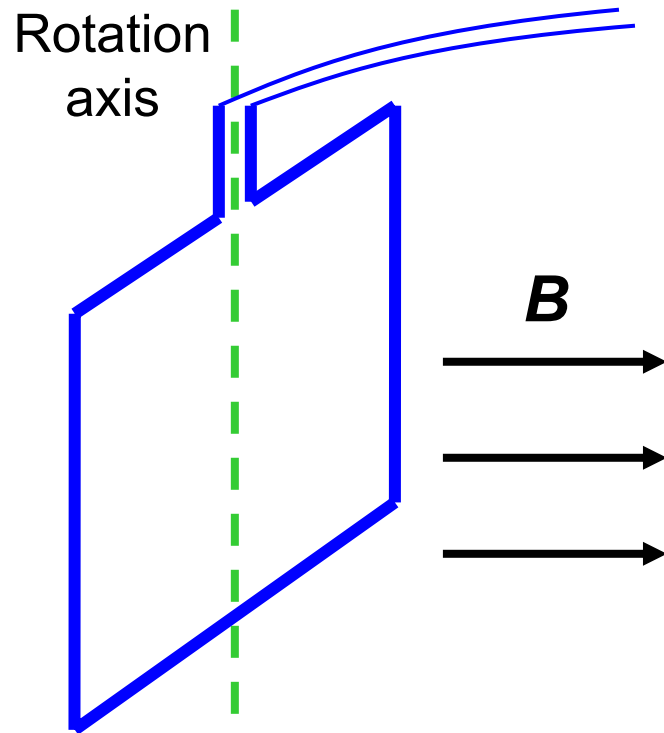

Principle of a generator

A frame of area  $S$  is rotated with angular speed  $\omega$  in magnetic field of induction  $B$

$\theta$  - angle between the induction and the normal to the plane

$$\theta = \omega t$$

Magnetic field  $\Phi$  flux through the frame is


$$\Phi = BS \cos \theta = BS \cos \omega t$$

EMF of the electromagnetic induction

$$e_i = -\frac{d\Phi}{dt} = \omega BS \sin \omega t = \mathcal{E}_m \sin \omega t$$

**Alternating EMF is directly related to the circular motion**

# WAVEFORM

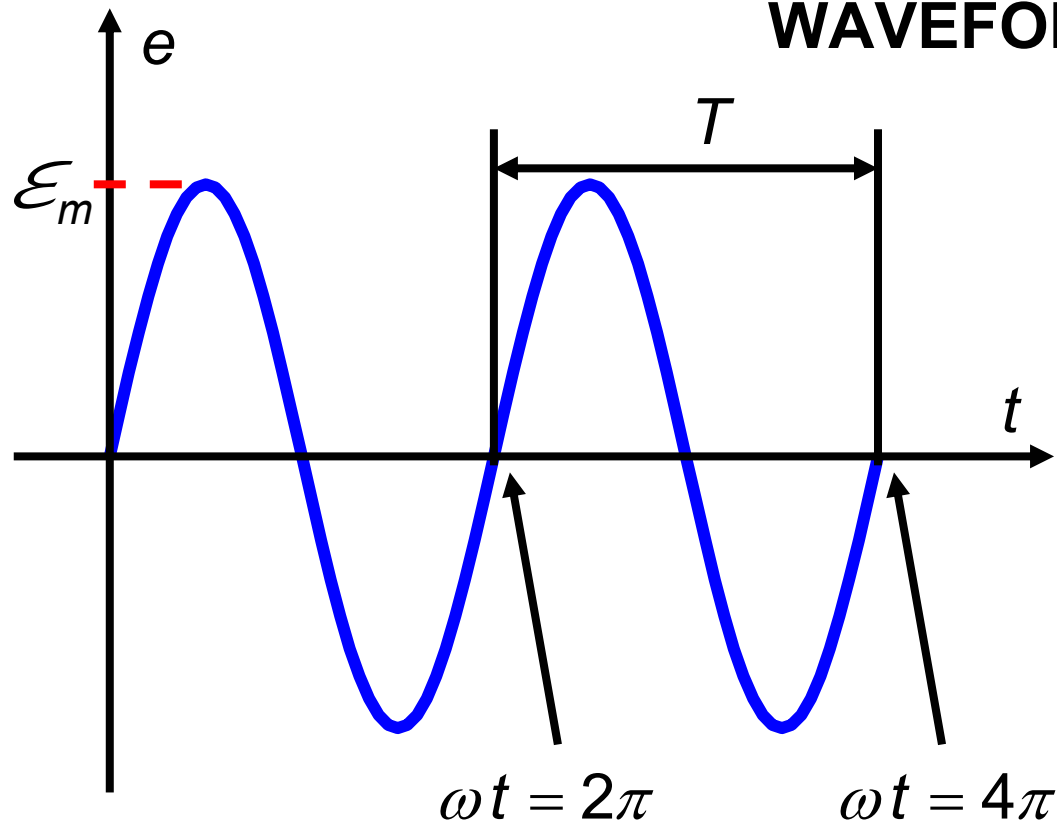

## Definitions

- Waveform** - varying voltage or current as a function of time
- Cycle** - each repetition recurring at equal intervals
- Period**  $T$  - duration of one cycle
- Frequency**  $f$  -- number of cycles in one second (hertz - Hz)

$$f = \frac{1}{T}$$


The circular motion and periodic processes are described by the same function

$$e = \mathcal{E}_m \sin \omega t$$

$\omega$  - angular speed for the circular motion or **angular frequency** for a periodic process  
(radian / sec)

$$f = \frac{\omega}{2\pi}$$
$$T = \frac{2\pi}{\omega}$$

# PARAMETERS OF ALTERNATING CURRENT

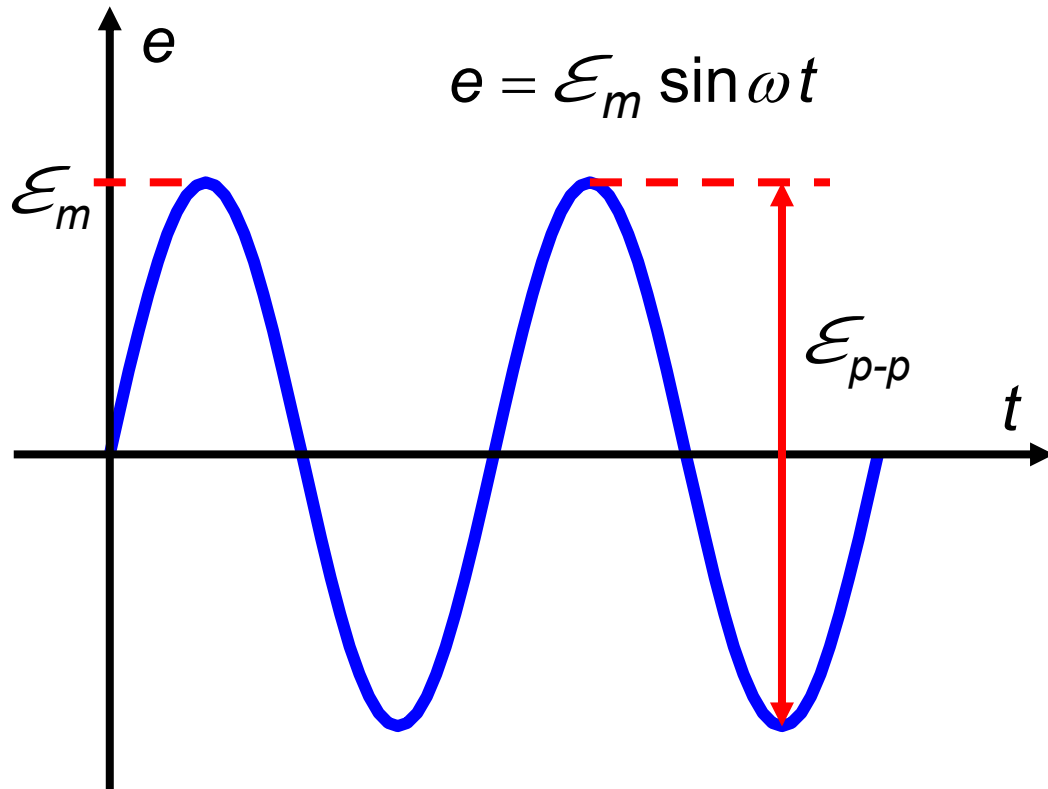

Parameters used to describe alternating quantities:

EMF, voltage, current

$\mathcal{E}_m$  - **amplitude** (maximum value)

$\mathcal{E}_{p-p}$  - **peak-to-peak** value

$$\mathcal{E}_{p-p} = 2\mathcal{E}_m$$

Also, some **average** values are required to describe alternating current

**However**


Average value of  $e = \mathcal{E}_m \sin \omega t$  equals zero!

Average of the absolute value of  $e$  (average over a half-period) is useless

The **effective** (**root-mean-square** - **r.m.s.**) value of voltage or current is typically used
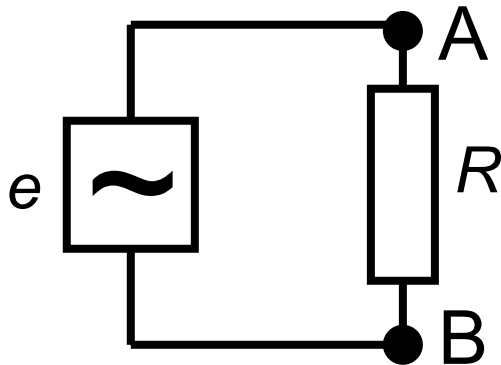
# ROOT-MEAN-SQUARE VALUES

**Root-mean-square (r.m.s.)**, or **effective** value of alternating current or voltage: **equivalent** value of **direct** current or voltage which would produce **the same heating effect** in the same resistor



$$e = \mathcal{E}_m \sin \omega t \quad ; \quad u_{AB} = U_m \sin \omega t$$

$$i = \frac{U_m}{R} \sin \omega t = I_m \sin \omega t$$

**Heating power**

$$P = i \cdot u = I_m U_m \sin^2 \omega t = I_m^2 R \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right)$$

**Average value of power:**  $P_{av} = \frac{1}{2} I_m^2 R = I_{rms}^2 R$


$$\therefore I = I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 \cdot I_m \quad ; \quad U = U_{rms} = \frac{U_m}{\sqrt{2}} = 0.707 \cdot U_m$$

**If not said otherwise, values of current or voltage are implied to be root-mean-square (effective) values.**

**Notations of amplitudes without subscripts are reserved for root-mean-square values**
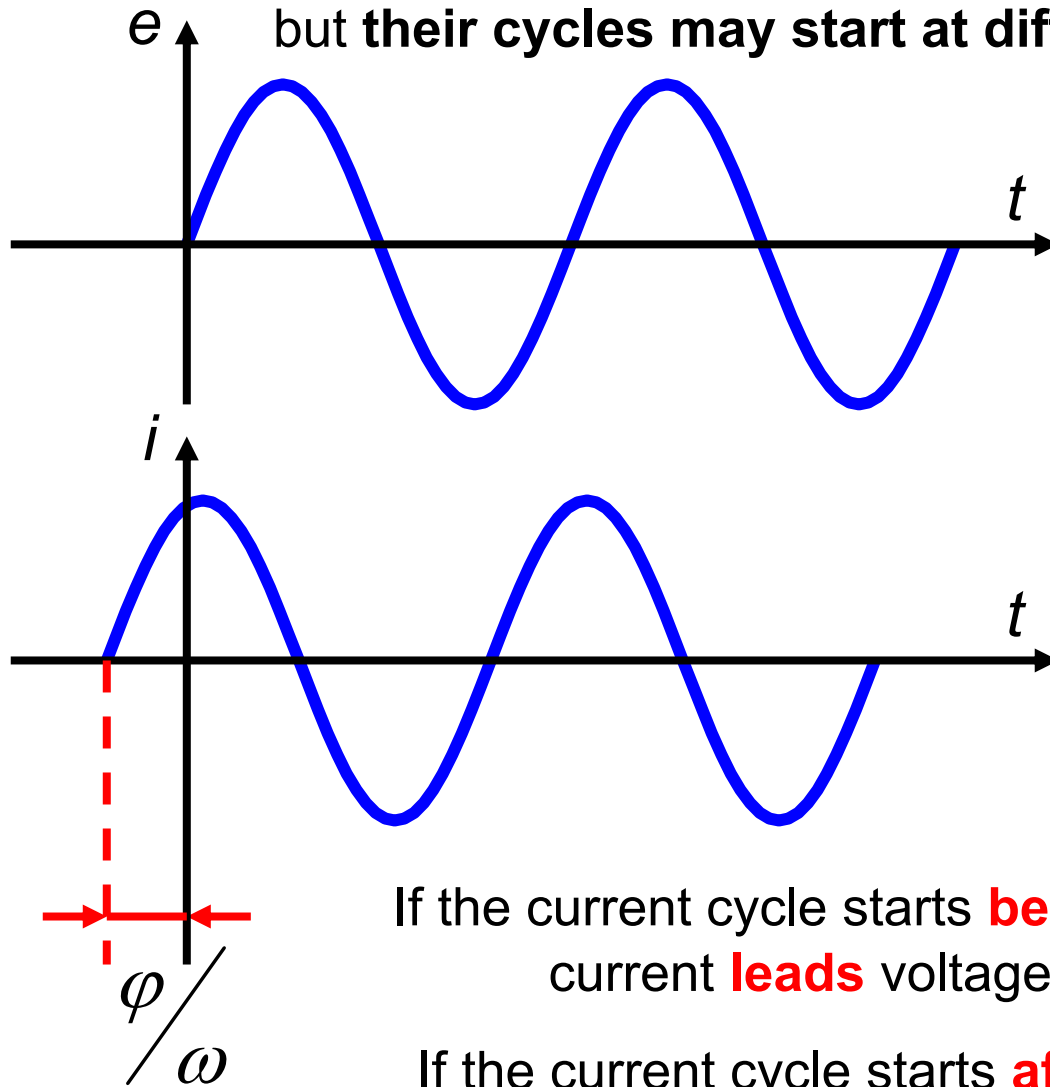
# PHASE AND PHASE DIFFERENCE

Two alternating quantities can have the same frequency, but **their cycles may start at different moments of time**



$$u = U_m \sin \omega t$$

$$i = I_m \sin(\omega t + \varphi)$$

The argument of the sine function ( $\omega t + \varphi$ ) is called **phase**.

It is equivalent to the full rotation angle for the circular motion.

The difference  $\varphi$  between the phases of two alternating quantities - **phase difference**

If the current cycle starts **before** the voltage cycle ( $\varphi > 0$ ) - current **leads** voltage, or voltage **lags** current

If the current cycle starts **after** the voltage cycle ( $\varphi < 0$ ) - current **lags** voltage, or voltage **leads** current

**Phase is a function of time while phase difference is constant**

# POWER IN A.C. CIRCUITS

If current and voltage in a circuit are in phase,

$$P = i \cdot u = I_m U_m \sin^2 \omega t = I_m U_m \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right)$$

$$P_{av} = \frac{I_m U_m}{2} = I \cdot U \quad (\text{r.m.s. values})$$

If they are not in phase,

$$P = i \cdot u = I_m U_m \sin \omega t \cdot \sin(\omega t + \varphi) = I_m U_m \frac{\cos \varphi - \cos(2\omega t + \varphi)}{2}$$

$$P_{av} = \frac{I_m U_m \cos \varphi}{2} = I \cdot U \cdot \cos \varphi \quad - \text{active power [watt]}$$

$$S = I \cdot U \quad - \text{apparent (maximum possible) power [volt ampere]}$$

The active power **may be much smaller** than the apparent power

$$\cos \varphi = \frac{\text{active power}}{\text{apparent power}} \quad - \text{power factor} \leq 1$$

# IMPORTANCE OF THE PHASE DIFFERENCE

A major problem in the analysis of a.c. circuits is due to the effect of capacitors and inductors

**which results in phase differences**

For example, we need to add two voltages  $u_1$  and  $u_2$

If the voltages  $u_1 = U_1 \sin \omega t$  and  $u_2 = U_2 \sin \omega t$  are **in phase** (their phase difference  $\varphi$  is zero), we need to add amplitudes

If they are not in phase ( $\varphi \neq 0$ ), we need to add both amplitudes and phases

$$\begin{aligned} u_1 &= U_1 \sin \omega t \quad ; \quad u_2 = U_2 \sin(\omega t + \varphi) \\ u_1 + u_2 &= U_1 \sin \omega t + U_2 \sin(\omega t + \varphi) = \\ &= (U_1 + U_2 \cos \varphi) \cdot \sin \omega t + U_2 \sin \varphi \cdot \cos \omega t = \\ &= \sqrt{(U_1 + U_2 \cos \varphi)^2 + (U_2 \sin \varphi)^2} \sin(\omega t + \beta) \end{aligned}$$

$$\beta = \tan^{-1} \left( \frac{U_2 \sin \varphi}{U_1 + U_2 \cos \varphi} \right)$$

**New methods of analysis are required**