



- viii) Circuit hazards are present in
- a) combination circuits only
 - b) combination and sequential circuit only
 - c) sequential circuits only
 - d) none of these.
- ix) When two n -bit binary numbers are added, the sum will contain at the most
- a) n bits
 - b) $n + 1$ bits
 - c) $n + 2$ bits
 - d) $n + n$ bits.
- x) In a binary R - Z - R ladder DAC, the input resistance of each input is
- a) R
 - b) $2R$
 - c) $3R$
 - d) $4R$.
- xi) The number of control lines for a 8 to 1 multiplexer is
- a) 2
 - b) 3
 - c) 4
 - d) 5.
- xii) The simplification of the Boolean expression $(A + \bar{A} + B + C)$ is
- a) 0
 - b) 1
 - c) A
 - d) BC .

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following.

$3 \times 5 = 15$

2. Explain race around condition of J-K flip-flop. Show how this condition can be avoided.
3. Simplify the Boolean function using K -map :

$$F(A, B, C, D) = \sum m(0, 1, 2, 8, 10, 11, 14, 15).$$
4. Design a full subtractor using (i) NAND gates, (ii) NOR gates.
5. Simplify algebraically, $Y = AB + A\bar{B} \left(\overline{\overline{A} \overline{C}} \right)$.



6. Define the following terms as applied to digital circuits :


- Set-up time
- Hold time
- Maximum clock frequency
- Fin in
- Power dissipation.

GROUP - C

(Long Answer Type Questions)

Answer any *three* questions. $3 \times 15 = 45$

- What is the difference between a latch and a edge triggered flip-flop ?
 - Design a clocked R-S flip-flop using NAND gates. Explain its principle of operation.
 - Design a MOD 10 synchronous binary UP counter using J-K flip-flop and necessary logic gates. $3 + 8 + 4$
- Describe the operation of successive approximation type ADC. How many clock pulses are required in worst case for each conversion cycle of an 8-bit SAR type ADC ?
 - Draw a neat diagram of a R-2R ladder type DAC.
 - Design a sequential circuit that implements the following state diagram. Use all D-type flip-flops for the design. $5 + 3 + 7$

 



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2007
DIGITAL ELECTRONICS AND INTEGRATED CIRCUIT
SEMESTER - 4

Time : 3 Hours]

[Full Marks : 70

GROUP - A
(Multiple Choice Type Questions)

1. Choose the correct alternatives for any ten of the following : 10 × 1 = 10
- i) Excess-3 coded representation of $(19)_{10}$ is
- | | | |
|-------------|--------------|--------------------------|
| a) 10011 | b) 00011001 | |
| c) 01001100 | d) 11000100. | <input type="checkbox"/> |
- ii) The decimal equivalent of the binary number $(101111.1101)_2$ is
- | | | |
|---------------------|---------------------|--------------------------|
| a) $(46.8125)_{10}$ | b) $(47.8125)_{10}$ | |
| c) $(47.8155)_{10}$ | d) $(47.8145)_{10}$ | <input type="checkbox"/> |
- iii) A 10 MHz signal is applied to a MOD 5 counter followed by a MOD 8 counter. The output frequency will be
- | | | |
|-----------|------------|--------------------------|
| a) 10 kHz | b) 2.5 kHz | |
| c) 5 kHz | d) 25 kHz. | <input type="checkbox"/> |
- iv) A 4-stage ripple counter counts upto
- | | | |
|-------|-------|--------------------------|
| a) 12 | b) 15 | |
| c) 11 | d) 4. | <input type="checkbox"/> |
- v) Which family has the better noise margin ?
- | | | |
|--------|---------|--------------------------|
| a) ECL | b) DTL | |
| c) MOS | d) TTL. | <input type="checkbox"/> |
- vi) On a Karnaugh map, grouping of OS produces
- | | | |
|---------------------------|----------------------|--------------------------|
| a) a PVS expression | b) an SOP expression | |
| c) a don't care condition | d) none of these. | <input type="checkbox"/> |
- vii) The number of flip-flops required for a MOD-10 ring counter is
- | | | |
|-------|--------|--------------------------|
| a) 10 | b) 5 | |
| c) 4 | d) 12. | <input type="checkbox"/> |