



vi) Which one of the following is a self complementing code ?

- a) Ex-3 code
- b) Gray code
- c) 8421 code
- d) None of these.


vii) A clock frequency of 100 kHz is applied to MOD - 8 followed by a decade counter. What will be the output frequency ?

- a) 12.5 kHz
- b) 10 kHz
- c) 1.25 kHz
- d) None of these.

viii) A 3-bit synchronous counter uses flip-flops with propagation delay time of 20 ns each. The maximum possible time required for change of state will be

- a) 60 ns
- b) 40 ns
- c) 20 ns
- d) none of these.

 ix) If the negative logic is used, the diode gate shown in the given figure will represent



- a) OR gate
- b) AND gate
- c) NOR gate
- d) NAND gate.

x) The minimum number of NAND gates required to implement $A + A\bar{B} + A\bar{B}C$ is equal to

- a) 0
- b) 1
- c) 4
- d) 7.



xi) In standard TTL, the "totem pole" stage refers to the

- a) multi-emitter i/p stage b) phase splitter
 c) o/p buffer d) open collector o/p stage.

xii) The SOP form of logical expression is most suitable for designing logic circuits using only

- a) XOR gates b) NOR gates
 c) NAND gates d) OR gates.

GROUP - B

(Short Answer Type Questions)

Answer any three of the following.

3 × 5 = 15

2. What is fan out ? What is the basic difference of a latch and edge triggered flip-flop ?

Design a 9-bit even parity generator circuit.

1 + 1 + 3

3. Design BCD-Excess 3 code converter using basic logic gates with proper truth table. 5

4. What is Race Around condition ? Explain the working of Master-Slave Flip-flop. 1 + 4

5. Draw a neat diagram of a R-2R ladder type DAC and explain its operation. 5

6. Draw the neat diagram of a 4 bit Bi-directional Shift register using mode control (M).

When M is logic zero then left shift and right shift for M are logic one.

5



GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following questions.

3 × 15 = 45

7. a) What do you mean by Prime implicant ? Simplify the following Boolean expression using K-map :
- $F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 11, 12, 14) + d(1, 4, 9, 10)$
- b) Design full adder using two half adders and necessary gate.
- c) Draw a network using only NAND gate to generate the function $Y = (\bar{A} + BC)$.
- (2 + 5) + 4 + 4
8. a) What are the advantage and disadvantage of totem pole ?
- b) What are the output voltages caused by logic 1 in each bit position in an 8 bit ladder if the input level for 0 level is 0 volt and for level 1 is 10 volt ?
- c) Compare the maximum conversion period of an 8 bit Digital ramp ADC and 8 bit successive approximation ADC if both utilize 1 MHz clock frequency ?
- d) With proper circuit diagram explain the operation of NMOS NAND gate. 3 + 3 + 4 + 5
9. a) Perform the conversion of D flip-flop to J-K flip-flop.
- b) What is presettable counter ? Design a MOD-5 counter that counts its natural count sequence from 000 to 100.
- c) Distinguish between a ripple counter and synchronous counter. 5 + 8 + 2
10. a) What are the differences between the Decoder and Demultiplexer ?
- b) Form a multiplexer tree to give 4X1 MUX from two 2X1 MUX.
- c) Show how a 16 input MUX is used to generate the function
- $F(A, B, C, D) = \bar{A}\bar{B}CD + BCD + A\bar{B}\bar{C} + ABC\bar{D}$. 5 + 5 + 5
11. a) What are RAM and ROM ? What is the basic difference between EPROM and EEROM ?
- b) What is the major difference between the two classes of finite state machines and proper state diagram ?
- c) What is Schmitt Trigger ? (2 + 3) + (4 + 4) + 2

END