



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2009
DIGITAL ELECTRONICS & INTEGRATED CIRCUITS
SEMESTER - 4

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) The octal equivalent of the binary number 11010111 is

a) 656

b) 327

c) 653

d) D7. ii) The minimum number of NAND gates required to implement the Boolean function $A + AB' + AB'C$ is equal to


a) zero

b) 1

c) 4

d) 7.

 iii) Identify the operation of the following logic gate circuit.



a) OR gate

b) AND gate

c) NOT gate

d) none of these.



3. Minimize the following expression in SOP form using Quine McClusky method :

$$F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + \sum d(7, 15).$$

4. Explain the race around condition. Draw the Master/Slave JK flip-flop using all NAND gates. 2 + 3
5. Implement a full-adder circuit using 3 to 8 decoder with all active high outputs and other necessary logic gates.
6. Draw and explain the circuit of 8×1 MUX using two 4×1 MUX and one 2×1 MUX.


GROUP - C

(Long Answer Type Questions)

Answer any three of the following questions.

$3 \times 15 = 45$

 7. a) Design a clocked synchronous sequential network whose state diagram is given below : 8



- b) Design a combinational circuit, which converts excess - 3 number to its corresponding BCD number. 7
8. a) Implement the following Boolean expressions using Decoder.

$$F_1(A, B, C, D) = \sum (1, 2, 5, 7, 8, 10, 12, 13).$$

5

- b) Implement a full adder circuit using minimum number of NOR gates only. 5



- c) An 8 : 1 MUX has inputs A, B, C connected to select line S_2, S_1, S_0 respectively. The data inputs I_0 to I_7 are connected as $I_1 = I_2 = I_7 = 0$,
 $I_3 = I_5 = 1, I_0 = I_4 = D, I_6 = D'$. Determine the Boolean expression of the MUX output. 5
9. a) Construct a 4-bit register with parallel load. 10
b) Describe the basic principles of Successive Approximation Method for A/D converter. 5
10. a) Design MOD-10 synchronous UP-counter using the JK flip-flops and other required logic gates. 10
b) Calculate the propagation delay for a 4-bit synchronous UP-counter when JK flip-flops are connected in series connection and parallel connection. Given propagation delay t_p (FF) equals to 30 nsec and the propagation delay of the gates used in the circuit are 20 nsec (assumed to be equal for all gates). 5
11. Write short notes on any *three* of the following : 3 × 5
- a) Tri-state gates in TTL family
 - b) Data Lock-out in a counter
 - c) EPROM
 - d) A/D converter
 - e) Parity generator.

END