

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech (EE-N)/SEM-4/EC(EE)-402/2010

2010

**DIGITAL ELECTRONICS & INTEGRATED
CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any ten of the following :

10 × 1 = 10

i) The 2's complement of the number $(01100111)_2$ is

a) 10011000

b) 10011001

c) 01100100

d) 01010111.

ii) The binary equivalent of the decimal number
 $(42.6875)_{10}$ is

a) $(101010.0100)_2$

b) $(011001.1101)_2$

c) $(010101.1011)_2$

d) $(101010.1011)_2$.

viii) Gray code for $(1011)_2$ is

- a) 1000
- b) 1100
- c) 1110
- d) none of these.

ix) 8421 is a

- a) non-weighted code
- b) weighted code
- c) complementary code
- d) none of these.

x) In general, a multiplexer has

- a) one data input, several data outputs and selection inputs
- b) one data input, one data output and one selection input
- c) several data inputs, several data outputs and selection inputs
- d) several data inputs, one data output and selection inputs.

xi) The modulus of a counter is

- a) the number of flip-flops
- b) the actual number of states in its sequence
- c) the number of times it recycles in a second
- d) the maximum possible number of states.

CS/B.Tech (EE-N)/SEM-4/EC(EE)-402/2010


xii) The carry expression of full adder circuit is

- a) $X'Y + ZX'$ b) $XY + YZ + ZX$
c) $XY' + YZ' + ZX$ d) $X'Y' + XZ' + YZ$.

xiii) The equation $\sqrt{213} = 13$ is valid for which one of the following number systems with base ?

- a) Base 8 b) Base 6
c) Base 5 d) Base 4.

 xiv) The operation of the circuit in the negative level logic system is



- a) AND b) OR
c) NAND d) NOR.

xv) The flip-flop, which is free from race around problem is

- a) R-S flip-flop
b) Master-slave JK flip-flop
c) J-K flip-flop
d) none of these.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Draw EX-OR gate circuit using minimum number of NAND gates and NOR gates.
3. Implement a 16 : 1 MUX using only 4 : 1 MUX. Show block diagram only.
4. Design and implement a full-adder circuit using a decoder and other necessary logic gates. Assume that the decoder has all active low outputs.
5. What is lock-out condition of a counter and how can we overcome it ? $3 + 2$
6. What are the specifications of D/A converter ?
7. Implement the function $F(A, B, C) = \Sigma m(0, 1, 4, 6)$ using all NOR gates.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

8. a) Simplify the logic function using Quine-McCluskey method :
$$F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$
- b) What is Don't care condition ? How is it useful to simplify a Boolean expression ? Simplify the function
$$F(A, B, C, D) = \Sigma m(1, 3, 7, 11, 15) + d(0, 2, 5).$$

$10 + 5$

CS/B.Tech (EE-N)/SEM-4/EC(EE)-402/2010

9. a) Design a 3-bit synchronous counter using J-K flip-flops.

b) Design a 3-bit binary UP/DOWN counter with a direction control M . Use J-K flip-flops in your design.

7 + 8


10. a) Describe the working principle of R-2R ladder D/A converter.

b) What is a *Sample and Hold* circuit? Why do we need to use this circuit?

10 + 5

11. a) What is the difference between a Mealy and Moore type sequential circuits?

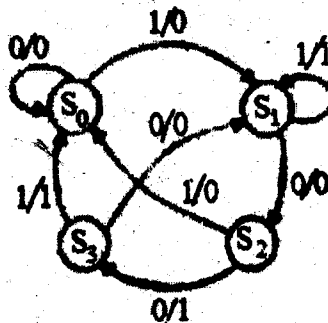b) Design a sequential circuit that implement the following state diagram. Use all D-type flip-flops for the design.



c) Describe the basic principles of successive approximation method for A/D converter.

3 + 7 + 5

12. Write short notes on any three of the following : 3×5

- a) EPROM
 - b) Odd parity generator
 - c) Carry Look Ahead
 - d) Dual slope ADC
 - e) Multiplexer
 - f) SOP and POS canonical forms of binary function.
-