

GATE Electronics & Communication Sample Paper – IV

Q-1 A circuit has a resistance of $11\ \Omega$, a coil of inductive reactance $120\ \Omega$, and a capacitor with a $120\text{-}\Omega$ reactance, all connected in series with a 110-V , 60-Hz power source. What is the potential difference across each circuit element?

- A) (a) $V_R = 110\ \text{V}$, (b) $V_L = V_C = 1.2\ \text{kV}$
- B) (a) $V_R = 120\ \text{V}$, (b) $V_L = V_C = 2.4\ \text{kV}$
- C) (a) $V_R = 4.8\ \text{V}$, (b) $V_L = V_C = 0\ \text{kV}$
- D) (a) $V_R = 5.0\ \text{V}$, (b) $V_L = V_C = 8.0\ \text{V}$

Q-2 Applying DeMorgan's theorem to the expression, we get

- A) $(A+B)+C$
- B) $A(B+C)$
- C) Both A & B
- D) None of above

Q-3 Refer Below figure to Determine the resonant frequency...

- A) $123.4\ \text{kHz}$
- B) $61.7\ \text{kHz}$
- C) $45.97\ \text{kHz}$
- D) $23.1\ \text{kHz}$

Q-4 Express the decimal number 57 in binary.

- A) 100101
- B) 111010
- C) 110010
- D) 111001

Q-5 A vertical electric dipole antenna

- a) radiates uniformly in all directions.
- b) radiates uniformly in all horizontal directions, but more strongly in the vertical direction.
- c) radiates most strongly and uniformly in the horizontal directions
- d) does not radiate in the horizontal directions

Q-6 A particle oscillates according to the equation $y=5.0 \cos 23 t$, where y is in centimeters. Find its frequency of oscillation and its position at $t=0.15\ \text{s}$.

- a) $f = 23\ \text{Hz}$, $y = -4.8\ \text{cm}$
- B) $f = 3.7\ \text{Hz}$, $y = -5.0\ \text{cm}$
- C) $f = 3.7\ \text{Hz}$, $y = -4.8\ \text{cm}$
- D) $f = 3.7\ \text{Hz}$, $y = +4.8\ \text{cm}$

Q-7 A $10.0\text{-}\mu\text{F}$ capacitor is in series with a $40.0\text{-}\Omega$ resistance, and the combination is connected to a 110-V , 60.0-Hz line. Calculate (a) the capacitive reactance, (b) the impedance of the circuit, (c) the current in the circuit, (d) the phase angle between current and supply voltage

- A) (a) $0.0038\ \Omega$ (b) $305\ \Omega$ (c) $0.415\ \text{A}$ (d) voltage lags by 8.58°
- B) (a) $266\ \Omega$ (b) $269\ \Omega$ (c) $0.409\ \text{A}$ (d) voltage lags by 81.4°
- C) (a) $16\ \text{k}\Omega$ (b) $72\ \text{k}\Omega$ (c) $2.75\ \text{A}$ (d) voltage lags by 6.63°

D) (a) 2.6 kW (b) 262W (c) 0.256 MA (d) voltage leads by 81.4°

Q-8 A circuit has a resistance of 11 W, a coil of inductive reactance 120 W, and a capacitor with a 120-W reactance, all connected in series with a 110-V, 60-Hz power source. What is the potential difference across each circuit element?

A) (a) $V_R = 110\text{ V}$, (b) $V_L = V_C = 1.2\text{ kV}$

B) (a) $V_R = 120\text{ V}$, (b) $V_L = V_C = 2.4\text{ kV}$

C) (a) $V_R = 4.8\text{ V}$, (b) $V_L = V_C = 0\text{ kV}$

D) (a) $V_R = 5.0\text{ V}$, (b) $V_L = V_C = 8.0\text{ V}$

Q-9 What is the primary function of multiplexing?

A) To match the frequency range of a signal to a particular channel.

B) To reduce the bandwidth of a signal.

C) To select one radio channel from a wide range of transmitted channels.

D) To allow a number of signals to make use of a single communications channel.

Q-10 A second step to further increase system capacity is a digital access method called TDMA (Time Division Multiple Access). Using the same frequency channelization and reuse as FDMA analog but adding a time sharing element, the effective capacity is:

A) Doubled

B) Tripled

C) Reduced by one third

D) Unchanged

Q-11 What are Pseudo-Random noise sequences, or P/N Sequences?

A) P/N Sequences are known sequences which exhibit the properties or characteristics of random sequences

B) P/N Sequences can be used to logically isolate users on the same physical (frequency) channel

C) P/N Sequences appear as random noise to everyone else, except to the transmitter and intended receiver

D) All of the above

Q-12 An op-amp integrator has a square-wave input. The output should be

A) a sine wave.

B) a triangle wave

C) a square wave.

D) pure DC.

Q-13 What is the relationship between the series and parallel resonant frequencies of a quartz crystal?

A) They are equal.

B) Parallel resonant frequency is approximately 1 kHz higher than series resonant frequency

C) Series resonant frequency is approximately 1 kHz higher than parallel resonant frequency.

D) none of the above

Q-14 Refer Below figure to Determine the resonant frequency...

A) 123.4 kHz

B) 61.7 kHz

C) 45.97 kHz

D) 23.1 kHz

Q-15 Which FET amplifier(s) has (have) a phase inversion between input and output signals?

- A) common-gate
- B) common-drain
- C) common-source
- D) all of the above