

**JUNE 2009**

**AMIETE – ET (OLD SCHEME)**

Code: AE08  
Time: 3 Hours


Subject: CIRCUIT THEORY & DESIGN  
Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


**Q.1** Choose the correct or the best alternative in the following: (2 × 10)

a.

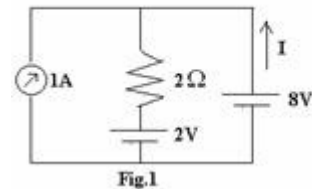

In the circuit shown, I is given by

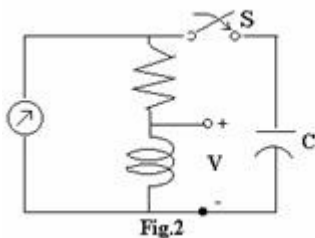- (A) -2A.
  - (B) 2A.
  - (C) 3A.
  - (D) 4A.
- b. A series RLC circuit has  $R=10,000$  ohms,  $L=10\text{mH}$ ,  $C=1\mu\text{F}$ . The resonant frequency  $\omega_0$ (rad/sec) is given by
- (A)  $10^4$ .
  - (B)  $10^2$ .
  - (C)  $10^5$ .
  - (D)  $10^3$ .



c. In the circuit shown, steady state is reached

with S-open. S is closed at  $t=0$ . At  $t=0_+$ , the voltage across 'L' is given by

- (A) 0.
- (B) 6.
- (C) -6.
- (D) 2.

d. An instantaneous voltage of  $V = 200 \sin 100t$  is applied across an element and the instantaneous power is observed to be  $p = 2000 \sin 200t$ . Then the element is a


- (A) Resistor.
- (B) Inductor.
- (C) Capacitor.
- (D) None of the above.

e. A system function  $Z(s) = \frac{V(s)}{I(s)} = \frac{1}{s+3}$ . The system is at rest for  $t < 0$ .  $i(t)$  = unit step, is given at  $t = 0$  then  $v(t)$  for  $t > 0$  is given by

- (A)  $e^{-3t}$ .
- (B)  $1 - e^{-3t}$ .
- (C)  $1 - 3e^{-3t}$ .
- (D)  $\frac{1}{3} - \frac{1}{3}e^{-3t}$ .

f. The current  $i(t)$ , through a  $10\Omega$  resistor in series with an inductance, is given by  $i(t) = 3 + 4 \sin(100t + 45^\circ) + 4 \sin(300t + 60^\circ)$  Amperes. The RMS value of the current in the circuit is

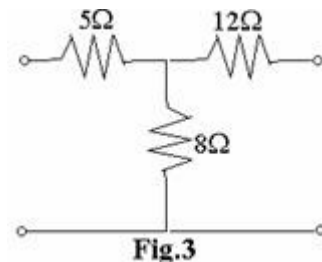- (A)  $\sqrt{41}A$ .
- (B)  $\sqrt{35}A$ .
- (C) 5A.
- (D) 11A.



g. Determine the z-parameters of the network shown in Fig.3

- (A) 5, 8, 12, 0
- (B) 13, 8, 8, 20
- (C) 8, 20, 13, 12
- (D) 5, 8, 8, 12

h. The condition  $AD-BC=1$  for a two port network implies that the network is a

- (A) reciprocal network.
- (B) lumped element network.
- (C) lossless network.
- (D) unilateral element network.

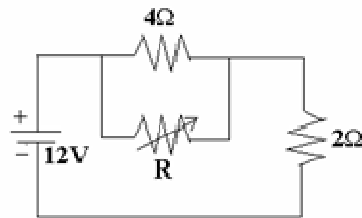


Fig.4

i. The value of the resistance 'R' in Fig.4 shown is adjusted such that the power dissipated in the  $2\Omega$  resistor is maximum. Under this condition

- (A) The value of R is zero ohm.
- (B) The value of R is 4 ohms.
- (C) The power dissipated in the 2 ohms resistor is 18W.
- (D) The value of R is 2 ohms.


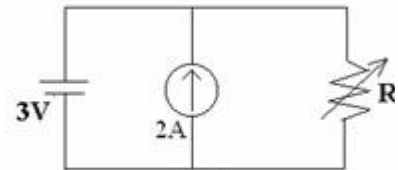


Fig.5

j. The value of R in the Fig.5 is adjusted so that Power developed by the voltage source is zero Watt. The value of R is

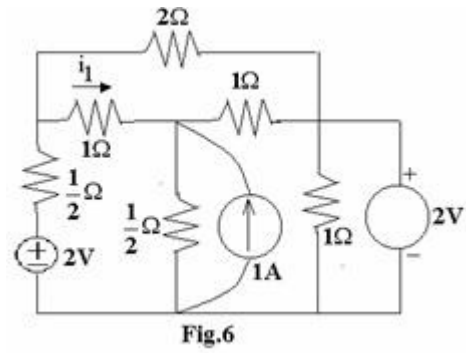
- (A)  $0\Omega$ .
- (B)  $1.5\Omega$ .
- (C)  $6\Omega$ .
- (D)  $0.667\Omega$ .

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**



**Q.2** a. For the network shown in Fig.6, determine the numerical value of the branch current  $i_1$ . All the sources in the network are time invariant.

**(8)**

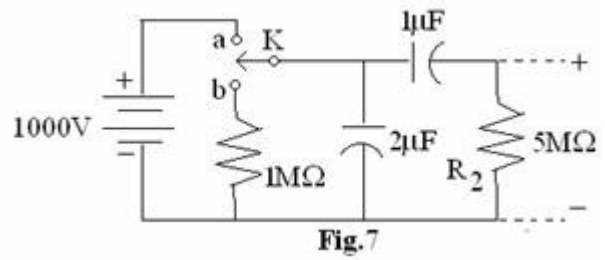

b. With switch K in a position a, the network shown in Fig.7 attains equilibrium. At time  $t=0$ , the switch is moved to position b. Find

the voltage across  $R_2$  as a function of time.

(8)

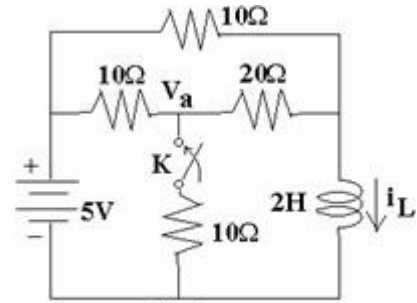


Fig.8

**Q.3** a. In the network shown in the Fig.8, a steady state is reached with the switch K open. At  $t=0$ , the switch is closed.

For the element values given,  
determine the value of  $V_{a(0-)}$  and

$V_{a(0+)}.$   
(8)

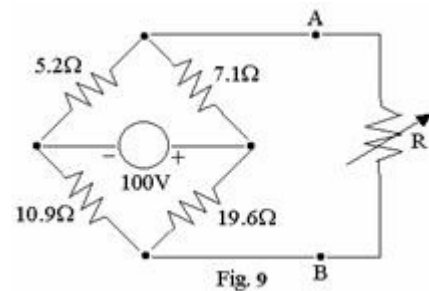


Fig. 9

b. Use the Thevenin equivalent of the network shown in Fig.9 to find the value of R which will

receive maximum power. Find also this power.

(8)

**Q.4** a. Given the ABCD parameters of two port network determine its 'Z' parameter. (8)

b. Find the y-parameters of the circuit shown in Fig.10. (8)

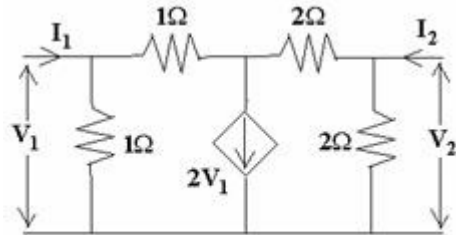


Fig.10

**Q.5** a. State the Hurwitz criteria for stability. Determine whether the given polynomial  $H(s) = s^4 + 7s^3 + 4s^2 + 18s + 6$  is Hurwitz or not? (8)

b. Explain the following:

(i) phasor

(ii) Resonance

(iii) Q

(iv)

Damping

coefficient

(8)

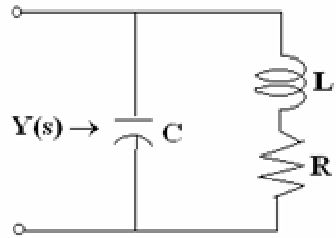


Fig.11

- Q.6** a. For the shunt peaking circuit shown in Fig.11 that the admittance  $Y(s)$  is of the

$$Y(s) = \frac{K(s-s_1)(s-s_2)}{(s-s_3)}$$

form express  $s_1$ ,  $s_2$  and  $s_3$  in terms of  $R$ ,  $L$  and  $C$ .

(8)

(8)

(8)

- b. Determine the amplitude and phase for  $F(j\omega)$  from the pole-zero plot in

s-plane for the network function  $F(s) = \frac{s^2 + 2s + 5}{(s+2)(s+1)}$  (8)

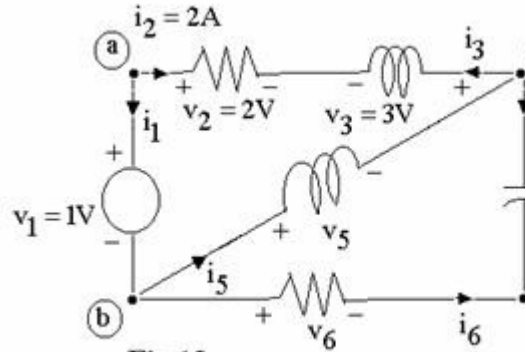


Fig.12

**Q.7** a. Check whether the function  
function. (8)

$$Z(s) = \frac{2s^2 + 2s + 1}{s^3 + s^2 + s + 2}$$

b. Using Kirchhoff's laws to the network shown in Fig.12, determine the values of  $v_6$  and  $i_5$ . Verify that the network satisfies Tellegen's theorem.

**Q.8** a. Find the networks for the following function in I Foster and I Cover

$$\text{form } Y(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}. \quad (8)$$

b. Synthesize the voltage ratio  
bridged-T network  
resistor.

$$\frac{V_2}{V_1} = \frac{s^2 + 1}{s^2 + 2s + 1}$$

as a constant resistance  
terminated in a 1Ω  
(8)

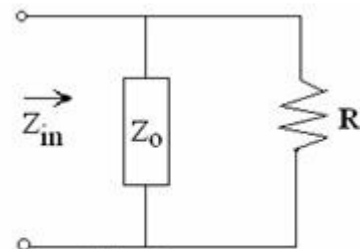


Fig.13



**Q.9** a. The input impedance for the network shown in Fig.13

is 
$$Z_{in} = \frac{2s^2 + 2}{s^3 + 2s^3 + 2s + 2}.$$

If  $Z_o$  is an LC network:

(i) find the expression for  $Z_o$ .

(ii) synthesize  $Z_o$  in a Foster series form. **(8)**

b. Synthesize the 3<sup>rd</sup> order low pass Butterworth filter terminated in a  $1\Omega$  load resistance. **(8)**