

**JUNE 2008**

Code: AE08

Subject: CIRCUIT THEORY & DESIGN

Time: 3 Hours


Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1** Choose the correct or best alternative in the following: (2x10)

a.

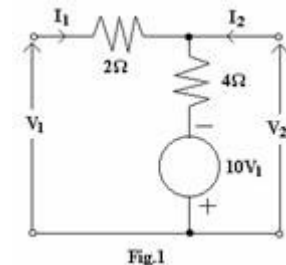

The value of  $z_{22}$  ( $\Omega$ ) for the circuit of Fig.1 is:

- |                    |                    |
|--------------------|--------------------|
| (A) $\frac{4}{11}$ | (B) $\frac{11}{4}$ |
| (C) $\frac{4}{9}$  | (D) $\frac{9}{4}$  |

b.



A possible tree of the topological equivalent of the network of Fig.2 is

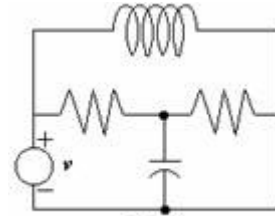


Fig.2

(A)



(B)

(C) Neither (A) nor (B)

(D) Both (A) and (B)

c. Given  $F(s) = \frac{5s+3}{s(s+1)}$  then  $f(\infty)$  is

(A) 1

(B) 2

(C) 0

(D) 3

d. The two-port matrix of an  $n:1$  ideal transformer is  $\begin{bmatrix} n & 0 \\ 0 & 1/n \end{bmatrix}$ . It describes the transformer in terms of its

(A)  $z$ -parameters.

(B)  $y$ -parameters.

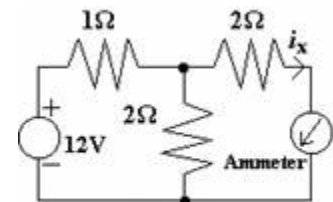



Fig. 3

(C)  $Chain$ -parameters.

(D)  $h$ -parameters.

e. The value of  $i_x$ (A) (in the circuit of Fig.3) is

- (A) 1 (B) 2  
 (C) 3 (D) 4

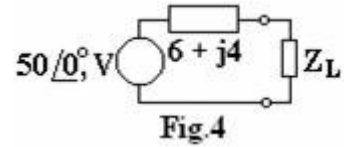

f. To effect maximum power transfer to the load,  $Z_L$  ( $\Omega$ ) in Fig.4 should be

- (A) 6  
 (B) 4  
 (C)  $7.211/33.69^\circ$   
 (D)  $7.211/-33.69^\circ$


g. The poles of a stable Butter worth polynomial lie on

- (A) parabola (B) left semicircle  
 (C) right semicircle (D) an ellipse

h. If  $F_1(s)$  and  $F_2(s)$  are p.r., then which of the following are p.r. (Positive Real)?

- (A)  $\frac{1}{F_1(s)}$  and  $\frac{1}{F_2(s)}$  (B)  $F_1(s) + F_2(s)$   
 (C)  $\frac{F_1(s) \cdot F_2(s)}{F_1(s) + F_2(s)}$  (D) All of these

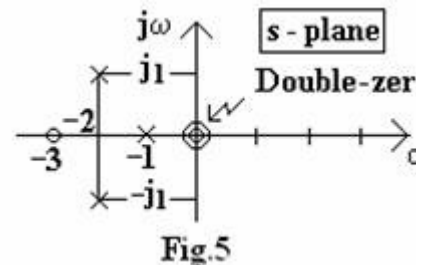i. For the pole-zero of Fig.5, the network function is



$$(A) \frac{s^2(s+1)}{(s+3)(s+2+j)(s+2-j)}$$

$$(B) \frac{s^2(s+2+j)(s+2-j)}{(s+1)(s+3)}$$

$$(C) \frac{(s+1)(s^2+4s+5)}{s^2(s+3)}$$

$$(D) \frac{s^2(s+3)}{(s+1)(s^2+4s+5)}$$

j. For a series R-C circuit excited by a d-c voltage of 10V, and with time-constant  $\tau$ , the voltage across C at time  $t = \tau$  is given by

$$(A) 10(1 - e^{-1}), V$$

$$(B) 10(1 - e), V$$

$$(C) 10 - e^{-1}, V$$


$$(D) 1 - e^{-1}, V$$

**Answer any FIVE Questions out of EIGHT Questions.**


**Each question carries 16 marks.**

**Q.2** a. Determine the loop currents,  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$  using mesh (loop) analysis for the network shown in Fig.6.

**(8)**

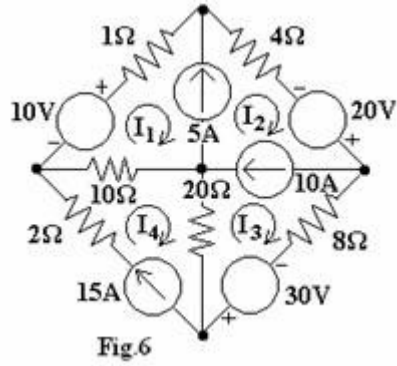

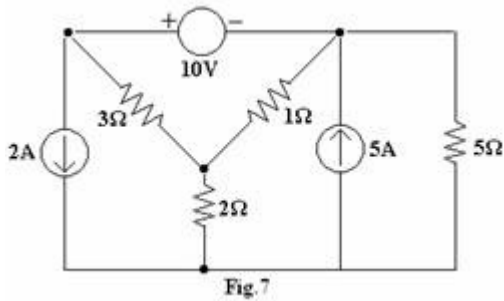- b. Find the power delivered by the 5A current source (in Fig.7) using nodal analysis. (8)



- Q.3 a. The capacitor in the circuit of Fig.8 is initially charged to 200V. Find the transient current after the switch is

closed at  
 $t=0$ .

(8)

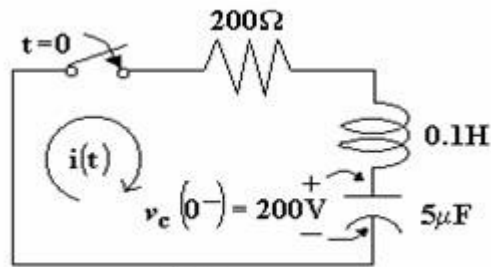


Fig.8

- b. Determine the r.m.s. value of current, voltage drops across R and L, and power loss when 100 V (r.m.s.), 50 Hz is applied across the series combination of  $R=6\ \Omega$  and  $L = \frac{8}{314}$  H. Represent the current and voltages on a phasor diagram. (8)

- Q.4 a. Using Kirchhoff's laws to the network shown in Fig.9, determine the values of  $v_6$  and  $i_5$ . Verify that the network satisfies Tellegen's theorem. (8)

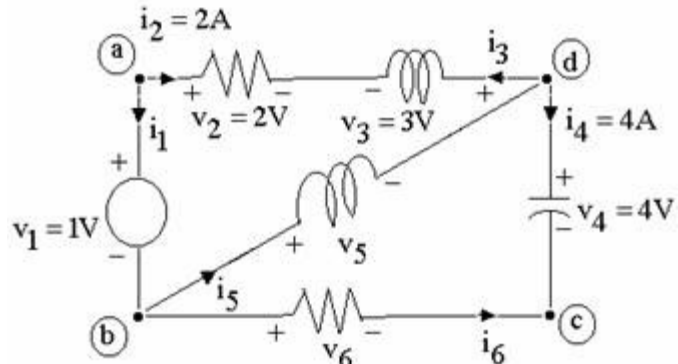


Fig.9

- b. State Reciprocity Theorem for a linear, bilateral, passive network. Verify reciprocity for the network shown in Fig.10. (8)

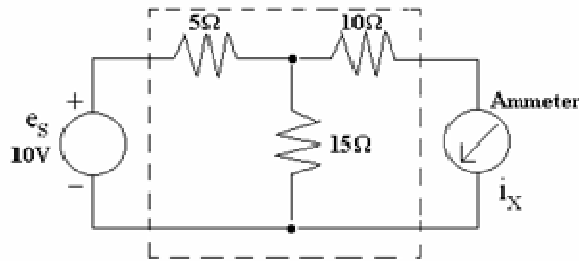


Fig.10

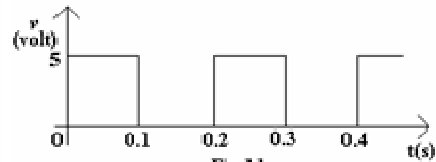


Fig.11

- Q.5 a. Find
- the r.m.s. value of the square-wave shown in Fig.11.
  - the average power for the circuit having  $z_{in} = 1.05 - j0.67, \Omega$  when the driving current is  $40 - j3, A$ .

(8)

- b. The voltage across an impedance is  $80 + j60$  Volt, and the current through it is  $3 + j4$  Amp. Determine the impedance and identify its element values, assuming frequency to be 50Hz. From the phasor diagram, identify the lag or lead of current w.r.t. voltage. (8)

- Q.6** a. Consider the function  $F(s) = \frac{s^2 + 1.03}{s^2 + 1.23}$ . Plot its poles and zeroes. Sketch the amplitude and phase for  $F(s)$  for  $1 \leq \omega \leq 10$ . (8)

- b. Determine whether the function  $F(s) = \frac{s^3 + 2s^2 + 3s + 1}{s^3 + s^2 + 2s + 1}$  is positive real or not. (8)

- Q.7** a. Given the Z parameters of a two-port network, determine its Y parameters. (8)

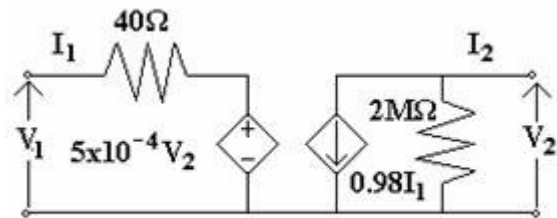


Fig.12

- b. Find the y-parameters for the two-port network of Fig.12. (8)

- Q.8** a. Synthesise a one-port L-C network whose driving-point impedance is  $Z(s) = \frac{6s^3 + 2s}{12s^4 + 8s^2 + 1}$ . (8)

- b. Determine the condition for a lattice terminated in R as shown in Fig.13 to be a constant-resistance network. (8)

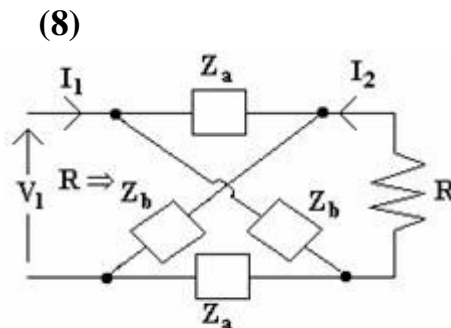


Fig.13



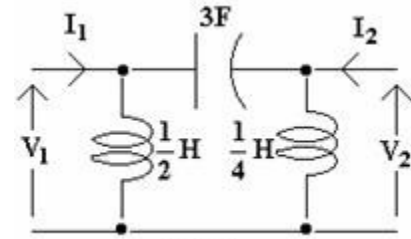


Fig.14

- Q.9** a. Find the y-parameters of the circuit of Fig.14 in terms of  $s$ . Identify the poles of  $y_{ij}(s)$ . Verify whether the residues of poles satisfy the general property of L-C two-port networks. **(8)**
- b. A third-order Butterworth polynomial approximation is desired for designing a low-pass filter. Determine  $H(s)$  and plot its poles. Assume unity d-c gain constant. **(8)**