

JJUNE 2007

Code: AE-08

Subject: CIRCUIT THEORY & DESIGN

Time: 3 Hours

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following: (2x10)

- a. The minimum amount of hardware required to make a lowpass filter is
- (A) a resistance, a capacitance and an opamp.
(B) a resistance, an inductance and an opamp.
(C) a resistance and a capacitance.
(D) a resistance, a capacitance and an inductance.
- b. A system is described by the transfer function $\frac{1}{s^2 + 2s + 1}$. The value of its step response at very large time will be close to
- (A) -1 (B) 0
(C) 1 (D) ∞
- c. A network N is to be connected to load of 500 ohms. If the Thevenin's equivalent voltage and Norton's equivalent current of N are 5Volts and 10mA respectively, the current through the load will be
- (A) 10mA (B) 5mA
(C) 2.5mA (D) 1mA
- d. A unit impulse voltage is applied to one port network having two linear components. If the current through the network is 0 for $t < 0$ and decays exponentially for $t > 0$ then the network consists of
- (A) R and L in series (B) R and L in parallel

(C) R and C in parallel

(D) R and C in series

- e. The two-port matrix of an $n:1$ ideal transformer is $\begin{bmatrix} n & 0 \\ 0 & 1/n \end{bmatrix}$. It describes the transformer in terms of its
- (A) z -parameters. (B) y -parameters.
(C) Chain-parameters. (D) h -parameters.

- f. If $F(s)$ is a positive-real function, then $\text{Ev}\{F(s)\}|_{s=j\omega}$
- (A) must have a single zero for some value of ω .
- (B) must have a double zero for some value of ω .
- (C) must not have a zero for any value of ω .
- (D) may have any number of zeros at any values of ω
- but $\text{Ev}\{F(s)\}|_{s=j\omega} \geq 0$ for all ω .

- g. The poles of a Butterworth polynomial lie on
- (A) a parabola. (B) a left semicircle.
(C) a right semicircle. (D) an ellipse.

- h. A reciprocal network is described by $z_{21} = \frac{s^3}{3s^2 + 2}$ and $z_{22} = \frac{s^3 + 4s}{3s^2 + 2}$. Its transmission zeros are located at
- (A) $s = 0$ (B) $s = \pm j2$
(C) $s = 0$ and at $s = \pm j2$ (D) $s = 0$ and at $s = \infty$

- i. In order to apply superposition theorem, it is necessary that the network be only
- (A) Linear and reciprocal.
(B) Time-invariant and reciprocal.
(C) Linear and time-invariant.
(C) Linear.
- j. The Q-factor of a parallel resonance circuit consisting of an inductance of value 1mH, capacitance of value 10^{-5} F and a resistance of 100 ohms is
- (A) 1 (B) 10
(C) 20π (D) 100

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Write minimum number of integro-differential mesh equations required to solve for all node voltages and branch currents in the network of Fig.Q2. The term v_g should not be present in your equations. (6)

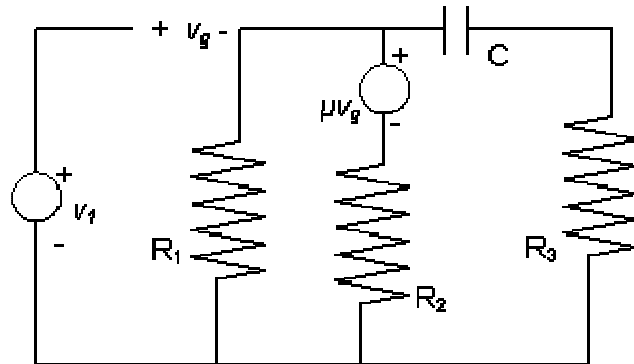


Fig.Q2

- b. Derive the condition for maximum power transfer from a source whose internal impedance is resistive to a load which is a series combination of a resistance and a reactance. (10)
- Q.3** a. In Fig.Q3, $v_1 = 230\sqrt{2} \cos 2\pi 50t$ and the initial voltage on the capacitor is 50V. If the switch is closed at $t=0$, determine the current through the capacitor and the voltage across the inductor at $t=0+$. (6)
- b. Assume that the switch in Fig.Q3 has been closed for a long time. Using phasor methods, find the current drawn from the source and the circuit impedance, resistance and reactance. (10)

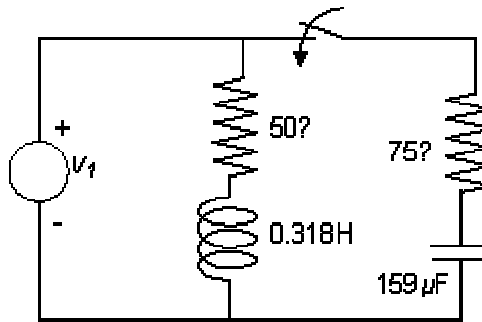


Fig.Q3

- Q.4** a. Find the Thevenin's voltage and the Thevenin's equivalent resistance across terminals a-b in Fig.Q4. Assume $V_1=10V$, $R_1=5$ Ohms, $R_2= 2$ Ohms, $r= 1$ Ohm, $I=2A$ and $V=12V$. Determine the power drawn from the 12V source when the load is connected. (8)

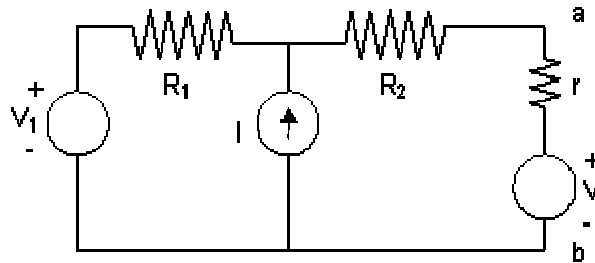


Fig.Q4

- b. Consider a series resonance circuit consisting of a 10 Ohms resistance, a 2mH inductance and a 200nF capacitance. Determine the maximum energy stored, the energy dissipated per cycle and the bandwidth of the circuit. Write the normalized form of the admittance for this circuit. (8)

- Q.5** For the given network function $F(s) = \frac{26}{s^2 + s + 26}$, draw its pole-zero plot and determine (i) ω_{max} , the frequency at which $F(j\omega)$ attains its maximum value, (ii) $|F(j\omega_{max})|$, (iii) the half power points, and (iv) the

magnitude of the function at half power points. Using this information, draw a neat sketch of the magnitude and the phase responses. (16)

Q.6 Determine the h-parameters of the network shown in Fig.Q6. (16)

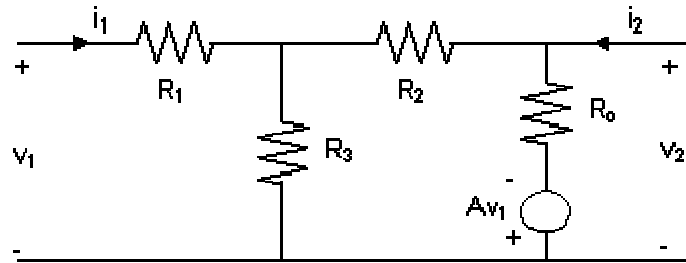


Fig.Q6

Q.7 a. Determine if the function $F(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$ is positive real. (10)

b. Given that $\text{Re } G(j\omega) = \frac{\omega^4 + 21\omega^2}{\omega^4 + 17\omega^2 + 16}$, determine a realizable $G(s)$. (6)

Q.8 a. Synthesise the voltage transfer function $T(s) = \frac{2Ks}{s^3 + 2s^2 + 2s + 1}$ by any method and obtain the realized value of K . (9)

b. Determine the voltage transfer function of the network shown in Fig.Q8. All resistances are 1 ohm, inductors 1H and capacitors 1F. (7)

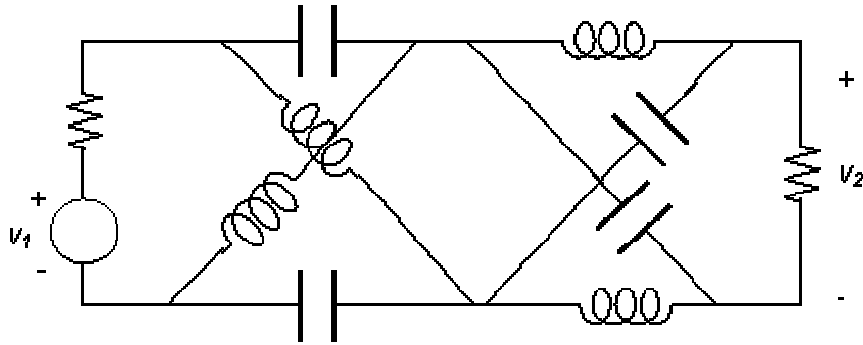


Fig.Q8

- Q.9** a. Realize the impedance $Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{(s^2 + 4)s}$ in three different ways. (12)
- b. Show that the filter described by the transfer function

$$H(s) = \frac{1}{(s^2 + 0.76536s + 1)(s^2 + 1.84776s + 1)}$$

is a filter.

a

lowpass
(4)