

DECEMBER 2005

Code: A-08

Subject: CIRCUIT THEORY & DESIGN

Time: 3 Hours

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following: (2x10)

- a. The free response of RL and RC series networks having a time constant τ is of the form:

(A) $A + Be^{-\frac{t}{\tau}}$

(B) $Ae^{-\frac{t}{\tau}}$

(C) $Ae^{-t} + Be^{-\tau}$

(D) $(A + Bt)e^{-\frac{t}{\tau}}$

- b. A network function can be completely specified by:

(A) Real parts of zeros

(B) Poles and zeros

(C) Real parts of poles

(D) Poles, zeros and a scale factor

- c. In the complex frequency $s = \sigma + j\omega$, ω has the units of rad/s and σ has the units of:

(A) Hz

(B) neper/s

(C) rad/s


(D) rad

- d. The following property relates to LC impedance or admittance functions:

(A) The poles and zeros are simple and lie on the $j\omega$ -axis.

(B) There must be either a zero or a pole at origin and infinity.

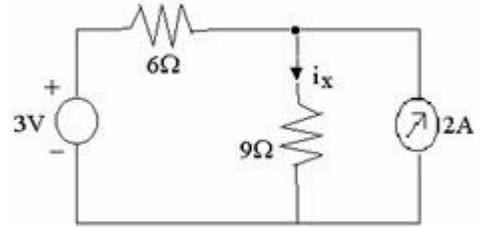
(C) The highest (or lowest) powers of numerator or denominator differ by unity.



(D) All of the above.

e. The current i_x in the network is:

(A) 1A (B) $\frac{1}{2}A$

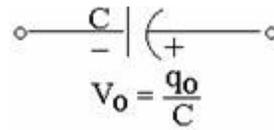


(C) $\frac{1}{3}A$ (D) $\frac{4}{5}A$

f. The equivalent circuit of the capacitor


shown is



(A)

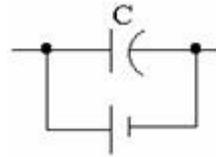


(B)

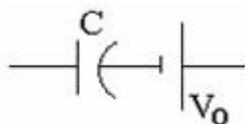

(C)

(D)

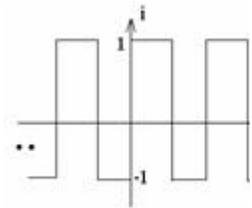

g. The value of $\left(\frac{I_{rms}}{I_{max}}\right)$ for the wave form shown is


(A) $\sqrt{2}$

(B) 1.11

(C) 1

(D) $1/\sqrt{2}$

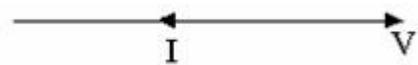h. The phasor diagram for an ideal inductance having current I through it and voltage V across it is :



(A)

(B)



(C)

(D)


- i. If the impulse response is realisable by delaying it appropriately and is bounded for bounded excitation, then the system is said to be :
- (A) causal and stable (B) causal but not stable
 (C) noncausal but stable (D) noncausal, not stable


$$\sum_{k=1}^b v_k(t) i_k(t) = 0,$$

- j. In any lumped network with elements in b branches, for all t , holds good according to:
- (A) Norton's theorem. (B) Thevenin's theorem.
 (C) Millman's theorem. (D) Tellegen's theorem.


**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

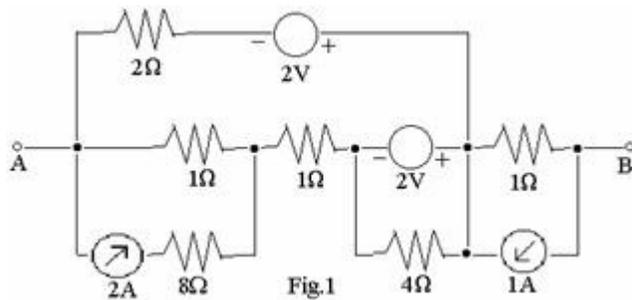- Q.2** a. Simplify the network, shown in Fig.1, using source transformations: (8)




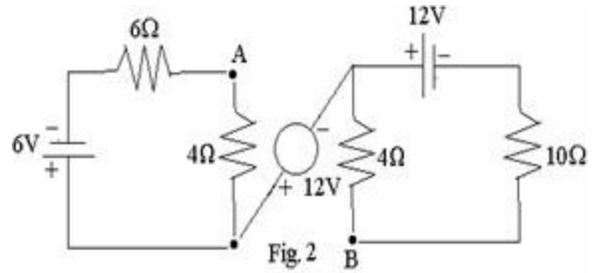

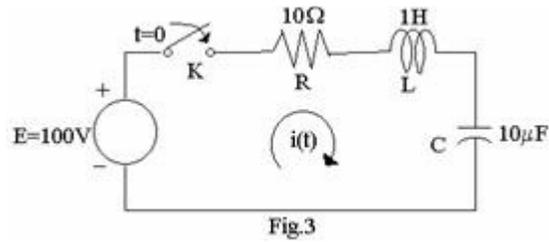
- b. Using any method, obtain the voltage V_{AB} across terminals A and B in the network, shown in Fig.2: (8)



- Q.3** a. For the network shown in Fig.3, the switch is closed at $t = 0$. If the current in L and voltage across C are 0 for $t < 0$, find $i(0^+)$, $\left. \frac{di(t)}{dt} \right|_{t=0^+}$, $\left. \frac{d^2i(t)}{dt^2} \right|_{t=0^+}$. (8)

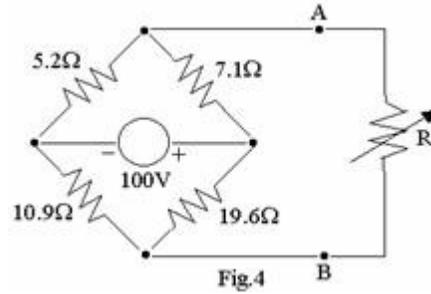


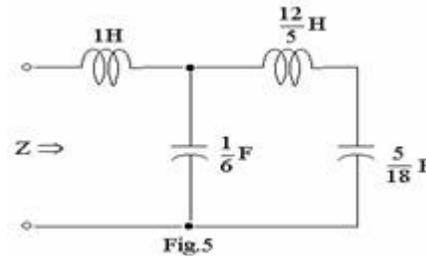- b. Use the Thevenin equivalent of the network shown in Fig.4 to find the value of R which will receive maximum power. Find also this power. (8)



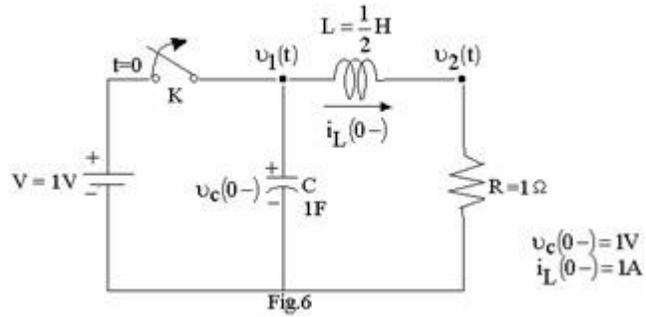
- Q.4 a. Express the impedance $Z(s)$ for the network shown in Fig.5 in the

form: $Z(s) = K \frac{N(s)}{D(s)}$. Plot its poles and zeros. From the pole-zero plot, what can you infer about the stability of the system? (8) the




- b. Switch K in the circuit shown in Fig.6 is opened at $t = 0$. Draw the Laplace transformed network for $t > 0+$ and find the voltages $v_1(t)$ and $v_2(t)$, $t > 0+$. (8)

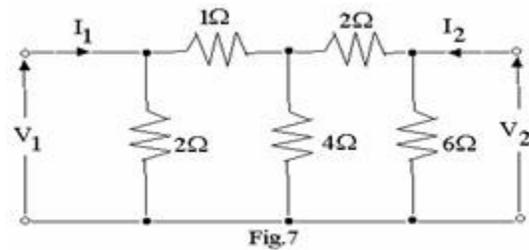- Q.5 a. Given the ABCD parameters of a two-port, determine its z-parameters. (8)



- b. Find the y-parameters for the network shown in Fig.7. (8) in

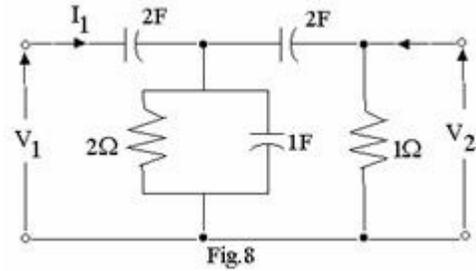- Q.6** a. Distinguish between Chebyshev approximation and maximally flat approximation as applicable to low pass filters. What is the purpose of magnitude and frequency scaling in low pass filter design? (8)




- b. Show that the voltage-ratio transfer-function of the ladder network shown in Fig.8 is given

$$\frac{V_2(s)}{V_1(s)} = \frac{8s^2}{12s^2 + 12s + 1}$$

by:


(8)

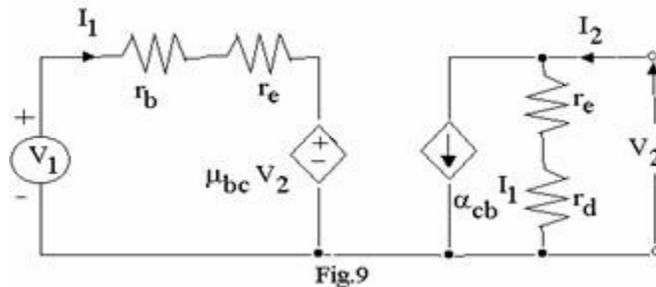- Q.7** a. Explain the following:
 (i) Phasor. (ii) Resonance. (iii) Q (iv) Damping coefficient. (8)
- b. Determine the Thevenin equivalent circuit of the network shown in Fig.9. (8)



- Q.8** a. Test whether:
 (i) the polynomial $F_1(s) = s^4 + s^3 + 2s^2 + 3s + 2$ is Hurwitz; and
 (ii) the function $F_2(s) = \frac{Ks}{s^2 + \alpha}$ is positive real, where α and K are positive constants. (8)

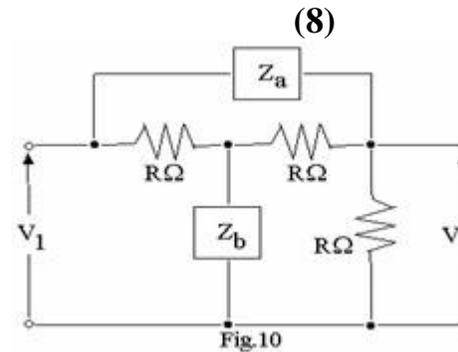- b. A system admittance function $Y(s)$ has two zeros at $s = -2, -3$ and two poles at $s = -1, -4$, with system constant = 1. Synthesise the admittance in the form of three parallel branches: $R_1, R_2 - L_2$ in series, and $R_3 - C_3$ in series.



- Q.9** a. Explain the meaning of “zeros of transmission”. Determine the circuit elements of the constant-resistance bridged-T circuit, shown in Fig.10, that provides the voltage-ratio:

$$\frac{V_2(s)}{V_1(s)} = \frac{s^2 + 1}{s^2 + 2s + 1}$$

.Assume
(8)

R=1

Ω

- b. Synthesise a ladder network whose driving-point impedance function is given

by
$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

(8)