

Answer Keys

1	D	2	A	3		4	A	5	A	6	A	7	B
8	D	9	D	10	D	11	D	12	C	13	D	14	C
15	C	16	B	17	B	18	A	19	C	20	A	21	C
22		23	C	24	B	25		26		27	C	28	D
29		30		31	D	32		33	B	34	A	35	B
36	A	37	B	38	A	39	D	40	C	41	C	42	B
43	B	44	A	45		46	C	47		48		49	
50		51	D	52	B	53	A	54	C	55	A	56	
57	D	58	D	59	C	60	A						

1. (D)


$$\left| e^{j(x+iy)} \right| = \left| e^{-y+jx} \right| = e^{-y} \left| e^{jx} \right| = e^{-y} [\cos x + j \sin x] = e^{-y}$$

4. (A)

$$\frac{x}{\sqrt{x^2 + y^2 + z^2}}, \frac{y}{\sqrt{x^2 + y^2 + z^2}}, \frac{z}{\sqrt{x^2 + y^2 + z^2}} \Rightarrow (x, y, z)$$

Given $r=1$, \therefore

6. (A)

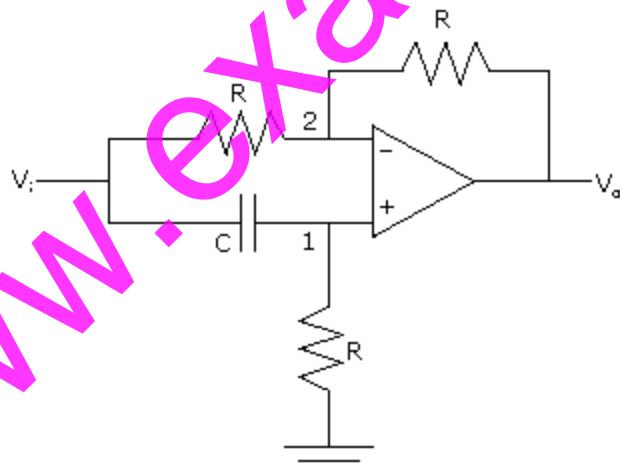

$$V_+ = \left[\frac{sCR}{1+sCR} \right] V_i$$

$$V_- = V_+$$

$$\frac{V_i - \frac{sCR V_i}{1+sCR}}{R} = \frac{\frac{sCR}{1+sCR} V_i - V_o}{R} \Rightarrow \frac{V_o}{V_i} = \frac{sCR-1}{sCR+1}$$

gain = 1, Hence it is APF

7. (B)

It is an AND gate

8. (D)

		PQ				R'P'Q		
		00	01	11	10			
RS		00	0	1	0	0		
		01	0	1	1	1		
P'RS		11	1	1	1	0		
		10	0	0	1	0		
RPQ								

9. (C)

JK	Q(t+1)
00	Q(t)
01	0
10	1
11	Q(t̄)

10. (C)

$$(1.375)_{10} = (1.011)_2$$

$$0.375 \times 2 = 0.75$$

$$0.75 \times 2 = 1.5$$

$$0.5 \times 2 = 1$$

12. (C)

$$\text{For } 2\sin(2\pi), \quad T_1 = \frac{2\pi}{2\pi} = 1\text{s}$$

$$3\sin(3\pi t), \quad T_2 = \frac{2\pi}{3\pi} = \frac{2}{3}\text{s}$$

$$\text{LCM}\left(1, \frac{2}{3}\right) = 2 \text{ sec}$$

13. (D)


$$x(t) = \sin t$$

$$\omega = 1$$


$$\frac{1}{\sqrt{1+\omega^2}} \angle -\tan^{-1} \omega = \frac{1}{\sqrt{2}} \angle (-\pi/4)$$

$$\therefore \text{output} = \frac{1}{\sqrt{2}} \sin (t - (\pi/4))$$

14. (C)

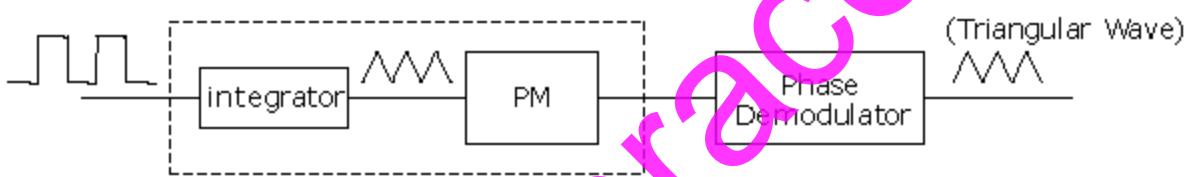

16. (B)

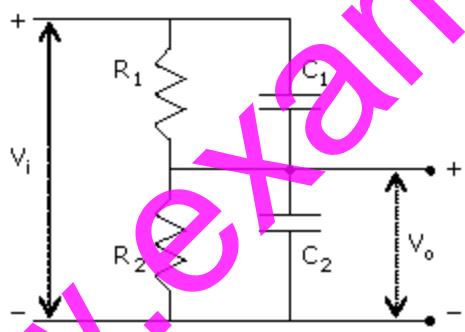

$$K = \frac{V_i}{V_o}, \quad R_2 = C_1 [K - 1]; \quad R_2 = \frac{R_1}{K - 1}$$

$$K = 10$$

$$R_2 = 1M\Omega$$

$$C_2 = 45\text{pF}; \quad C_1 = \frac{45\text{pF}}{g} = 5\text{pF}$$

17. (B)

$$I_{fs} = 1 \text{ mA}; R_m = 100\Omega$$

$$V = 10V$$

$$V = I_m (R_m + R_s)$$

$$R_s = \frac{V}{I_{fs}} - R_m = \frac{10}{1 \text{ mA}} - 100 = 10,000 - 100 = 9.9k\Omega$$

21. (C)

$$\begin{bmatrix} -3 & 0 \\ 0 & -1 \end{bmatrix}$$

Hence eigen values are -3,-1

24. (B)

$$x^3 = j = e^{j\pi/2}$$

$$x = e^{j\pi/6} = \cos 30 + j \sin 30 = \frac{\sqrt{3}}{2} + j \frac{1}{2}$$

28. (D)

$R_L = 2\Omega$, max power transfer thereon

$$P_{max} = 6.125W$$

31. (D)

For thermistor,

$$R_{T_1} = R_{T_2} e^{-\beta \left(\frac{1}{T_1} - \frac{1}{T_2} \right)}$$

For P: $\beta = 3000\text{K}$, At $T_2 = 298\text{K}$, $R_{T_2} = 2\text{k}\Omega$

For Q, $\beta = 3000\text{K}$, At $T_2 = 298\text{K}$, $R_{T_2} = 2\text{k}\Omega$

At $T_1 = 373\text{K}$,

$$R_{T_1P} = (2k) e^{-3000 \left[\frac{1}{373} - \frac{1}{298} \right]} \quad \dots \dots \dots (1)$$

$$R_{T_1Q} = (2k) e^{-3000 \left[\frac{1}{373} - \frac{1}{298} \right]} \quad \dots \dots \dots (2)$$

$$\frac{\text{Eqn. 1}}{\text{Eqn. 2}} = 0.509$$

33. (B)

By KCL at V_o ,

$$\frac{V_i}{1k} = \frac{0 - V_o}{10k} + \frac{0 - [3.2 - V_o]}{10k} \Rightarrow V_o = -6.6V$$

34. (A)

$$\text{Input resistance} = \frac{V_i}{I}$$


$$I = \frac{V_i - 0}{R} + \frac{V_i - V_o}{2R} \quad \text{KCL at node 1.}$$

$$\frac{V_i - 0}{R} = \frac{0 - V_o}{3R} = \frac{-V_o}{3R} \quad \text{KCL at node 2.}$$

$$V_o = -3V_i$$

$$I = \frac{V_i}{R} + \frac{V_i + 3V_i}{2R} = \frac{2V_i}{R} + \frac{V_i}{R} = \frac{3V_i}{R}$$

$$\frac{V_i}{I} = R / 3$$

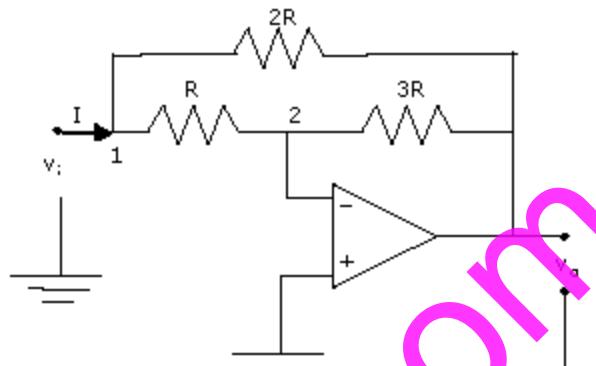

35. (B)

It is a limited circuit

It makes a transition from +5V to -5V.

$$30(1 - e^{-t/RC}) = 5 \times \frac{4.7}{9.4} = \text{Voltage across bottom } \sim 7\text{k}\Omega$$

$$= V_+$$

$$R = 10\text{k}\Omega; C = 1\mu\text{F}; [t = 8.7 \text{ m sec}]$$

38. (A)

XRAA \rightarrow A = 00H

40. (C)


$$3 + 2 \sin t \cos 2t = 3 + [\sin(t+2t) + \sin(t-2t)]$$

$$= 3 + \sin 3t - \sin t$$

It is of $a + b \sin \theta + c \sin 3\theta$

$$\text{RMS value} = \sqrt{a^2 + \left(\frac{b}{\sqrt{2}}\right)^2 + \left(\frac{c}{\sqrt{2}}\right)^2} = \sqrt{9 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{10}$$

44. (A)

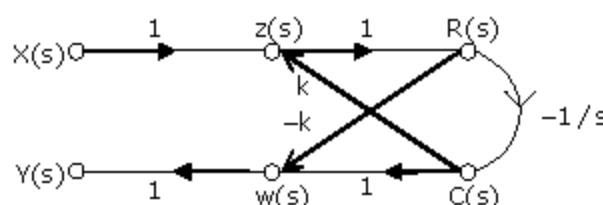

$$Z(s) = kC(s) + X(s)$$

$$y(s) = W(s)$$

$$C(s) = \frac{-1}{s}R(s)$$

$$R(s) = Z(s)$$

$$W(s) = C(s) - kR(s)$$

$$\begin{aligned}\therefore y(s) &= c(s) - k z(s) \\ &= \frac{-1}{s} C(s) - k Z(s) \\ &= -\left[\frac{1+ks}{s}\right] Z(s) = X(s)\end{aligned}$$

$$Z(s) = k \left(-\frac{1}{s}\right) Z(s) + X(s)$$

$$\left(1 + \frac{k}{s}\right) Z(s) = X(s)$$

$$\boxed{\therefore \frac{Y(s)}{X(s)} = \frac{-(1+ks)}{k+s}}$$

46. (B)

Characteristic equation is

$$|sI - F| = 0$$

$$\left| \begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} - \begin{pmatrix} 0 & 1 \\ -4 & -2 \end{pmatrix} \right| = \begin{vmatrix} s & -1 \\ 4 & s+2 \end{vmatrix} = s(s+2) + 4 = 0$$

$$= s^2 + 2s + 4 = 0; \quad \boxed{s=0.5}$$