

S 114

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2005.

Second Semester

Electronics and Communication Engineering

EC 142 — CIRCUIT THEORY


Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

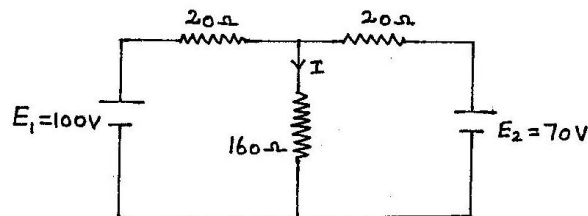
1. State Kirchoff's law.
2. What do you understand by Nodal analysis?
3. State the compensation theorem.
4. For the circuit shown in Fig., find I using Millmann's theorem.




5. Define series resonance.
6. State the usefulness of tuned circuits.
7. Distinguish between the forced response and free response of a circuit.
8. How is a transient state attained in a circuit?
9. Define tieset of a graph.
10. Define linear graph and subgraph.

PART B — (5 × 16 = 80 marks)

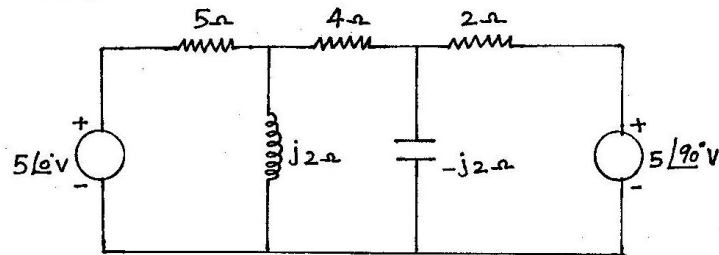
11. (i) Determine the node voltage for the circuit shown in figure by Nodal analysis. (8)



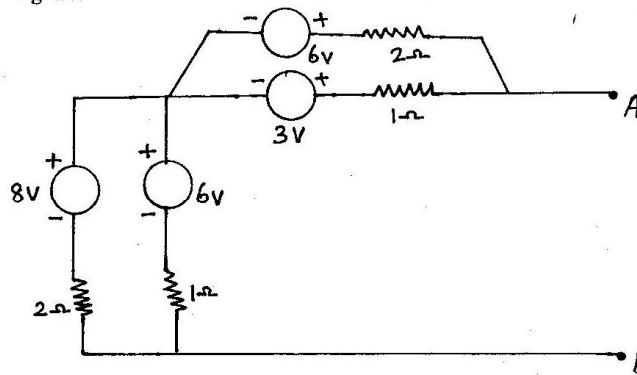
- (ii) Using source transformation techniques, simplify the network shown in figure. (8)



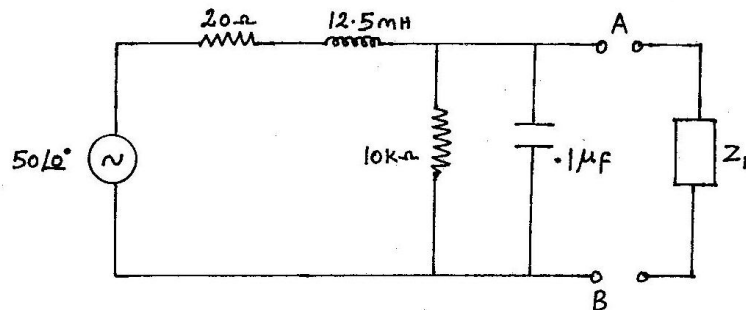12. (a) (i) For the circuit shown in Fig, find the load impedance Z_L that maximizes the power transfer and also find the power transferred with the conjugate matched load impedance ($\omega = 500$ r/s). (8)




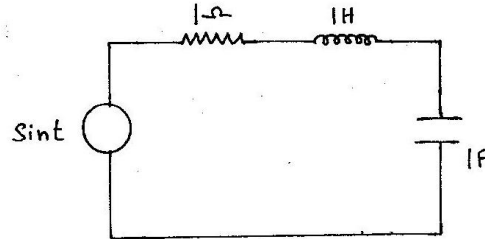- (ii) Verify Tellegen's theorem for the network shown in Fig. (8)




Or

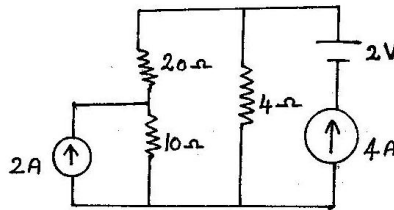
- (b) (i) A d.c. generator supplies current to a series combination of $1\text{ k}\Omega$ and $3\text{ k}\Omega$ resistors. A voltmeter is used to measure the voltage across $1\text{ k}\Omega$ resistor. Using Thevenin's theorem, determine the lowest resistance which the voltmeter must have that the measurement error shall not exceed 1%. (8)
- (ii) Determine V_{AB} using superposition theorem in the circuit shown in fig. (8)



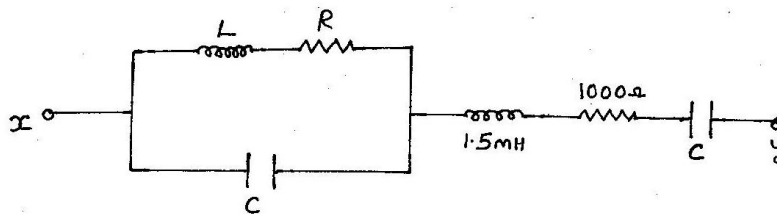13. (a) (i) Determine the values of R , L and C for the network shown in Fig. to have a resistance of $11\text{ k}\Omega$ across the terminals xy ($f_0 = 10\text{ kHz}$). (8)




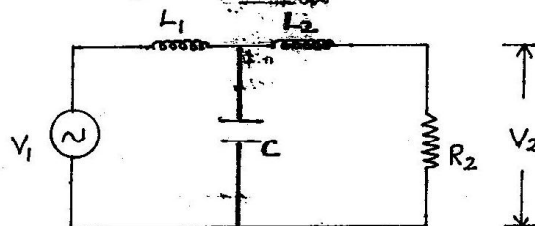- (ii) Obtain the voltage transfer function $\frac{V_2}{V_1}$ for the coupled circuit shown in fig. (8)




Or

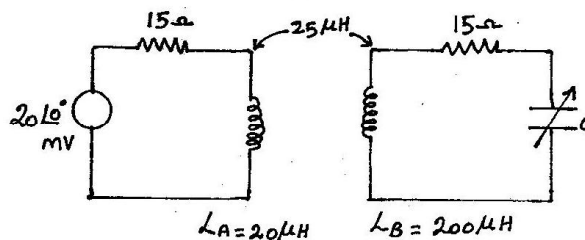- (b) (i) In the coupled circuit shown in fig., the input to the primary is 20 mV at $f = 1$ MHz and secondary is tuned to this frequency. Determine (1) the value of C (2) input impedance (3) secondary current and (4) the voltage across the capacitor. (8)




- (ii) Obtain the resonant frequency, Q factor bandwidth and the voltage across the capacitor at resonance for the circuit series RLC having $R = 7.5 \Omega$, $L = 6 \mu\text{H}$ and $C = 40 \text{ pF}$ with a supply voltage of 0.5 V. (8)

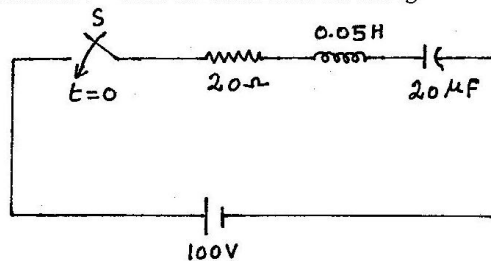14. (a) (i) Obtain an expression for the transient current when the switch S is closed at $t = 0$ for the circuit shown in Fig. (8)




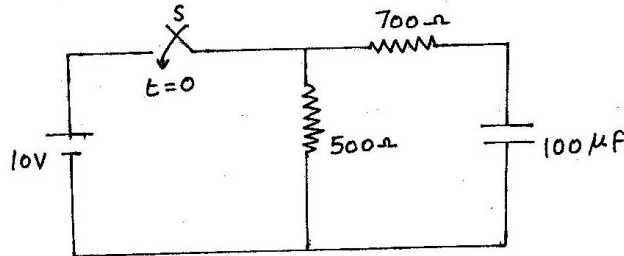- (ii) In the circuit shown in Fig, how long does it take after the switch S is closed before the total current from the supply reaches 30 mA. (8)




Or

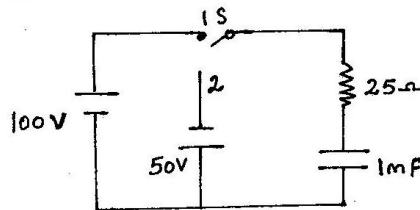- (b) (i) In the circuit shown in Fig., the switch is put in position 1 for 1 ms and then thrown to position 2. Find the transient current in both intervals. (8)



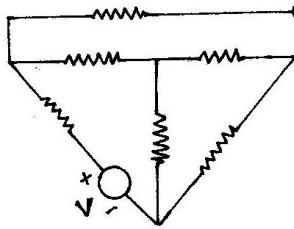
- (ii) Obtain the transient voltage across the elements R and C in a series RC circuit excited by a d.c. voltage when the switch is closed at $t = 0$. (8)
15. (a) (i) For the network shown in Fig., obtain the tie-set matrix and hence write down the equilibrium equations. Also give the expression for branch current in terms of link currents. (8)



- (ii) Explain the procedure to form a cut-set matrix. (8)

Or

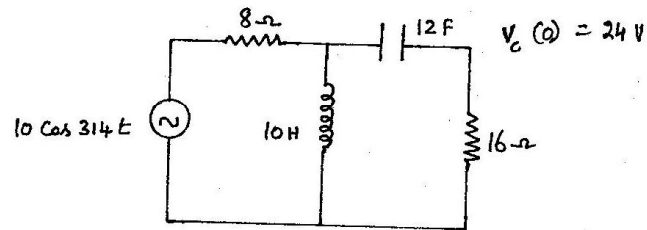- (b) (i) For the circuit shown in Fig., write the mesh equations. Obtain the duals of the mesh equations and hence derive the dual network from the dual equations derived. (8)



- (ii) State the properties of
- (1) Tree of a graph
 - (2) Path of a graph. (8)