

Questions Q1. to Q20. carry one mark each.

Q1. If $\mathbf{A} = \begin{bmatrix} 0 & 1 & -2 \\ -1 & 0 & 3 \\ 2 & -2 & \lambda \end{bmatrix}$ is a singular matrix, then λ is

- (A) 0 (B) -2
(C) 2 (D) -1

Q2. Let $f(x) = e^x$ in $[0, 1]$. Then, the value of c of the mean-value theorem is

- (A) 0.5 (B) $(e - 1)$
(C) $\log(e - 1)$ (D) None

Q3. If $\mathbf{D} = xy\mathbf{u}_x + yz\mathbf{u}_y + zx\mathbf{u}_z$, then the value of $\oiint \mathbf{A} \cdot d\mathbf{S}$ is, where S is the surface of the cube defined by $0 \leq x \leq 1, 0 \leq y \leq 1, 0 \leq z \leq 1$

- (A) 0.5 (B) 3
(C) 0 (D) 1.5

Q4. The gradient of field $f = y^2x + xyz$ is

- (A) $y(y + z)\mathbf{u}_x + x(2y + z)\mathbf{u}_y + xy\mathbf{u}_z$
(B) $y(2x + z)\mathbf{u}_x + x(x + z)\mathbf{u}_y + xy\mathbf{u}_z$
(C) $y^2\mathbf{u}_x + 2yx\mathbf{u}_y + xy\mathbf{u}_z$
(D) $y(2y + z)\mathbf{u}_x + x(2y + z)\mathbf{u}_y + xy\mathbf{u}_z$

Q5. In the circuit of fig. Q5 the value of R_1 will be

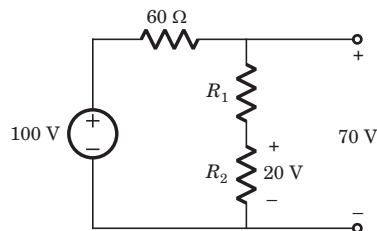


Fig Q5

- (A) 25 Ω (B) 50 Ω
(C) 100 Ω (D) 2000 Ω

GATE ECE By R. K. Kanodia

MCQs : The book contains only solved Multiple choice questions (MCQ) which is the main requirement of the GATE exam. Each and every problem has its complete solution. **We understand the fact that theoretical studies should be done from the standard book, that one has studied for the semester exams and thus one should use the same material to understand the concepts of the same.** We have deliberately excluded theoretical matter in the book so as not to mislead the students. However, wherever needed, satisfactory explanation of the formula has been included in the solution.

Q6. The voltage v_o in fig. Q6 is always equal to

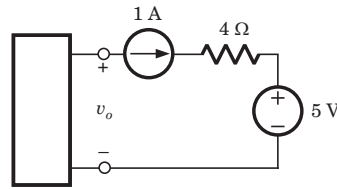


Fig Q6

- (A) 1 V (B) 5 V
(C) 9 V (D) None of the above

Q7. Epitaxial growth is used in integrated circuit

- (A) because it produces low parasitic capacitance
(B) because it yields back-to-back isolating junctions
(C) to grow single crystal n -doped silicon on a single-crystal p -type substrate
(D) to grow selectively single-crystal p -doped silicon of one resistivity on p -type substrate of a different resistivity.

Q8. The chemical reaction involved in epitaxial growth in IC chips takes place at a temperature of about

- (A) 500°C (B) 800°C
(C) 1200°C (D) 2000°C

Q9. In the circuit of fig. Q9 the output voltage v_o is

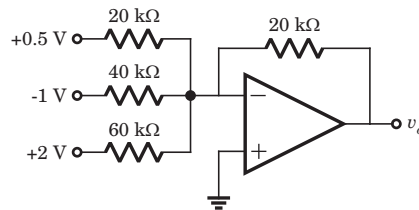


Fig Q9

- (A) 2.67 V (B) -2.67 V
(C) -6.67 V (D) 6.67 V

Q10. **Assertion (A)** In the self bias CE transistor amplifier a single battery is used.
Reason (R) The collector base junction is forward biased by V_{CC} .

Chose the correct option:

- (A) Both A and R individually true and R is the correct explanation of A.
(B) Both A and R individually true and but R is not the correct explanation of A.
(C) A is true but R is false
(D) A is false

- Q11.** The address bus width of a memory of size 1024×8 bits is
- (A) 10 bits (B) 13 bits
(C) 8 bits (D) 18 bits
- Q12.** Consider the TTL circuit in fig Q12. The value of V_H and V_L are respectively

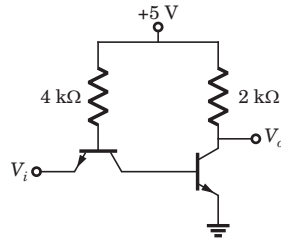


Fig Q12

- (A) 5 V, 0 V (B) 4.8 V, 0 V
(C) 4.8 V, 0.2 V (D) 5 V, 0.2 V
- Q13.** Consider a discrete-time system S whose response to a complex exponential input $e^{j\pi n/2}$ is specified as $S : e^{j\pi n/2} \Rightarrow e^{j\pi 3n/2}$. The system is
- (A) definitely LTI (B) definitely not LTI
(C) may be LTI (D) information is not sufficient.
- Q14.** The DTFT of signal $2\delta[4-2n]$ is
- (A) $2e^{-j2\Omega}$ (B) $2e^{j2\Omega}$
(C) 1 (D) None of the above
- Q15.** Consider the List I and List II

List I

List II

- P. Derivative control
Q. Integral control
R. Rate feed back control
S. Proportional control

1. Improved overshoot response
2. Less steady state errors
3. Less stable
4. More damping

The correct match is

- | | P | Q | R | S |
|-----|---|---|---|---|
| (A) | 1 | 2 | 3 | 4 |
| (B) | 4 | 3 | 1 | 2 |
| (C) | 2 | 3 | 1 | 4 |
| (D) | 1 | 2 | 4 | 3 |

Q16. The pole-zero plot given in fig.Q16 is that of a

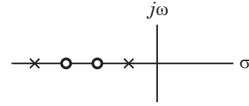


Fig Q16

- (A) PID controller
(B) PD controller
(C) Integrator
(D) Lag-lead compensating network

Q17. In TDM non essential frequency components of the modulating signal are removed by

- (A) sampler
(B) attenuator
(C) pre-alias filter
(C) modulator

Q18. Coherent demodulation of FSK signal can be affected using

- (A) correlation receiver
(B) bandpass filter and envelope detectors
(C) discriminator detection
(C) above all

Q19. Two dissimilar antennas having their maximum directivities equal,

- (A) must have their beamwidths also equal.
(B) can not have their beamwidths equal because they are dissimilar antenna.
(C) may not necessarily have their maximum power gain equal.
(D) must have their effective aperture areas (capture areas) also equal.

Q20. The dominant mode in a rectangular waveguide is TE_{10} because this mode has

- (A) no attenuation
(B) no cut-off
(C) no magnetic field component
(D) the highest cut-off wavelength

Problem

Solution

10. $v_1 = ?$

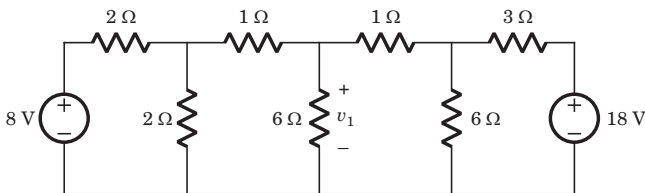


Fig. P.1.4.10

- (A) 6 V
(B) 7 V
(C) 8 V
(D) 10 V

10. (A) By changing the LHS and RHS in Thevenin equivalent

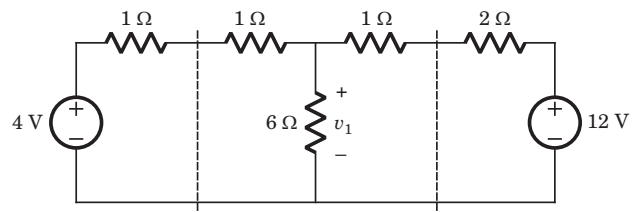


Fig. S1.4.10

$$v_1 = \frac{\frac{4}{1+1} + \frac{12}{1+2}}{\frac{1}{1+1} + \frac{1}{6} + \frac{1}{1+2}} = 6 \text{ V}$$

Consider above problem and its solution from book **GATE ECE** by **R. K. Kanodia** (chapter 1.4 Circuit Theorems). If problem is solved using mesh analysis or nodal gives 4 or 3 variables. The solution shown above has only one variable and require less calculation reducing time and errors as well. The trick in this book are not new but it equip students to think differently.

Questions Q21. to Q75. carry two marks each.

Q21. If the rank of the matrix, $\mathbf{A} = \begin{bmatrix} 2 & -1 & 3 \\ 4 & 7 & \lambda \\ 1 & 4 & 5 \end{bmatrix}$ is 2, then the value of λ is

- (A) -13 (B) 13
(C) 3 (D) None of these

Q22. If $u = e^{xyz}$, then $\frac{\partial^3 u}{\partial x \partial y \partial z}$ is equal to

- (A) $e^{xyz} [1 + xyz + 3x^2 y^2 z^2]$
(B) $e^{xyz} [1 + xyz + x^3 y^3 z^3]$
(C) $e^{xyz} [1 + 3xyz + x^2 y^2 z^2]$
(D) $e^{xyz} [1 + 3xyz + x^3 y^3 z^3]$

Q23. The value of $\int e^x \left(\frac{1 + \sin x}{1 + \cos x} \right) dx$ is

- (A) $e^x \tan \frac{x}{2} + c$ (B) $e^x \cot \frac{x}{2} + c$
(C) $e^x \tan x + c$ (D) $e^x \cot x + c$

Q24. The solution of the differential equation $(x - y^2)dx + 2xydy = 0$ is

- (A) $ye^{2/x} = A$ (B) $xe^{y^2/x} = A$
(C) $xe^{x/y^2} = A$ (D) $ye^{x/y^2} = A$

Q25. The Taylor's series expansion of $f(z) = \sin z$ about $z = \frac{\pi}{4}$ is

- (A) $\frac{1}{\sqrt{2}} \left[1 + \left(z - \frac{\pi}{4} \right) - \frac{1}{2!} \left(z - \frac{\pi}{4} \right)^2 - \dots \right]$
(B) $\frac{1}{\sqrt{2}} \left[1 + \left(z - \frac{\pi}{4} \right) + \frac{1}{2!} \left(z - \frac{\pi}{4} \right)^2 + \dots \right]$
(C) $\frac{1}{\sqrt{2}} \left[1 - \left(z - \frac{\pi}{4} \right) - \frac{1}{2!} \left(z - \frac{\pi}{4} \right)^2 - \dots \right]$
(D) None of the above

Q26. Consider the following table

Diameter of heart (in mm)	Number of persons
120	5
121	9
122	14
123	8
124	5
125	9

The median of the above frequency distribution is

- (A) 122 mm (B) 123 mm
(C) 122.5 mm (D) 122.75 mm

Q27. For $\frac{dy}{dx} = x + y^2$, given that $y = 0$ at $x = 0$, using Picard's method up to third order of approximation the solution of the differential equation is

- (A) $\frac{x^2}{2} + \frac{x^5}{40} + \frac{x^8}{480} + \frac{x^{11}}{1600}$
(B) $\frac{x^2}{2} + \frac{x^5}{20} + \frac{x^8}{160} + \frac{x^{11}}{4400}$
(C) $\frac{x^2}{2} + \frac{x^5}{20} + \frac{x^8}{160} + \frac{x^{11}}{2400}$
(D) $\frac{x^2}{2} + \frac{x^5}{40} + \frac{x^8}{480} + \frac{x^{11}}{2400}$

Q28. The bilateral laplace transform of $\cos 3t u(-t) * e^{-t} u(t)$ is

- (A) $\frac{-s}{(s+1)(s^2+9)}$, $\operatorname{Re}(s) > 0$
(B) $\frac{-s}{(s+1)(s^2+9)}$, $-1 < \operatorname{Re}(s) < 0$
(C) $\frac{s}{(s+1)(s^2+9)}$, $-1 < \operatorname{Re}(s) < 0$
(D) $\frac{s}{(s+1)(s^2+9)}$, $\operatorname{Re}(s) > 0$

Q29. The z -transform of $x[n] = \left(\frac{2}{3}\right)^{|n|}$ is

(A) $\frac{-5z}{(2z-3)(3z-2)}, -\frac{3}{2} < z < -\frac{2}{3}$

(B) $\frac{-5z}{(2z-3)(3z-2)}, \frac{2}{3} < |z| < \frac{3}{2}$

(C) $\frac{5z}{(2z-3)(3z-2)}, \frac{2}{3} < |z| < \frac{2}{3}$

(D) $\frac{5z}{(2z-3)(3z-2)}, -\frac{3}{2} < z < -\frac{2}{3}$

Q30. Consider the graph shown in fig. Q30 in which twigs are solid line and links are dotted line.


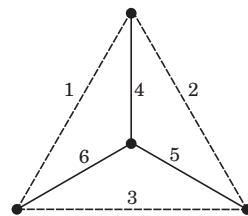


Fig Q30


A fundamental loop matrix for this tree is given as below

$$\mathbf{B}_F = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & -1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix}$$


The oriented graph will be

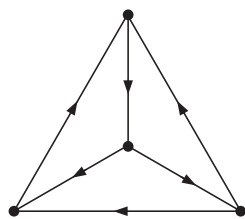


(A)

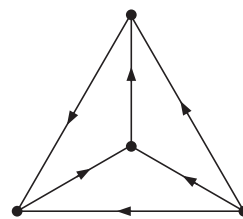

(B)

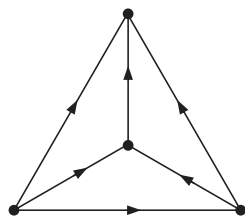

(C)

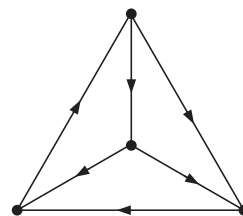

(D)

Q34. In the circuit of fig. Q34 the $i(t)$ will be

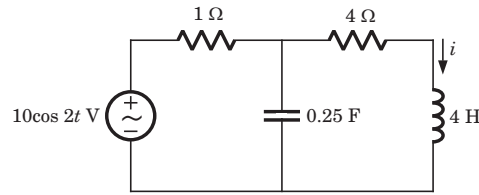


Fig Q34

- (A) $2\sin(2t + 5.77^\circ)$ A (B) $\cos(2t - 84.23^\circ)$ A
 (C) $2\sin(2t - 5.77^\circ)$ A (D) $\cos(2t + 84.23^\circ)$ A

Q35. In the circuit of fig. Q35 L_{eq} will be

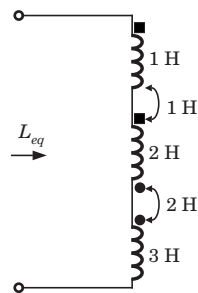


Fig Q35

- (A) 1 H (B) 2 H
 (C) 3 H (D) 4 H

Q36. The maximum voltage across capacitor would be

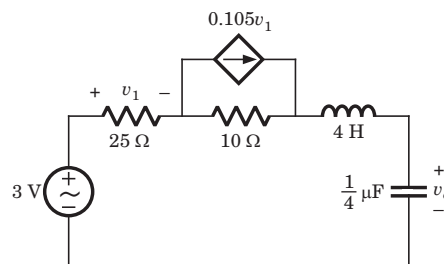


Fig Q36

- (A) 3200 V (B) 3 V
 (C) -3 V (D) 1600 V

- Q37.** Three scattering mechanism exist in a semiconductor. If only the first mechanism were present, the mobility would be $500 \text{ cm}^2/\text{V} - \text{s}$. If only the second mechanism were present, the mobility would be $750 \text{ cm}^2/\text{V} - \text{s}$. If only third mechanism were present, the mobility would be $1500 \text{ cm}^2/\text{V} - \text{s}$. The net mobility is
- (A) $2750 \text{ cm}^2/\text{V} - \text{s}$
- (B) $1114 \text{ cm}^2/\text{V} - \text{s}$
- (C) $818 \text{ cm}^2/\text{V} - \text{s}$
- (D) $250 \text{ cm}^2/\text{V} - \text{s}$
- Q38.** In a silicon ($n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, $D_n = 35 \text{ cm}^2/\text{s}$) sample the electron concentration drops linearly from 10^{18} cm^{-3} to 10^{16} cm^{-3} over a length of $2.0 \text{ } \mu\text{m}$. The current density due to the electron diffusion current is
- (A) $93 \times 10^4 \text{ A}/\text{cm}^2$
- (B) $2.8 \times 10^4 \text{ A}/\text{cm}^2$
- (C) $93 \times 10^9 \text{ A}/\text{cm}^2$
- (D) $2.8 \times 10^9 \text{ A}/\text{cm}^2$
- Q39.** A *pn* junction diode is operating in reverse bias region. The applied reverse voltage, at which the ideal reverse current reaches 90% of its reverse saturation current, is
- (A) -59.6 mV
- (B) 2.7 mV
- (C) 4.8 mV
- (D) 42.3 mV
- Q40.** In bipolar transistor biased in the forward-active region the base current is $I_B = 50 \text{ } \mu\text{A}$ and the collector current is $I_C = 2.7 \text{ mA}$. The α is
- (A) 0.949
- (B) 54
- (C) 0.982
- (D) 0.018

Q41. An n -channel silicon ($n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$) JFET at $T = 300 \text{ K}$ has doping concentration of $N_d = 8 \times 10^{16} \text{ cm}^{-3}$ and $N_a = 3 \times 10^{18} \text{ cm}^{-3}$. The channel thickness dimensions is $a = 0.5 \mu\text{m}$. If the undepleted channel has to be $0.2 \mu\text{m}$, the required gate voltage is

- (A) 2.73 V
- (B) -2.73 V
- (C) 4.66 V
- (D) -4.66 V

Q42. In the circuit shown in fig. Q42 voltage $V_E = 4 \text{ V}$. The value of α and β are respectively

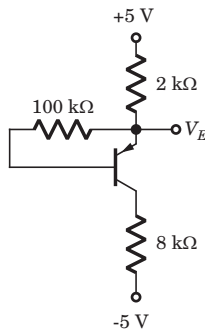


Fig Q42

- (A) 0.943, 17.54
- (B) 0.914, 17.54
- (C) 0.914, 10.63
- (D) 0.914, 11.63

Q43. In the current mirror circuit of fig. Q43 the transistor parameters are $V_{BE} = 0.7 \text{ V}$, $\beta = 50$ and the Early voltage is infinite. Assume transistor are matched. The output current I_o is

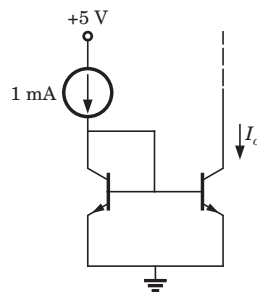


Fig Q43

- (A) 1.04 mA
- (B) 1.68 mA
- (C) 962 μA
- (D) 432 μA

- Q44.** The parameter of the transistor in fig. Q44 are $V_{TN} = 1.2 \text{ mA} / \text{V}^2$, $K_n = 0.5 \text{ mA} / \text{V}^2$, and $\lambda = 0$. The voltage V_{DS} is

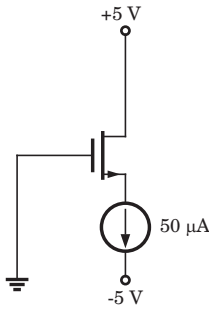


Fig Q44

- (A) 2.83 V (B) 6.52 V
(C) 3.48 V (D) 4.98 V
- Q45.** In the circuit shown in fig. Q45 the op-amp is ideal. If transistor has $\beta = 60$, then the total current supplied by the 15 V source is

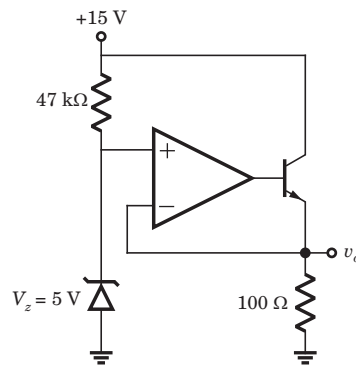


Fig Q45

- (A) 123.1 mA (B) 98.3 mA
(C) 49.4 mA (D) 168 mA
- Q46.** Consider the statements below:
1. If the output waveform from an OR gate is the same as the waveform at one of its inputs, the other input is being held permanently LOW.
 2. If the output waveform from an OR gate is always HIGH, one of its input is being held permanently HIGH.

The statement, which is always true, is

- (A) Both 1 and 2 (B) Only 1
(C) Only 2 (D) None of the above

Q47. A logic circuit consist of two 2×4 decoder as shown in fig. Q47.

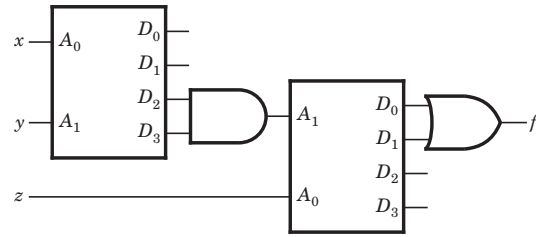


Fig Q47

The output of decoder are as follow

$$D_0 = 1 \text{ when } A_0 = 0, \quad A_1 = 0$$

$$D_1 = 1 \text{ when } A_0 = 1, \quad A_1 = 0$$

$$D_2 = 1 \text{ when } A_0 = 0, \quad A_1 = 1$$

$$D_3 = 1 \text{ when } A_0 = 1, \quad A_1 = 1$$

The value of $f(x, y, z)$ is

- (A) 0 (B) z
 (C) \bar{z} (D) 1

Q48. The circuit shown in fig. Q48 implements the function

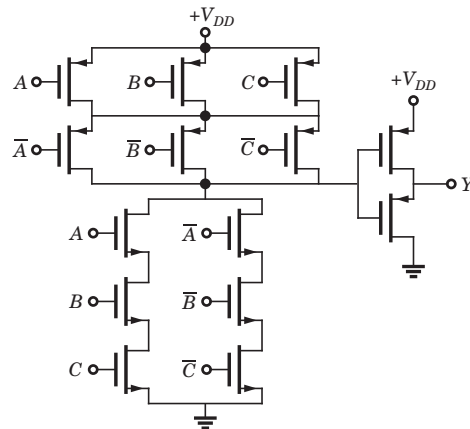


Fig Q48

- (A) $ABC + \overline{ABC}$ (B) $ABC + \overline{(A + B + C)}$
 (C) $\overline{ABC} + \overline{(A + B + C)}$ (D) None of the above

Q49. Consider the following 8085 assembly program

```

                MVI        A, DATA1
                MOV        B, A
                SUI        51H
                JC         DLT
                MOV        A, B
                SUI        82H
                JC         DSPLY
DLT :           XRA        A
                OUT PORT1
                HLT
DSPLY :        MOV        A, B
                OUT PORT2
                HLT

```

This program will display

- (A) the bytes from 51H to 82H at PORT2
- (B) 00H AT PORT1
- (C) all byte at PORT1
- (D) the bytes from 52H to 81H at PORT 2

Q50. Consider the following program

```

                MVI        A, BYTE1
                RRC
                RRC

```

If BYTE1 = 32H, the contents of A after the execution of program will be

- (A) 08H
- (B) 8CH
- (C) 12H
- (D) None of the above

Q51. The response of a system S to a complex input $x(t) = e^{j5t}$ is specified as $y(t) = te^{j5t}$. The system

- (A) is definitely LTI
- (B) is definitely not LTI
- (C) may be LTI
- (D) information is insufficient

Q52. The following input output pairs have been observed during the operation of a time invariant system :

$$\begin{array}{ccc} x_1[n] = \{1, 0, 2\} & \xleftrightarrow{s} & y_1[n] = \{0, 1, 2\} \\ \uparrow & & \uparrow \\ x_2[n] = \{0, 0, 3\} & \xleftrightarrow{s} & y_2[n] = \{0, 1, 0, 2\} \\ \uparrow & & \uparrow \\ x_3[n] = \{0, 0, 0, 1\} & \xleftrightarrow{s} & y_3[n] = \{1, 2, 1\} \\ \uparrow & & \uparrow \end{array}$$

The conclusion regarding the linearity of the system is

- (A) System is linear
- (B) System is not linear
- (C) One more observation is required.
- (D) Conclusion cannot be drawn from observation.

Q53. The transfer function $H(s)$ of a stable system is

$$H(s) = \frac{s^2 + 5s - 9}{(s+1)(s^2 - 2s + 10)}$$

The impulse response is

- (A) $-e^{-t}u(t) + (e^t \sin 3t + 2e^t \cos 3t)u(t)$
- (B) $-e^{-t}u(t) - (e^t \sin 3t + 2e^t \cos 3t)u(-t)$
- (C) $-e^{-t}u(t) - (e^t \sin 3t + 2e^t \cos 3t)u(t)$
- (D) $-e^{-t}u(t) + (e^t \sin 3t + 2e^t \cos 3t)u(-t)$

Q54. The frequency response which has nonlinear phase is

- (A) $\frac{1}{j\omega + 1}$
- (B) $\frac{1}{(j\omega + 1)^2}$
- (C) $\frac{1}{(j\omega + 1)(j\omega + 2)}$
- (D) All above

GATE ECE By R. K. Kanodia

Aim : The aim of the book is to provide quality material, a fact which can easily be seen in books available for the preparation of IIT-JEE, AIEEE, CPMT & CAT, but till date never observed in the material available GATE preparation. In other words, we want to provide ELITE material but which is also economical.

E : Expressive
L : Less Erroneous
I : Individualistic
T : Targeted approach
E : Exhaustive content

Q55. Consider a discrete-time periodic signal

$$x[n] = \frac{\sin\left(\frac{11\pi}{20}n\right)}{\sin\left(\frac{\pi}{20}n\right)}$$

with a fundamental period $N = 20$. The Fourier series coefficients of this function are


(A) $\frac{1}{20}(u[k + 5] - u[k - 6]), |k| \leq 10$

(B) $\frac{1}{20}(u[k + 5] - u[k - 5]), |k| \leq 10$

(C) $(u[k + 5] - u[k + 6]), |k| \leq 10$

(D) $(u[k + 5] - u[k - 6]), |k| \leq 10$

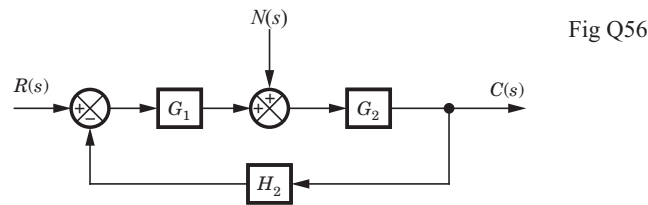Q56. A feedback control system shown in fig. Q56 is subjected to noise $N(s)$.



The noise transfer function $\frac{C_N(s)}{N(s)}$ is


(A) $\frac{G_1 G_2}{1 + G_1 G_2 H}$

(B) $\frac{G_2}{1 + G_1 H}$

(C) $\frac{G_2}{1 + G_2 H}$

(D) None of the above

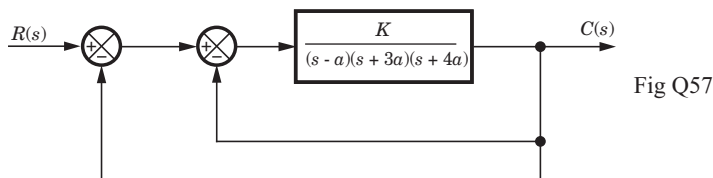Q57. For the block diagram shown in the fig. Q57 the limiting value of K for stability of inner loop is found to be $X < K < Y$. The over all system will be stable if and only if



(A) $4X < K < 4Y$

(B) $\frac{X}{2} < K < \frac{Y}{2}$

(C) $2X < K < 2Y$

(D) $X < K < Y$


Q58. The transfer function of a *ufb* system is

$$G(s) = \frac{10^5 (s+3)(s+10)(s+20)}{s(s+25)(s+a)(s+30)}$$


The value of a to yield velocity error constant $K_v = 10^4$ is

- (A) 4 (B) 0
(C) 8 (D) 16

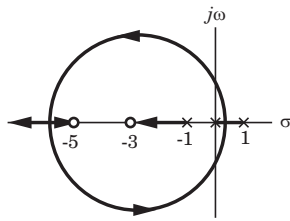
Q59. The forward-path transfer function of a *ufb* system is $G(s) = \frac{K(s+\alpha)(s+3)}{s(s^2-1)}$. The root-loci for $K > 0$ with $\alpha = 5$ is




(A)

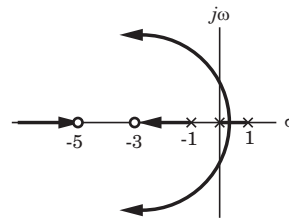

(B)

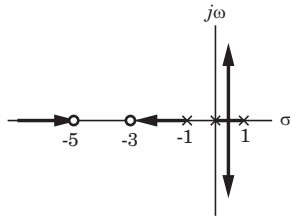

(C)

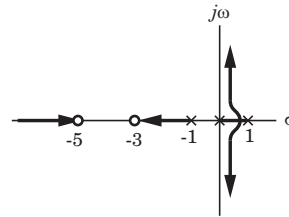

(D)

Q60. Consider the asymptotic Bode plot of a minimum phase linear system given in fig. Q60.

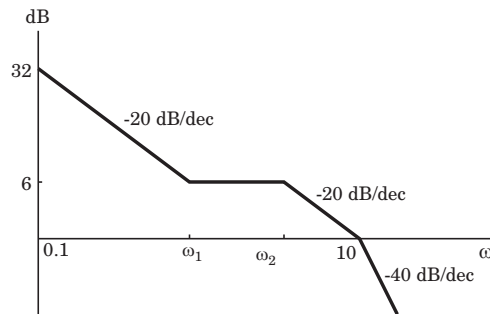


Fig Q60

The transfer function is

- (A) $\frac{8s(s+2)}{(s+5)(s+10)}$ (B) $\frac{4(s+5)}{(s+2)(s+10)}$
(C) $\frac{4(s+2)}{s(s+5)(s+10)}$ (D) $\frac{8s(s+5)}{(s+2)(s+10)}$

Q61. The joint PDF of random variable x and y is shown in fig. Q61. The value of A is

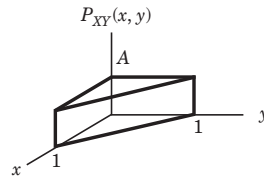


Fig Q61

- (A) 1 (B) 2
(C) 4 (D) None of the above

Q62. The probability density function of a random variable X is given as $f_X(x)$. A random variable Y is defined as $y = ax + b$ where $a < 0$. The PDF of random variable Y is

- (A) $bf_X\left(\frac{y-b}{a}\right)$ (B) $af_X\left(\frac{y-b}{a}\right)$
(C) $\frac{1}{a}f_X\left(\frac{y-b}{a}\right)$ (D) $\frac{1}{b}f_X\left(\frac{y-b}{a}\right)$

Q63. A carrier is amplitude modulate to 100 % by a polar rectangular signal as shown in fig. Q62. The percentage increase in signal power is

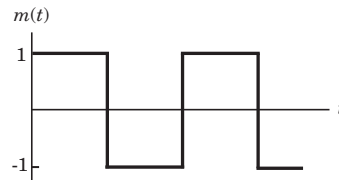



Fig Q62

- (A) 83.3 % (B) 100 %
(C) 50 % (D) None of the above

Q64. In a AM signal the received signal power is 10^{-10} W with a maximum modulating signal of 5 kHz. The noise spectral density at the receiver input is 10^{-18} W/Hz. If the noise power is restricted to the message signal bandwidth only, the signals-to-noise ratio at the input to the receiver is

- (A) 43 dB (B) 66 dB
(C) 56 dB (D) 33 dB

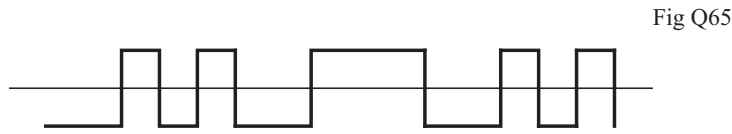Q65. Fig. Q65 shows a PCM signals in which amplitude level of +1 volt and -1 volt are used to represent binary symbol 1 and 0 respectively. The code word used consists of three bits.



The sampled version of analog signal from which this PCM signal is derived is

- (A) 4 5 2 1 3 (B) 8 4 3 1 2
 (C) 6 4 3 1 7 (D) 1 2 3 4 5


Q66. The flux of $\mathbf{D} = \rho^2 \cos^2 \phi \mathbf{u}_\rho + 3 \sin \phi \mathbf{u}_\phi$ over the closed surface of the cylinder $0 \leq z < 3$, $\rho = 3$ is

- (A) 324 (B) 81π
 (C) 81 (D) 64π

Q67. In a certain region $\mathbf{J} = (4y\mathbf{u}_x + 2xz\mathbf{u}_y + z^3\mathbf{u}_z) \sin(10^4 t)$ A/m. If volume charge density ρ_v in $z = 0$ plane is zero, then ρ_v is

- (A) $3z^2 \cos(10^4 t) \text{mC/m}^3$
 (B) $0.3z^2 \cos(10^4 t) \text{mC/m}^3$
 (C) $-3z^2 \cos(10^4 t) \text{mC/m}^3$
 (D) $-0.3z^2 \cos(10^4 t) \text{mC/m}^3$

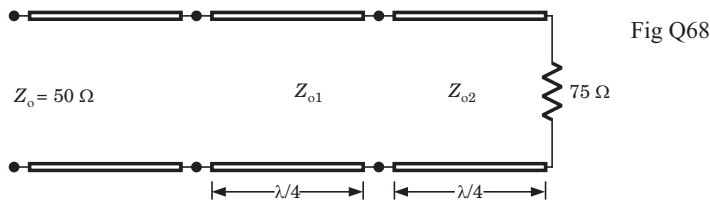Q68. Two $\lambda/4$ transformer in tandem are to connect a 50Ω line to a 75Ω load as shown in fig. Q68. If $Z_{o2} = 30 \Omega$ and there is no reflected wave to the left of A, then the characteristic impedance Z_{o1} is



- (A) 28Ω (B) 56Ω
 (C) 49Ω (D) 24.5Ω

- Q69.** The cross section of a waveguide is shown in fig. Q69. It has dielectric discontinuity as shown in fig. If the guide operate at 8 GHz in the dominant mode, the standing wave ratio is

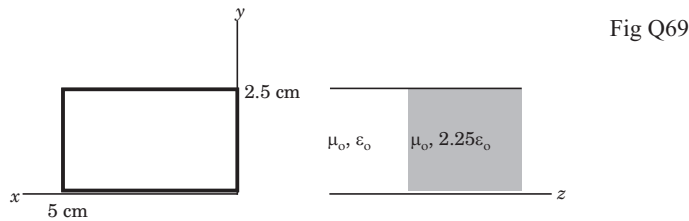


Fig Q69

- (A) -3.911
(B) 2.468
(C) 1.564
(D) 4.389
- Q70.** An antenna consists of 4 identical Hertzian dipoles uniformly located along the z -axis and polarized in the z -direction. The spacing between the dipole is $\frac{\lambda}{4}$. The group pattern function is

- (A) $4 \cos\left(\frac{\pi}{4} \cos \theta\right) \cos\left(\frac{\pi}{2} \cos \theta\right)$
(B) $4 \cos\left(\frac{\pi}{4} \cos \theta\right) \cos\left(\frac{\pi}{8} \cos \theta\right)$
(C) $4 \cos\left(\frac{\pi}{4} \cos \theta\right) \sin\left(\frac{\pi}{2} \cos \theta\right)$
(D) $4 \cos\left(\frac{\pi}{4} \cos \theta\right) \sin\left(\frac{\pi}{8} \cos \theta\right)$

Common Data Questions

Common Data for Questions Q71-73:

In the voltage regulator circuit in fig. Q71-73 the Zener diode current is to be limited to the range $5 \leq i_z \leq 100$ mA.

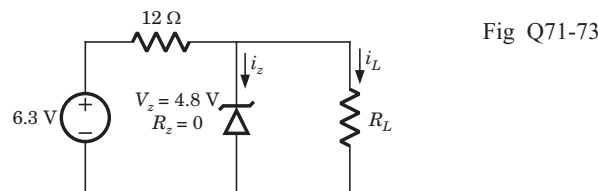


Fig Q71-73

- Q71.** The range of possible load current is
- (A) $5 \leq i_L \leq 130$ mA
(B) $25 \leq i_L \leq 120$ mA
(C) $10 \leq i_L \leq 110$ mA
(D) None of the above
- Q72.** The range of possible load resistance is
- (A) $60 \leq R_L \leq 372 \Omega$
(B) $60 \leq R_L \leq 200 \Omega$
(C) $40 \leq R_L \leq 192 \Omega$
(D) $40 \leq R_L \leq 360 \Omega$
- Q73.** The power rating required for the load resistor is
- (A) 576 mW
(B) 360 μ W
(C) 480 mW
(D) 75 μ W

Common Data for Questions Q74-75:

The state-space representation of a system is given by $\dot{\mathbf{x}}(t) = \mathbf{A} \cdot \mathbf{x}(t) + \mathbf{B} \cdot \mathbf{u}(t)$, where

$$\mathbf{A} = \begin{bmatrix} 0 & 2 \\ -2 & 0 \end{bmatrix}, \mathbf{B} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

If $\mathbf{x}(0)$ is the initial state vector, and the component of the input vector $\mathbf{u}(t)$ are all unit step function, then the state transition equation is given by $\mathbf{x}(t) = \Phi(t)\mathbf{x}(0) + \theta(t)$, where $\Phi(t)$ is a state transition matrix and $\theta(t)$ is a vector matrix.

Q74. The $\Phi(t)$ is

(A) $\begin{bmatrix} \cos 2t & \sin 2t \\ -\sin 2t & \cos 2t \end{bmatrix}$

(B) $\begin{bmatrix} \cos 2t & -\sin 2t \\ \sin 2t & \cos 2t \end{bmatrix}$

(C) $\begin{bmatrix} \sin 2t & \cos 2t \\ -\cos 2t & \sin 2t \end{bmatrix}$

(D) $\begin{bmatrix} \sin 2t & -\cos 2t \\ \cos 2t & \sin 2t \end{bmatrix}$

Q75. The $\theta(t)$ is

(A) $\begin{bmatrix} 0.5(1 - \sin 2t) \\ 0.5 \cos 2t \end{bmatrix}$

(B) $\begin{bmatrix} \sin 2t \\ \cos 2t \end{bmatrix}$

(C) $\begin{bmatrix} 0.5(1 - \cos 2t) \\ 0.5 \sin 2t \end{bmatrix}$

(D) $\begin{bmatrix} \cos 2t \\ \sin 2t \end{bmatrix}$

Linked Answer Questions: Q76. to Q85. carry two marks each.

Statement for Linked Answer Questions: Q76. and Q77:

A silicon Hall device at $T = 300 \text{ K}$ has the geometry $d = 10^{-3} \text{ cm}$, $W = 10^{-2} \text{ cm}$, $L = 10^{-1} \text{ cm}$. The following parameters are measured: $I_x = 0.75 \text{ mA}$, $V_x = 15 \text{ V}$, $V_H = +5.8 \text{ mV}$, $B_z = 0.1 \text{ tesla}$.

Q76. The majority carrier concentration is

(A) $8 \times 10^{15} \text{ cm}^{-3}$, n -type

(B) $8 \times 10^{15} \text{ cm}^{-3}$, p -type

(C) $4 \times 10^{15} \text{ cm}^{-3}$, n -type

(D) $4 \times 10^{15} \text{ cm}^{-3}$, p -type

Q77. The majority carrier mobility is

(A) $430 \text{ cm}^2/\text{V} \cdot \text{s}$

(B) $215 \text{ cm}^2/\text{V} \cdot \text{s}$

(C) $390 \text{ cm}^2/\text{V} \cdot \text{s}$

(D) $195 \text{ cm}^2/\text{V} \cdot \text{s}$

Statement for Linked Answer Questions: Q82 and Q83:

In a certain frequency-modulation experiment conducted with $f_m = 1$ kHz and increasing amplitude (starting from 0 V), it is found that the carrier component of the FM signal is reduced to zero for the first time when $A_m = 2$ V. Given that Bessel function $J_0(x)$ is zero for $x = 2.44, 5.52, 8.65, 11.8$ and so on.

Q82. The frequency sensitivity of the modulator is

- (A) 1.38 kHz/V (B) 0.61 kHz/V
(C) 2.76 kHz/V (D) 1.22 kHz/V

Q83. The carrier components is reduced to zero for the second time for the value of A_m

- (A) 4.52 V (B) 3.38 V
(C) 2.68 V (D) 1.39 V

Statement for Linked Answer Questions: Q84 and Q85:

The amplitude of a wave traveling through a lossy nonmagnetic medium reduces by 18% every meter. The wave operates at 10 MHz and the electric field leads the magnetic field by 24° .

Q84. The propagation constant is

- (A) $0.198 + j0.448$ per meter
(B) $0.346 + j0.713$ per meter
(C) $0.448 + j0.198$ per meter
(D) $0.713 + j0.346$ per meter

Q85. The skin depth is

- (A) 2.52 m (B) 5.05 m
(C) 8.46 m (D) 4.23 m

Multiple Choice Questions
GATE
Electronics & Communications
By
R. K. Kanodia

Answers Paper-1

1. (B)	2. (C)	3. (D)	4. (A)	5. (C)
6. (D)	7. (C)	8. (C)	9. (B)	10. (A)
11. (A)	12. (D)	13. (B)	14. (A)	15. (D)
16. (D)	17. (C)	18. (A)	19. (C)	20. (D)
21. (B)	22. (C)	23. (A)	24. (B)	25. (A)
26. (A)	27. (B)	28. (B)	29. (B)	30. (D)
31. (C)	32. (B)	33. (C)	34. (B)	35. (D)
36. (A)	37. (D)	38. (B)	39. (A)	40. (C)
41. (D)	42. (C)	43. (C)	44. (B)	45. (C)
46. (D)	47. (D)	48. (B)	49. (A)	50. (B)
51. (B)	52. (B)	53. (D)	54. (D)	55. (A)
56. (A)	57. (B)	58. (A)	59. (A)	60. (C)
61. (B)	62. (C)	63. (B)	64. (A)	65. (D)
66. (B)	67. (B)	68. (D)	69. (C)	70. (A)
71. (B)	72. (C)	73. (A)	74. (A)	75. (C)
76. (B)	77. (C)	78. (C)	79. (D)	80. (D)
81. (B)	82. (D)	83. (A)	84. (A)	85. (B)

Vision of NODIA & COMPANY

1. **Highly Competitive:** To be able to provide, the student, with the best quality material for the targeted exam and the best production quality books. The books published by us would be accurate and precise in content, well-targeted in approach, expressive in style and available at an affordable price. We take pride in stating that our first publication **GATE-ECE by RK Kanodia** has been a great success last year, on all aspects. Everyone who got through, due to this book, has given excellent feedback. Reviews can be read at our website www.nodia.co.in.

2. **Avoid Student exploitation:** We are aware that setting a high MRP, giving discounts to students & incentives to retailers, to sell a book is unethical and in a way exploits students as far as money is concerned. We respect the publishing field & do not want to employ gimmicks to increase our sales. The true appreciation of our work lies if the student can be pickup our book for its quality not because the retailer is promoting it in lieu of incentive.

3. **Social Responsibility:** To help improve the socio-economic conditions of the grass-root level with the earning from this endeavor. Rs.10, from every book sold, is contributed to the NGOs/Govt. Organizations working for the education of child labour.

MCQ GATE-ECE by RK Kanodia

Kindly note that our publication **GATE-ECE by RK Kanodia**, has the following features that make it an excellent study material in comparison to other books available on the GATE exam:

1. **MCQs:** The book contains only solved Multiple choice questions (MCQ) which is the main requirement of the GATE exam. Each and every problem has its complete solution. **We understand that theoretical studies should be done from the standard book, that one has studied for the semester exams and thus one should use the same material to understand the concepts of the same.** We have deliberately excluded theoretical matter in the guide book so as not to mislead the students. However, wherever needed, satisfactory explanation of the formula has been included in the solution.
2. **Adherence to Pattern:** All Multiple choice questions are strictly according to the GATE pattern. Every problem selected and included in the book is a model problem for the preparation of the exam which would thus prepare and equip the students better. Kindly note, that the standard of **Multiple choice questions and their solution in every unit is much better than the ones available in a famous series of problems & solutions as far as GATE is concerned.**
3. **Levels of MCQs:** The Multiple choice questions included in this book are in a conceptually evolving method, allowing the student to progress from one level of complexity to another but always aiding in understanding the basic foundation of the subject. Thus, the MCQs gradually and scientifically advance from the basic level to a more complex level, helping in the systematic understanding of the problem rather than an abrupt one.
4. **Unit Division:** Each unit has been further sub-divided into separate chapters and not clustered together. Thus the non-combination of all the problems in a single unit makes the reader, to remain focused and able to manage his time during his preparation.
5. **Time Management:** Time is a very important factor in any competitive exam and the same applies for GATE too. It has been observed and concluded that if students can manage time, they can get a better score in GATE. **The solutions provided are extremely logical yet tricky** so that they save time when the student solve them in the examination, as they have already been used to solving difficult and tricky problems.
6. **Variety:** The book carries in it a large variety of problems. The words of one of the senior educators of a reputed coaching institute bear testimony to the fact wherein he comments that **“We can’t expect so much variety of problems in a single book available in the market.”**
7. **Includes Previous Exam Questions:** This **book contains questions on earlier IES, IAS & GATE exams that might be relevant to learn some concepts** but we have purposely not mentioned them in our book. We believe and strongly advocate that every year GATE contains new and unique problems.
8. **Less Erroneous:** The book has very few errors [less than 5%] compared to the other books available in the market which have upto 40% errors. This puts the students in a better and more comfortable situation as all the **errors are traceable due to availability of the complete solution** and moreover, the errors are never conceptual but data or typo mistakes. Kindly note that, all the errata will be soon available at our website www.nodia.co.in
9. **Attractive Format:** We understand student psychology and the fact that if the book is in an attractive format, the student would feel good in reading the book. This fact also heightens the interest to study in a student. Thus **the style of the book is so designed that it appeals to its readers**, yet is expressive and detailed.
10. **Aim :** The aim of the book is to provide quality material, a fact which can easily be seen in books available for the preparation of IIT-JEE, AIEEE, CPMT & CAT, but till date never observed in the material available GATE preparation. In other words, we want to provide ELITE material but which is also economical.

E : Expressive
L : Less Erroneous
I : Individualistic
T : Targeted approach
E : Exhaustive content

We have received feedback, which state that the book fulfills more than what is stated above and thus it has been a great success last year, on all aspects. Everyone who got through, due to this book, has given excellent feedback. Reviews can be read at our website www.nodia.co.in.

However, nothing in the world can be achieved without the help of constructive criticism and thus we would be obliged if you can send across your feedback to make our book, a **GUIDE** in true sense of the word.

Feel free to mail or call at following for any enquiry about book:

NODIA & COMPANY

09350292376

pk.goel@nodia.co.in

Dear Student,

We are a Delhi based publishing organization by the name of **NODIA & COMPANY**, conceptualized in June 2005, for providing competitive exam books in the field of Engineering.

The company has been started with following **AIM**:

- 1. Highly Competitive:** To be able to provide, the student, with the best quality material for the targeted exam and the best production quality books. The books published by us would be accurate and precise in content, well-targeted in approach, expressive in style and available at an affordable price. We take pride in stating that our first publication **GATE-ECE by RK Kanodia** has been a great success last year, on all aspects. Everyone who got through, due to this book, has given excellent feedback. Reviews can be read at our website www.nodia.co.in.
- 2. Avoid Student exploitation:** We are aware that setting a high MRP, giving high discounts to students & incentives to retailers, to sell a book is unethical and in a way exploits students as far as money is concerned. We respect the publishing field & do not want to employ gimmicks to increase our sales. The true appreciation of our work lies if the student can be pickup our book for its quality not because the retailer is promoting it in lieu of incentive.
- 3. Social Responsibility:** To help improve the socio-economic conditions of the grass-root level with the earning from this endeavor. Rs.10, from every book sold, is contributed to the NGOs/Govt. Organizations working for the education of child labour.

A Concern:

Regret to infer that, survival has been difficult keeping in mind the ethics. Publishers, who claim to be the partners in the progress of students, use cheap tactics to sell their material to them. A publisher, famous for providing books on GATE, which are incidentally also erroneous & copied, has also imitated our book this year. They have gone to the extent this year and introduced a revised edition of their book on GATE on Elect. & Comm., which also includes new large number of Multiple Choice Questions [MCQ]. All the MCQ's & their solutions have been copied from our book [GATE by RK Kanodia]. This is condemnable act of plagiarism. They are trying to restrict our book from reaching the students, by giving high incentives to retailers & distributors. They are using all possible unfair means of the publishing field, to make money and monetary exploit students, yet the book fails to reach the students.

An Appeal:

We would like to make this Appeal to you against plagiarism and exploitation, keeping in mind the interest of students & publishing field, to support us in our fight.

Our company has been started with very few resources and but have large vision. The greatest challenge for us is to reach every part of India. We realize that educators are busy people in times of change and thus they are not able to rate the books given to them, to be able to suggest the same to the students. Thus students, who are dependent on such educators for the knowledge of books, are not able to use the resources available to the maximum. The restriction of erroneous and plagiarized work, in reaching the hands of students thus becomes a huge task.

Therefore, we request and ask for your support against this condemnable act of plagiarism.

NODIA & COMPANY