

**DiplETE – ET (OLD SCHEME)**

Code: DE22  
Time: 3 Hours

Subject: INDUSTRIAL ELECTRONICS  
Max. Marks: 100

**DECEMBER 2009**

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or best alternative in the following: (2 × 10)**

a. Latching current

- (A) more than holding current
- (B) is same as holding current
- (C) less than holding current
- (D) None

b. Which of the following is not used for turning on thyristor:

- (A)  $dv/dt$  triggering
- (B)  $di/dt$  triggering
- (C) Gate triggering
- (D) light triggering

c. Which of the following is true for full wave controlled rectifier (single phase)

- (A) Two thyristors and two diodes
- (B) Two thyristors
- (C) Two thyristors and one diode
- (D) None

d. In parallel inverter

- (A) Capacitor C is not connected
- (B) Capacitor C and load are in series
- (C) Capacitor C and load are in parallel
- (D) Capacitor C and load are effectively in parallel

e. Choppers are used as

- (A) ac-dc converter
- (B) dc-ac converter
- (C) dc-dc converter
- (D) None

f. In controlled heating circuits thyristors act as

- (A) Chopper
- (B) Cyclo converter
- (C) AC regulator
- (D) None of above

- g. Jones chopper uses
- (A) Line commutation                      (B) Auxilliary commutation  
(C) Load commutation                  (D) None
- h. Three phase bridge inverter requires
- (A) Three thyristors and three diodes  
(B) Six thyristors and six diodes  
(C) Twelve thyristors and twelve diodes  
(D) None of above
- i. The operating frequency in dielectric heating is
- (A) 100 kHz to 0.5 MHz                  (B) 0.5 MHz to 1 MHz  
(C) 10 kHz to 100 kHz                  (D) 1 MHz to 40 MHz
- j. Auxilliary commutated chopper circuit has
- (A) 1 thyristor                              (B) 2 thyristors  
(C) 4 thyristors                              (D) None of above

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

- Q.2** a. Define any four voltage and current ratings of a thyristor. **(8)**
- b. A dc supply of 100 V feeds an inductance of 10 H through a thyristor. Find the minimum width of the gate pulse so that the thyristor is triggered. The latching current of thyristor is 80 mA. **(8)**
- Q.3** a. Draw the UJT relaxation oscillator triggering circuit for SCR and explain its operation. **(8)**
- b. A single phase half wave rectifier circuit using a thyristor is fed by a transformer whose secondary voltage is  $400 \sin \omega t$ . Find the average load voltage, rms load voltage, average load current and rms load current, if the thyristor is fired at  $30^\circ$  in each positive half cycle. The load resistance is  $50 \Omega$ . **(8)**
- Q.4** a. Draw the circuit diagram of single phase half wave converter with R load and without freewheeling diode and explain its operation. **(8)**
- b. Draw the circuit diagram of a single phase half bridge inverter and explain its operation. **(8)**
- Q.5** a. Explain the circuit of parallel inverter and also draw the waveforms of load voltage and load current. **(8)**
- b. A dc chopper has input voltage of 200 V and output voltage of 150 V. Load resistance is  $100 \Omega$ . Find (a) duty cycle (b) average and rms load currents (c) rms thyristor currents (d) average input current (e) effective input resistance. **(8)**

- Q.6** a. Explain the principle of operation of chopper. **(8)**
- b. Discuss the operation of an auxiliary commuted chopper. Draw the circuits showing the different modes of operation. **(8)**
- Q.7** a. What is Jones chopper? Describe its operation. **(8)**
- b. Describe series operation of SCRs. **(8)**
- Q.8** a. Describe the principle of operation of dielectric heating. **(8)**
- b. An insulating slab has  $100 \text{ cm}^2$  area and is 5 cm thick. It is to be heated by 300 W power at 10 MHz frequency. If relative permittivity is 4.5 and power factor is 0.05. Find applied voltage and current. **(8)**
- Q.9** a. Compare induction heating and dielectric heating and also give a few uses of each. **(8)**
- b. Describe the inverter configurations used for induction heating. **(8)**