

Code: AC03/AT
Time: 3 Hours

DECEMBER 2008

Subject: BASIC ELECTRONICS &
DIGITAL CIRCUITS


Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following: (2x10)

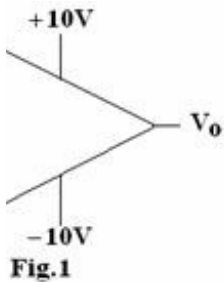- a. The mobility of electrons in an N-type semiconductor is $100 \times 10^{-4} \text{ m}^2/\text{volt} - \text{sec}$. If the resistivity of the semiconductor is $20 \times 10^{-2} \text{ ohm} - \text{m}$, then the number of electron carriers per m^3 will be,
- (A) $3.1 \times 10^{21}/\text{m}^3$. (B) $2.29 \times 10^{21}/\text{m}^3$.
(C) $1.82 \times 10^{21}/\text{m}^3$. (D) $3.82 \times 10^{21}/\text{m}^3$.



- b. The output of comparactor is
- (A) -2 V
(B) -5 V
(C) +10 V
(D) -10 V
- c. Which of the following h-parameters of a transistor has the greatest value
- (A) h_i (B) h_r
(C) h_f (D) h_o
- d. If the value of β for the two transistors used in a Darlington amplifier are 150 and 100 respectively, then the overall current gain of the amplifier is
- (A) 14000. (B) 12000.
(C) 15000. (D) 1000.
- e. The parameters of a JFET used in a common source amplifier are : $g_m = 2.5 \text{ mA/V}$ and $r_d = 500 \text{ K}\Omega$. If the value of the load in the drain circuit is $10 \text{ K}\Omega$, then the voltage gain for the amplifier is

- (A) -14.5.
(C) -100.

- (B) 52.5.
(D) -24.5.

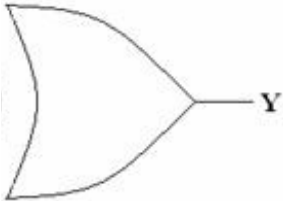


Fig.2

f. The output Y of Logic circuit is

- (A) 0
(B) 1
(C) \bar{A}
(D) $\bar{\bar{A}}$

g. The complement of the Boolean expression $\bar{A}B + C\bar{D}$ is

- (A) $A+BC$ (B) $B + \bar{A}$
(C) $(A + \bar{B})(\bar{C} + D)$ (D) 1

h. When $(1010)_2$ is subtracted from $(1000)_2$ using 2's complement method, the result is

- (A) $(1110)_2$. (B) $(0100)_2$.
(C) $(0010)_2$. (D) $(0111)_2$.

i. The fastest Logic family is

- (A) TTL (B) CMOS
(C) ECL (D) HTL

j. How many address bits are needed to operate a $2K \times 8$ - bit ROM memory?

- (A) 8 (B) 15
(C) 32 (D) 11

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. What is a semiconductor? How does a semiconductor behave at absolute zero temperature? Name four semiconductor materials. (6)
- b. Design a 4-bit serial-in parallel out Left shift Register. (5)

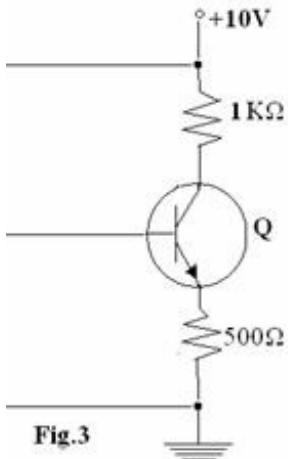


Fig.3

the value of the collector
collector-to-emitter voltage
age divider of biasing
sistor shown in Fig.3.

Take $v_{BE} = 0.7V$ and $\beta = 100$ for
the transistor used.

(5)

- Q.3** a. Describe the advantages of h-parameters? Draw Low frequency small signal hybrid-model for a common emitter transistor and determine Voltage gain (A_V), Current gain (A_I), Input Impedance (Z_i) and Output Impedance (Z_o).
(12)

- b. For the amplifier circuit shown in Fig.4, write the h-parameter equivalent circuit and find the current gain for the amplifier. The transistor h-parameters are: $h_i = 22\Omega, h_f = -0.98, h_r = 0.49\mu A/V, h_o = 2.9 \times 10^{-4}$

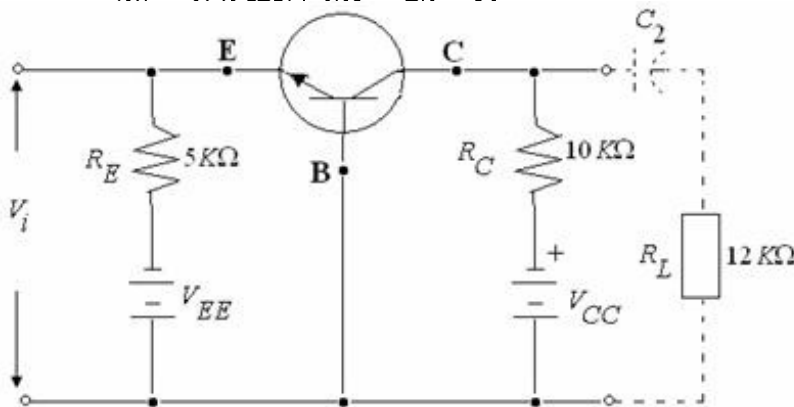



Fig.4

- Q.4** a. Draw the a.c. equivalent circuit of a JFET common-drain amplifier and derive the voltage gain of the amplifier.
(8)

- b. Draw the circuit diagram of RC phase oscillator and derive the condition for oscillation. Neglect the effects of h_{re} and h_{oe} . (8)

- Q.5** a. Draw the circuit of basic Integrator and differentiator using an op-Amp and explain its operation. (6)

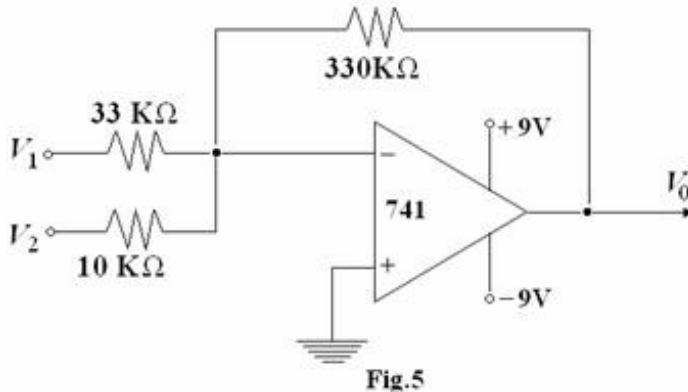- b. Calculate the output voltage for the circuit given in Fig.5. The input voltages are $V_1 = 50\sin(1000t)\text{mV}$ and $V_2 = 10\sin(3000t)\text{mV}$. (5)



- c. What do you mean by a Regulated Power Supply? What are the important elements of a regulated Power supply? Define the term Voltage Regulation. (5)

- Q.6** a. Prove the following: $(A + B)(\overline{A\overline{C}} + C)(\overline{B + AC}) = \overline{AB}$. (5)

- b. Minimize the Boolean expression given using K-map method.
 $f(A, B, C, D) = \prod(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$ (6)

- c. Write the truth table and logic diagram of 1:8 demultiplexer; using NAND gates only. (5)

- Q.7** a. What is a Schottky diode? Comment on the storage time of Schottky diodes. (6)

- b. Explain NMOS logic circuit? Draw the circuit of an NMOS inverter that uses an n-channel enhancement-type MOSFET as a load resistor and briefly explain its operation. (10)

- Q.8** a. What is ECL? Mention its characteristics. (8)

- b. Write a note on programmable logic arrays. (8)

- Q.9** a. Draw a static CMOS memory cell and explain its read and write operations. (6)

- b. What do you mean by 'STATE' of a counter? Draw the schematic of a four-bit synchronous binary UP-Counter using T flip-flops (positive edge triggered) and briefly explain it. (10)

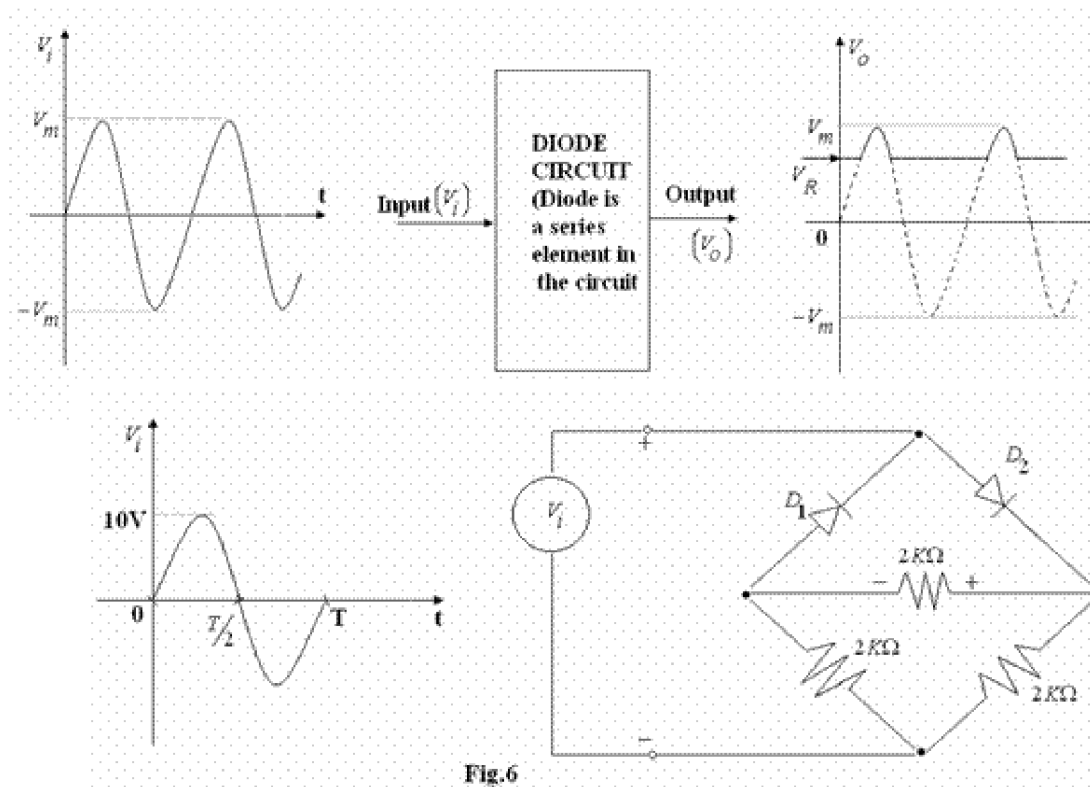


Fig.6

