

Code: AC-03 / AT-03

Subject: BASIC ELECTRONICS &amp; DIGITAL CIRCUITS

JUNE 2007

Time: 3 Hours


Max. Marks: 100

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or best alternative in the following: (2x10)**

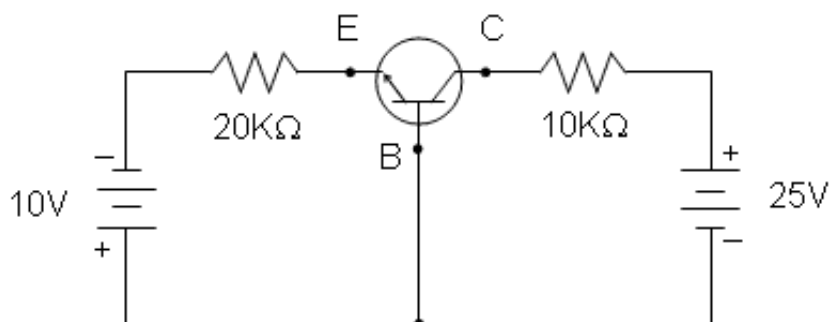- a. If the resistivity of a sample of N-type semiconductor with a Hall coefficient of  $160 \text{ cm}^3/\text{coulomb}$  is  $0.16 \text{ ohm-cm}$ , then the mobility of the electron in the sample is
- (A)  $950 \text{ cm}^2/\text{volt-sec}$  (B)  $1000 \text{ cm}^2/\text{volt-sec}$   
 (C)  $570 \text{ cm}^2/\text{volt-sec}$  (D)  $462 \text{ cm}^2/\text{volt-sec}$
- b. Allow  $0.7 \text{ V}$  for the  $V_{BE}$  drop in the circuit given. The dc collector-base voltage will be



- (A)  $16 \text{ V}$   
 (B)  $10 \text{ V}$   
 (C)  $20 \text{ V}$   
 (D)  $25 \text{ V}$
- c. The h-parameters are called hybrid parameters because they
- (A) are different from impedance and admittance parameters  
 (B) apply to circuits contained in a box  
 (C) are defined by using both short circuit and open circuit terminations  
 (D) are mixed with other parameters
- d. The voltage gain of a Darlington amplifier is
- (A) equal to unity


- (B) less than unity  
(C) greater than unity  
(D) equal to zero
- e. The N-channel MOSFET devices are preferred more than P-channel ones because
- (A) N-channel devices are faster than P-channel devices  
(B) N-channel devices have higher packing density than P-channel devices  
(C) N-channel devices consume less power than P-channel devices  
(D) Both (A) and (B) above,
- f. If the parameters of a crystal are:  $L=0.33H$ ,  $C_1=0.065 \text{ pF}$ ,  $C_2=1\text{pF}$  and  $R=5.5K\Omega$ , with usual notations, then the series resonant frequency is
- (A) 2.12 MHz (B) 1.09 MHz  
(C) 1.8 MHz (D) 2.5 MHz
- g. A three-variable Boolean expression in m-notation is  $f(xyz) = \Sigma m(0,4,7)$ . Its algebraic form is
- (A)  $\overline{x}yz + \overline{x}yz + xyz$  (B)  $\overline{x}yz + \overline{x}yz + xyz$   
(C)  $\overline{x}yz + \overline{x}yz + xyz$  (D)  $\overline{x}yz + \overline{x}yz + \overline{x}yz$
- h. When  $(1010)_2$  is subtracted from  $(1111)_2$  using 2's complement method, the result is
- (A)  $(0101)_2$  (B)  $(1011)_2$   
(C)  $(1101)_2$  (D)  $(0011)_2$
- i. The propagation delay time of a typical ECL gate is
- (A) 5 ns (B) 8 ns  
(C) 1 ns (D) 6.2 ns
- j. In a ROM how many words are addressed using 18 address bits?
- (A) 200 K (B) 2 K  
(C) 256 K (D) 138 K

**Answer any FIVE Questions out of EIGHT Questions.**

**Each question carries 16 marks.**

- Q.2** a. Define a semiconductor in terms of energy bands and comment in brief on free charge carriers in semiconductors. (8)
- b. A 4.7 V zener diode has a resistance of  $15\Omega$ . What is the terminal voltage when the current is 20 mA? (3)

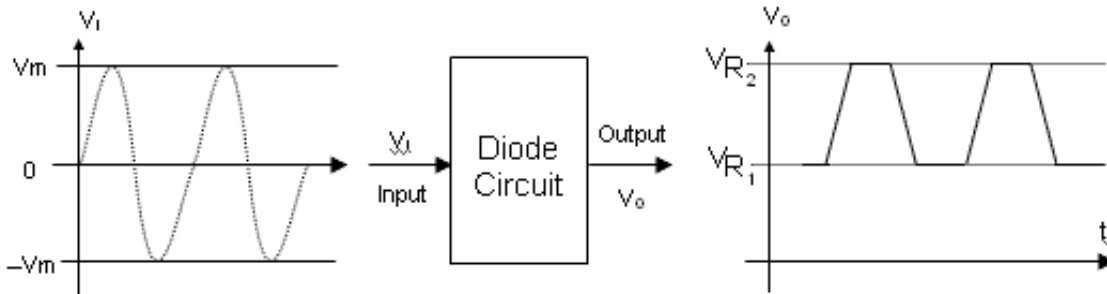
- c. A sinusoidal signal of peak voltage  $V_m$  is applied to a diode circuit to generate the waveform shown. Draw the diode circuit and briefly explain its operation.



Assume that the Peak of the input voltage is greater than  $V_{R_2}$ . (5)

- Q.3** a. Draw the hybrid model for a transistor and write the equations for the input voltage and output current for the above model. Define the hybrid parameters involved. (7)

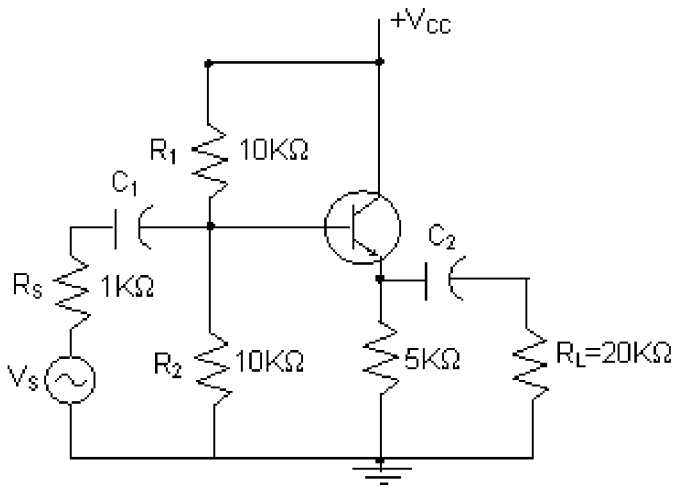- b. For the amplifier circuit shown below, calculate  $R_i$ ,  $A_i$ ,  $A_v$ .



The h-parameters for the transistor are:  $h_{ic}=1.2K\Omega$ ,  $h_{fc}=101$ ,  $h_{rc}=1$ ,  $h_{oc}=25A/V$ . (9)


- Q.4** a. FET amplifiers have become more popular than BJT amplifiers. Give reasons. Draw the circuit of a common-source amplifier using N-channel enhancement FET and draw its a.c. equivalent circuit. Deduce the equation for its voltage gain. (13)

- b. Write the basic configuration for any resonant circuit oscillator that uses an OP AMP and give its linear equivalent circuit. (3)



- Q.5** a. Illustrate neatly the basic operational amplifier in terms of its circuit symbol and draw its low-frequency equivalent circuit. What do you mean by single-ended amplifier?  $-V_{CC}$  (5)

- b. With neat sketches for illustration, explain the operation of the circuit shown below, by taking the voltage  $V_{in}$  as a sinusoidal signal and  $V_{Ref}$  equal to zero.

(6)

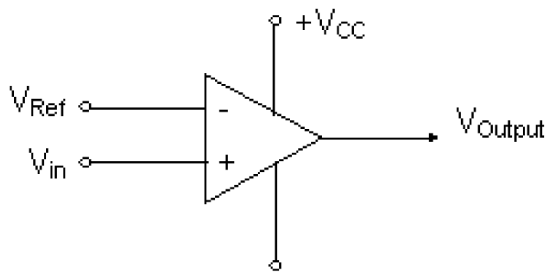

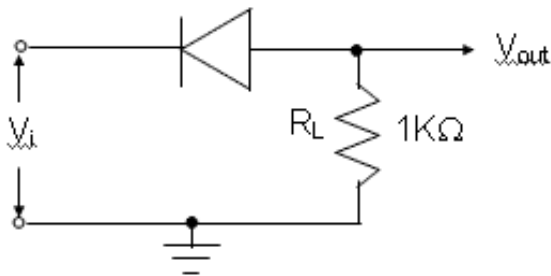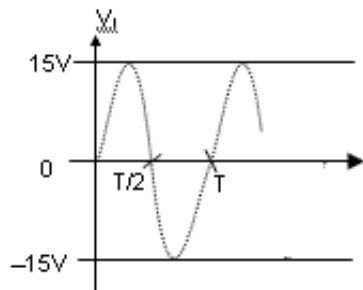- c. (i) Assuming the diode in the circuit shown to be an ideal one, calculate the dc output for the network shown below for the input voltage indicated.



- (ii) Repeat the above calculation by replacing the diode with a silicon diode of cut-in voltage 0.7 V. Take the forward resistance of the diode as zero.

(5)

**Q.6** a. Prove the following property of Boolean algebra

$$A + BC = (A + B)(A + C) \quad (4)$$

- b. Simplify the Boolean function given using Karnaugh Map method

$$f(ABCD) = Y = \sum m(3,4,5,7,9,13,14,15) \quad (7)$$

- c. Write the truth table and logic diagram of a one-to-four demultiplexer using inverters and AND gates only.

(5)

**Q.7** a. Write a note on FET switches. (7)

- b. When do you use NMOS logic circuits? Write a brief note on CMOS logic. Write the circuit of a two-input CMOS NAND gate. (9)

**Q.8** a. Briefly explain the following TTL parameters:

- (i) Fan-out (5)

(ii) Noise immunity

b. What is a RAM? Write the block schematic of a RAM and briefly explain. (11)

**Q.9** a. What is a Flip-Flop? Which are the different types commonly used? Explain how an S-R Flip-Flop can be constructed using two NOR gates and comment on its truth table. (8)

b. What is the primary function of a counter? Write the schematic of a four-bit binary UP-counter using positive edge triggered T flip-flops, and briefly explain. (8)