

1. (a) A typical PCB substrate consists of  $\text{Al}_2\text{O}_3$  with a relative dielectric constant of 10 and a loss tangent of 0.0004 at 10 GHz. Find the conductivity of substrate. 5
- (b) Starting with basic definition for the Standing Wave Ratio (SWR) :— 5

$$\text{SWR} = \frac{|V_{\max}|}{|V_{\min}|} = \frac{|I_{\max}|}{|I_{\min}|}$$

Show that it can be re-expressed as,

$$\text{SWR} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$$

- (c) For GaAs we find at  $T = 300 \text{ }^\circ\text{K}$  the effective densities of state  $N_C = 4.7 \times 10^{17} \text{ cm}^{-3}$ ,  $N_V = 7.0 \times 10^{18} \text{ cm}^{-3}$ . Assuming that the band gap energy of 1.42 eV remains constant, 5
- (i) Find the intrinsic carrier concentration at room temperature.
- (ii) Compute  $n_i$  at  $T = 400 \text{ }^\circ\text{K}$ .
- (d) Explain simplified Ebers-Moll model for forward active mode of transistor. 5
2. (a) A  $100 \text{ } \Omega$  microstrip line is connected to a  $75 \text{ } \Omega$  line. Determine  $\Gamma$ , SWR, percentage power reflected, return loss, percentage power transmitted and insertion loss. 10
- (b) Derive expressions for internal, external and loaded quality factors for the standard series and parallel resonance circuit. 10
3. (a) An abrupt pn-junction made of Si has the acceptor and donor concentrations of  $N_A = 10^{18} \text{ cm}^{-3}$  and  $N_D = 5 \times 10^{15} \text{ cm}^{-3}$ , respectively. Assuming that the device is at room temperature. Determine — 10
- (i) barrier voltage
- (ii) the space charge width in the p and n type semiconductors.
- (b) An unknown load impedance is connected to a  $0.3 \lambda$  long,  $50 \text{ } \Omega$  lossless transmission line. The SWR and phase of the reflection coefficient measured at the input of line are 2.0 and  $-20^\circ$ , respectively. Using the Smith chart, determine the input and load impedances. 10
4. (a) An  $N = 3$  Chebyshev bandpass filter is to be designed with a 3 dB passband ripple for a communication link. The centre frequency is at 2.4 GHz and the filter has to meet a bandwidth requirement of 20 %. The filter has to be inserted into a  $50 \text{ } \Omega$  characteristic line impedance. Find inductive and capacitive elements. Show the attenuation response from 1 to 4 GHz. 12
- (b) Explain Schottky diode with cross sectional view and circuit model. 8

5. (a) Obtain the h-parameter representation for a BJT in common base configuration, neglecting base, emitter and collector resistances ( $r_B$ ,  $r_E$  and  $r_C$ ). 10  
 (b) Explain construction and functionality of High Electron Mobility Transistor. 10
6. (a) Prove the first three Kuroda's identities by computing the appropriate ABCD matrices. 10  
 (b) A radio transmitter is capable of producing 3 W output power. The transmitter is connected to an antenna having characteristic impedance of  $75 \Omega$ . The connection is made using lossless co-axial cable with a  $50 \Omega$  characteristic impedance. Calculate the power delivered to antenna if the source impedance is  $45 \Omega$  and cable length is  $11 \lambda$ . 10
7. Write short notes on :—
- (a) RF behaviour of resistor 5  
 (b) Micro strip Transmission Lines 5  
 (c) Butterworth filter 5  
 (d) Measurements of AC parameters of BJT. 5

Table Chebyshev filter coefficients; 3 dB filter design ( $N = 1$  to 10)

$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095