


(REVISED COURSE)

(3 Hours)

[Total Marks : 100

- N.B.** (1) Question No. 1 is **compulsory**.
 (2) Answer any **four** out of remaining **six** questions.
 (3) Assume any **suitable** data wherever **required** but justify the **same**.
 (4) **Figures** to the **right** indicate marks.

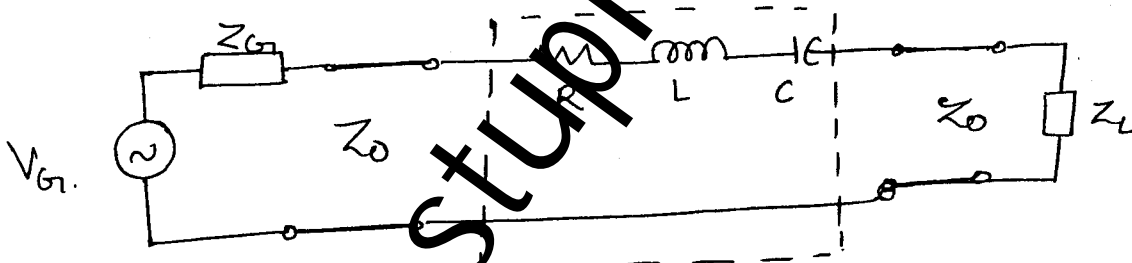1. (a) The leads of a resistor in an RF circuit are treated as straight aluminium wires ($\sigma_{Al} = 4.0 \times 10^7 \text{ s/m}$) of AWG size 14 cd = 64 mil) and of total length of 5 cm. 6
 (i) Compute the DC resistance
 (ii) Find the AC resistance and inductance at 100 MHz, 1 GHz, and 10 GHz operating frequencies.
 (b) A load impedance of $40 + j 70$ ohms terminates a 100 ohms transmission line i.e. 0.3λ long. Find the reflection coefficient of the load, the reflection coefficient at the input to the line, the input impedance, the SWR in the line and the return loss. 6
 (c) For the filter configuration shown in the **figure** below, the following parameters are given : 4
 $Z_0 = 50 \text{ ohms}$, $Z_G = Z_L = Z_0$, $R = 10 \text{ ohms}$, $L = 50 \text{ nH}$, $C = 0.47 \text{ pF}$, and the generator voltage is $V_G = 5 \text{ V}$. Find the external, internal and loaded quality factor.



- (d) Explain the design procedure of small signal BJT amplifier. (DC circuit design and RF circuit design). 4
2. (a) A particular RF circuit requires that a line impedance of 50 ohms is to be maintained. A selected PCB board with dielectric constant of 4.6 and thickness of 40 mil. Find phase velocity and wavelength at 2 GHz. 10
 (b) Consider the case of matching a 73Ω load to a 50 ohm line by means of a $\lambda/4$ transformer. Assume the matching is achieved for a center frequency of $f_c = 2 \text{ GHz}$. Plot the SWR for the frequency range $1/3 \leq f/f_c \leq 3$. 10
3. (a) Design a prototype low-pass Butterworth filter that will provide atleast 20 dB attenuation at the frequency of $f = 2 f_{3dB}$. Compute and plot the amplitude response for 0 to 5 GHz. 10
 (b) Plot the insertion loss of a low pass Chebyshev filter that has 6 dB ripple in the passband and at least 50 dB attenuation at $f = 2 f_{\text{cut-off}}$. 10


4. (a) A two-port transistorized Network has the following scattering matrix : 10

$$[s] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

Determine whether the transistorized Network is Reciprocal and lossless. If port 2 is terminated with a matched load, what is the return loss seen at port 1 ? If port 2 is terminated with a short circuit, what is the return loss seen at port 1 ?


- (b) A BJT is encapsulated in a plastic housing and mounted on a heat sink 10
 $(R_{thha} = 3.75 \text{ }^\circ\text{C/w})$ under these conditions the total power dissipation is supposed to be 20 w. at an ambient temperature of $20 \text{ }^\circ\text{C}$. What rating has the engineer to choose for the BJT casing if the maximum junction temperature should not exceed $175 \text{ }^\circ\text{C}$.

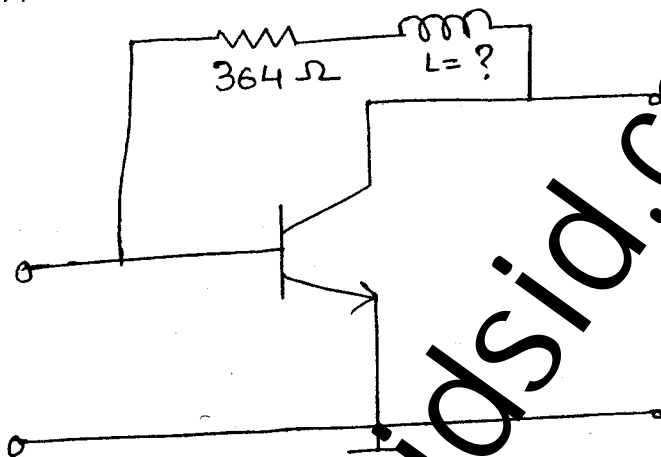5. (a) For small signal BJT amplifier shown, find the value of inductor that would provide negative feedback above $f = 600 \text{ MHz}$. Assume that the phase of S_{21} approaches 90° around 600 MHz . 8



- (b) An abrupt pn-junction made of Si has the acceptor and donor concentrations 12
of $N_A = 10^{18} \text{ cm}^{-3}$ and $N_D = 5 \times 10^{15} \text{ cm}^{-3}$, respectively. Assuming that the device operates at room temperature, determine :
- The barrier voltage
 - The space charge width in the p and n type semiconductors.
 - The peak electric field across the junction.
 - The junction capacitance for a cross sectional area of 10^{-4} cm^2 and a relative dielectric constant of $\epsilon_r = 11.7$.

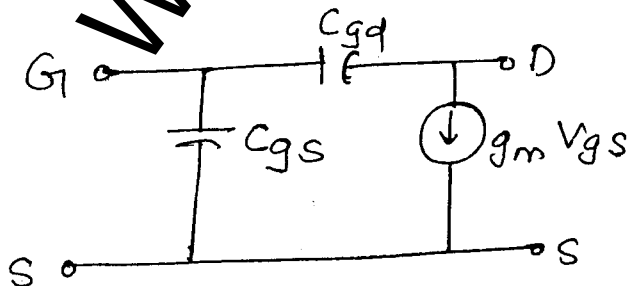6. (a) For the simplified FET model shown determine the capacitances C_{gs} and C_{gd} 10
as well as g_m . Show that for low frequency operation it is sufficient to record the drain current and gate-source voltage under short circuit output condition.



- (b) Plot and compare the frequency response of BJT, FET and HEMT. 10

7. Write short notes on following :—

- Chip components
 - Matching Networks
 - Parallel and series connections
 - Coupled Filters.
- 20