

SATHYABAMA UNIVERSITY

(Established under section 3 of UGC Act, 1956)

Course & Branch: B.E/B.Tech – CSE/IT

Title of the paper: Digital Computer Fundamentals

Semester: III

Max. Marks: 80

Sub.Code: 11305/12305(2003/2004/2005) 6C0044 Time: 3 Hours

Date: 05-11-2008

Session: FN

PART – A

(10 x 2 = 20)

Answer All the Questions

1. Define the $(r-1)^3$ compliment of a number.
2. Convert $(B65F)_{16}$ to Decimal.
3. If $F=x'yz' + x'y'z$. Find the dual of F.
4. Prove that $x+xy=x$.
5. What is decimal adder?
6. What is a Demultiplexer?
7. What is the significance of a state diagram?
8. What is a Synchronous counter?
9. Give the Storage Hierarchy.
10. What is a Virtual memory?

PART – B

(5 x 12 = 60)

Answer All the Questions

11. Use 2-s Complement to perform M-N and hence prove the same with an example.

(or)

12. Perform the following conversions.

(a) $(8620)_{10}$ to BCD

(b) $(8.3)_9$ to decimal

(c) $(50)_7$ to decimal

13. Implement the following function using don't care conditions. Assume that both the normal and Complement inputs are available.

$$F = A'B'C' + AB'D + A'B'CD'$$

$$D = ABC + AB'D' \text{ with not more than two Nor gates.}$$

(or)

14. Obtain the Sum of Expressions in Sum of Products for the Boolean function.

$$BDE + B'C'D + CDE + A'B'CE + A'B'C + B'C'D'E'$$

15. (a) Implement a Full-adder circuit with a decoder and two OR gates.
(b) Give the combinational circuit of a Full – Subtractor.

(or)

16. Implement the following Function with a Multiplexer.

$$F(A,B,C,D) = \Sigma (0,1,3,4,8,9,15)$$

17. Design a counter with the following Binary sequence 0, 1, 3, 7, 6, 4 and repeat. Use T-flop-flops.

(or)

18. What are the different steps involved in analyzing sequential circuits?

19. With an example Explain Random Access Memory.

(or)

20. What are the different operations that are performed on Memory?