

Second Semester Examination, 2004

Basic Electrical Engineering

Full Marks : 70

Time : 3 hours

Answer six questions including  
Q. No. 1 which is compulsory

*The figures in the right-hand margin indicate marks*

1. Answer the following : 2 × 10

- (a) A series R-C circuit is excited by d.c. voltage E through a switch. Find the value of initial current.
- (b) Find the value of final current in a series R-L circuit impressed by d.c voltage V.
- (c) In a single phase a.c. circuit  
 $V = (100 + j 100) \text{ V}$ ,  $Z = (3 + j4) \Omega$ ,  
find the current in polar form.
- (d) A 3-phase delta-connected balanced load each phase having resistance of  $200 \Omega$  is supplied by 3-phase star-connected voltage source of 200 V per phase. Find the total active power consumed by the load.

(Turn Over)

- (e) What is the relative permeability of a non-magnetic material?
- (f) A single-phase autotransformer is excited by 230 V, 1-phase a.c. supply. What would be the range of voltage values available on the secondary side?
- (g) What are the different methods of excitation of d.c. generators?
- (h) Why are 1-phase induction motors used in domestic appliances?
- (i) Which type of generation is preferred for pollution-free environment?
- (j) Name four industrial applications of electrical energy.

2. Use (a) Thevenin's theorem and (b) the principle of Superposition to find the current in a  $2\Omega$  resistor connected between A and B in the circuit shown in Fig. 1.

10



3. When a voltage of 100 V at 50 Hz is applied to a coil A having resistance  $R_A$  and inductance  $L_A$ ; the current taken and power consumed are 8 A and 120 W respectively. When applied to a coil B having resistance  $R_B$  and inductance  $L_B$  the current taken and power consumed are 10 A and 500 W respectively. What current and power will be taken when 100 V is applied across these two coils connected in series? 10

4. Three identical impedances are connected in star across a 440 V, 3-phase, 50 Hz supply. The line current is 40 A and the p.f. is 0.8 leading. Find the value of resistance and capacitance in each phase. 10

5. (a) An electromagnet has an air-gap of length 2 mm and an iron path of length 30 cm. Find the number of ampere-turns necessary to produce a flux density of  $0.8 \text{ Wb/m}^2$  in the gap.  
Take  $\mu = 1500$  for the magnetic material of the electromagnet. 7

- (b) The eddy current loss in a cold rolled grain oriented silicon steel sheet is 100 W when the supply frequency is 50 c/s. Find the eddy current loss when the frequency is 40 c/s, the flux density remaining the same. 3
6. (a) Explain the principle of operation of a single-phase transformer. 4
- (b) The emf per turn of a single-phase, 6600 V/440 V, 50 Hz transformer is 12 V. Calculate
- (i) the number of turns in the primary and secondary windings ;
- (ii) the net cross-sectional area of the core for a maximum flux density of  $1.5 \text{ Wb/m}^2$ . 6
7. (a) What are the different methods of speed control of d.c. shunt motor ? 2

- (b) A 500 V d.c. shunt motor has a speed of 1200 rpm, the line current being 5A. Find the speed when line current increases to 30 A. The shunt field resistance and armature resistance are  $250 \Omega$  and  $1.1 \Omega$  respectively. 5
- 8.
- (a) State the indicating and integrating type instruments that you have studied. 3
- (b) A moving coil instrument has a resistance of  $7.5 \Omega$  and its full scale deflection corresponds to 50 mA. How this instrument can be used to measure,
- (i) current up to 10 A and
- (ii) voltage up to 300 V. 7