

**DIPLOMA IN ELECTRICAL AND
MECHANICAL ENGINEERING (DEME)**

Term-End Examination

June, 2006

BEE-031 : ELECTRICAL TECHNOLOGY

Time : 2 hours

Maximum Marks : 70

Note : Answer **five** questions in all. Question number 1 is **compulsory**. Attempt any **four** of the remaining questions. Use of calculator is allowed.

1. (a) Select the correct answer from the given four alternatives. $1 \times 7 = 7$
- (i) Maximum power from a source having internal resistance R_i is delivered to the Resistive Load R_L if
- (a) $R_i = R_L$
- (b) $R_i > R_L$
- (c) $R_i < R_L$
- (d) $R_i = R_L^2$

(ii) Three resistances of $R \ \Omega$ each are connected in delta. Its equivalent star will comprise resistance of value

(a) $3R$ each

(b) $\frac{R}{3}$ each

(c) R each

(d) $3R, R, \frac{R}{3}$

(iii) Energy stored in an inductor is

(a) $\frac{1}{2} L I^2$

(b) $\frac{1}{2} I L^2$

(c) $L I^2$

(d) $L I$

(iv) Power factor of an AC circuit is equal to

(a) $\frac{R}{X_L}$

(b) $\frac{R}{X_C}$

(c) $\frac{R}{Z}$

(d) $\frac{Z}{R}$

- (v) Emf induced in each conductor of a d.c. machine is
- (a) an alternating emf
 - (b) a direct emf
 - (c) a pulsating emf
 - (d) any wave shape
- (vi) A transformer has maximum efficiency at $\frac{3}{4}$ full load. The ratio of its iron loss and full load copper loss is
- (a) $\frac{16}{9}$
 - (b) $\frac{4}{3}$
 - (c) $\frac{3}{4}$
 - (d) $\frac{9}{16}$
- (vii) An induction motor has synchronous speed of 1500 rpm. What will be the slip, if it is running on a speed of 1450 rpm ?
- (a) 3.33%
 - (b) 3%
 - (c) 5%
 - (d) 6%

(b) Write **true** or **false** for the following statements :

1×7=7


- (i) If the area of plates of a capacitor is doubled and distance between plates is halved then capacitance becomes 4 times.
- (ii) When temperature is decreased the resistance of carbon is increased.
- (iii) If a source is delivering maximum power to load, then efficiency of the circuit is 50%.
- (iv) An emf of 8 V is induced in a coil of inductance 4 H, then the rate of change of current is 0.5 A/s.
- (v) Average value of sinusoidal alternating voltage is $\frac{1}{\sqrt{2}}$ times of its maximum value
- (vi) The construction of DC generator and DC motor is slightly different.
- (vii) The core of transformer is made of insulating material.

2. (a) State superposition theorem. Explain using a practical problem.

7

- (b) Find the value of R_L in network shown in figure necessary to obtain maximum power in it. Also calculate current in R_L .

7

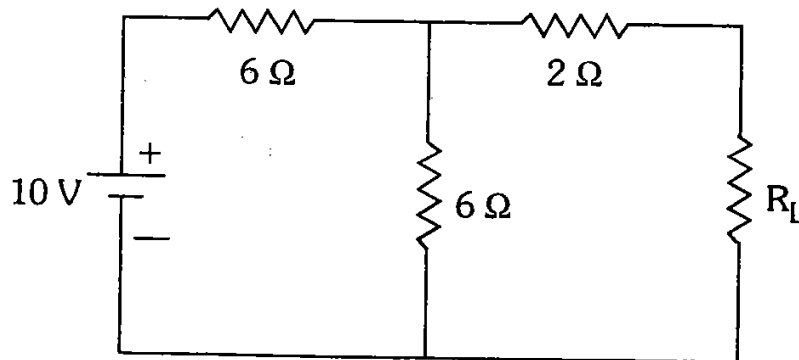


3. (a) Define the following terms :

7

- (i) KVL
- (ii) KCL
- (iii) Mesh & loop
- (iv) Linear and active networks

- (b) Calculate current in $5\ \Omega$ resistor in network shown in figure :

7

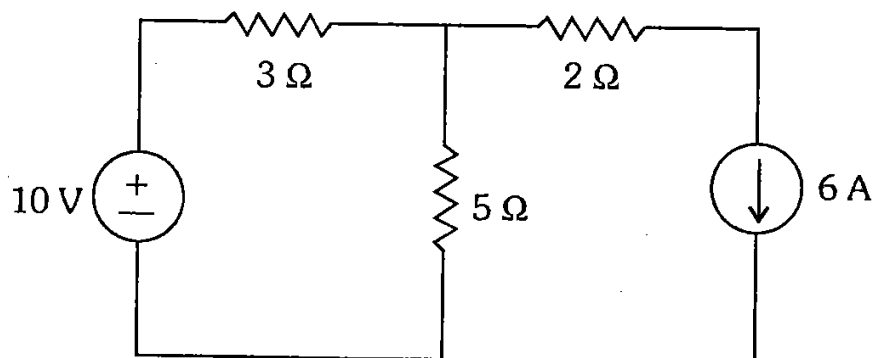

4. (a) Deduce the emf equation for a single phase transformer. 7
- (b) A 100 KVA transformer has 2 KW iron loss and 5 KW full load copper loss. Calculate its maximum efficiency when it delivers load at unity power factor. 7
5. (a) Explain constructional features and working of a 3-phase induction motor. 7
- (b) A 3-phase, star-connected alternator has 72 slots in stator, each slot contains 10 conductors, the stator winding is wound for 6 poles. Calculate voltage induced at terminals of alternator if speed of rotor is 1000 rpm and flux per pole is 0.5 Wb. 7
6. (a) Draw different characteristics of 7
- (i) DC series motor
- (ii) DC shunt generator
- (b) Write need of starter for DC motors. Explain working of three point starter. 7
7. (a) How is an induction motor different from a synchronous motor ? Write their applications. 7
- (b) A synchronous motor is not a self-starting motor. Discuss different methods of its starting. 7

8. Write short notes on any **two** of the following : **2×7=14**

- (i) Thevenin's theorem
- (ii) Voltage build-up in DC shunt generator
- (iii) Three phase rotating magnetic field
- (iv) Voltage regulation in alternator
- (v) Equivalent circuit of transformer