



ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2008
CIRCUIT THEORY & NETWORKS
SEMESTER - 3

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) Maximum power transfer occurs at efficiency of

- | | |
|---------|--------|
| a) 100% | b) 50% |
| c) 25% | d) 75% |
-

ii) A periodic waveform possessing half-wave symmetry has no

- | | |
|------------------|-------------------|
| a) odd harmonics | b) even harmonics |
| c) cosine terms | d) sine terms. |
-

iii) The impedance of an ideal current source should be

- | |
|--|
| a) 0 |
| b) infinite |
| c) greater than 0 but less than infinity |
| d) none of these. |
-

iv) In R-L circuit, the phase angle difference between voltage & current is


- | | |
|---------|---------------------------------------|
| a) 30° | b) 90° |
| c) 180° | d) greater than 0° but less than 90°. |
-



v) Unit step function is first derivative of

- a) ramp function b) impulse function
 c) gate function d) parabolic function.

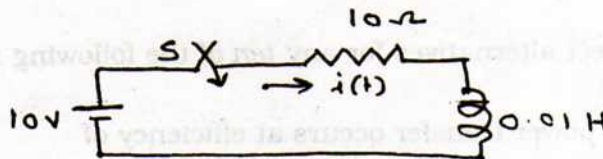vi) After closing the switch 's' at $t = 0$, the current $i(t)$ at any instant 't' in the network shown



is given by

- a) $10 + 10 e^{100t}$ b) $10 - 10 e^{100t}$
 c) $10 + 10 e^{-100t}$ d) $10 - 10 e^{-100t}$

vii) When compared to a first order low pass filter, a second order low pass filter has

- a) lower voltage gain b) higher voltage gain
 c) faster drop in filter response d) higher cut-off frequency.

viii) A cut set schedule gives relation between


- a) branch currents & link currents
 b) branch voltages & tree branch voltages
 c) branch voltages & link voltages
 d) branch currents & tree currents.

ix) The equation $Y = mx + c$ is

- a) linear b) non-linear
 c) parabolic d) none of these.



x) Graphical representation of $u(a-t)$

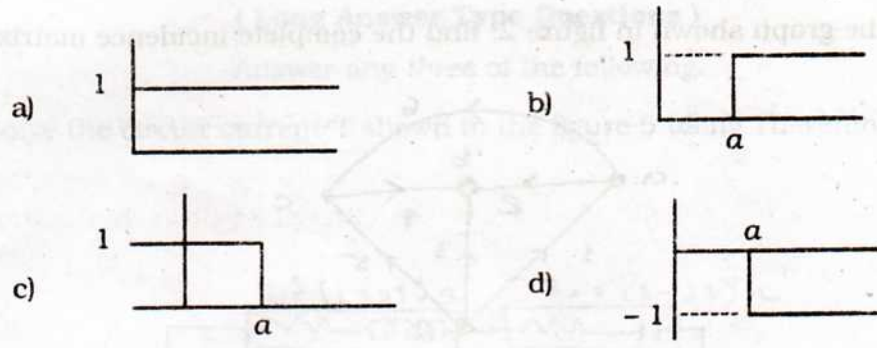

xi) A two port network is reciprocal if & only if

- a) $Z_{11} = Z_{22}$
- b) $BC - AD = -1$
- c) $Y_{12} = Y_{21}$
- d) $h_{12} = h_{21}$

xii) Given $V_{TH} = 20\text{ V}$ & $R_{TH} = 5\Omega$, the current in the load resistance of a network is

- a) 4A
- b) more than 4A
- c) 4A or less
- d) less than 4A.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. 3 × 5 = 15

2. For an RL series circuit shown in the figure 1 with $R = 2\Omega$ & $L = 1\text{H}$ and no initial current in the inductor. A voltage $V = 4e^{-t}$ volts is applied at $t = 0$. Find expression for the resulting current in the circuit for $t \geq 0$ using Laplace transform method.

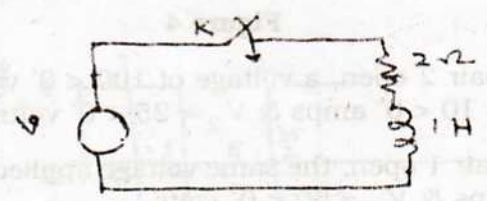


Figure 1



3. a) Define incidence matrix.
- b) For the graph shown in figure 2, find the complete incidence matrix.

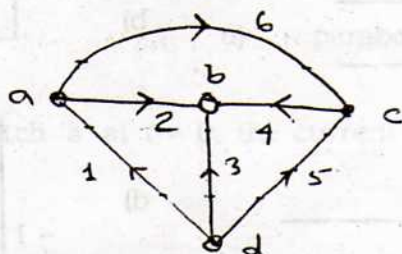


Figure 2

1 + 4

4. What should be the value of Z_2 for maximum power to be delivered in the circuit shown in fig. 3

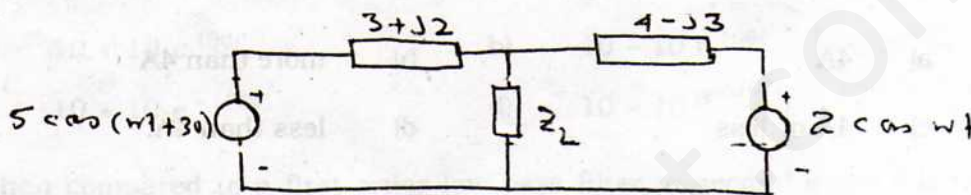


Figure 3

5. In a linear circuit consisting of $R = 9\Omega$ & $L = 8\text{ mH}$, a current. $i = 5 + 100 \sin (1000t + 45^\circ) + 100 \sin (3000t + 60^\circ)$ amps is flowing. Find the equation of applied voltage.
6. Measurements were made on two terminal network shown in figure 4.

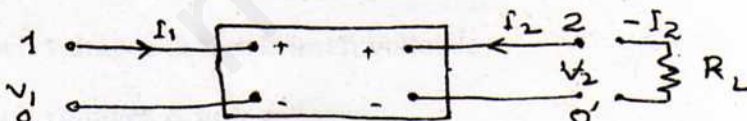


Figure 4

- a) With terminal pair 2 open, a voltage of $100 \angle 0^\circ$ volts applied to terminal pair 1 resulted in $I_1 = 10 \angle 0^\circ$ amps & $V_2 = 25 \angle 0^\circ$ volts.
- b) With terminal pair 1 open, the same voltage applied to terminal pair 2 resulted in $I_2 = 20 \angle 0^\circ$ amps & $V_1 = 50 \angle 0^\circ$ volts.

Write the loop equations for this network and also find the driving point & transfer impedances.



GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following.

3 x 15 = 45

7. a) Solve the circuit current 'i' shown in the figure 5 using Thevenin's theorem.

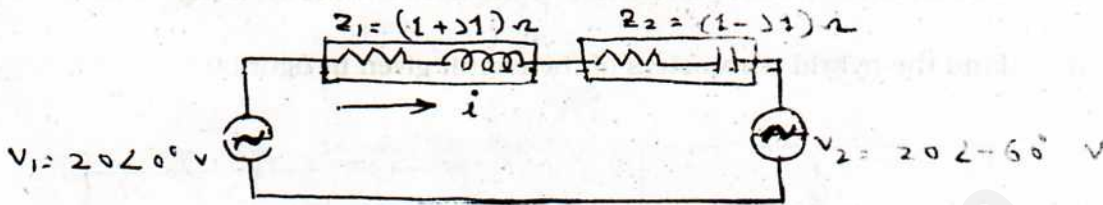


Figure 5

Verify the result obtained by Norton's theorem.

- b) Obtain the output voltage V_0 across X - Y terminal for the circuit shown in figure 6.

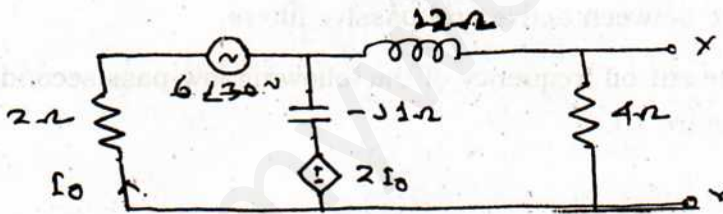


Figure 6

10 + 5

8. a) Find the Fourier series for the square wave shown in figure 7.

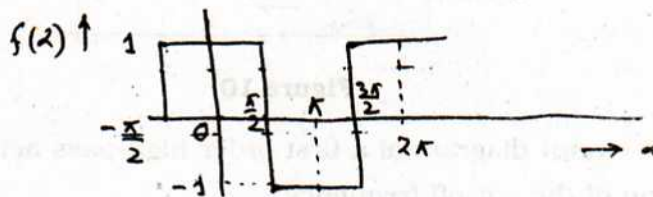


Figure 7



b) Find the Fourier transform of an exponential voltage waveform given by

$$v(t) = V_0 e^{-t} \text{ for } t \geq 0$$

$$= 0 \text{ for } t < 0.$$

10 + 5

9. a) What are transmission parameters ? Where are they most effectively used ?
 b) Calculate the ABCD parameters of the network shown in figure 8.
 c) Find the hybrid parameters of the circuit given in figure 9.

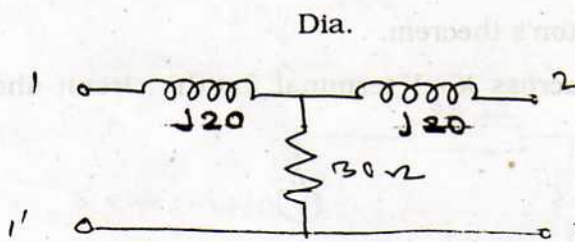


Figure 8

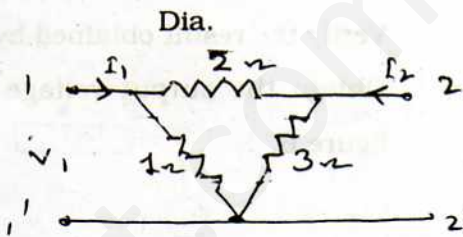


Figure 9

3 + 6 + 6

10. a) Differentiate between active and passive filters.
 b) Find out the cut-off frequency of the following low-pass second order active filter shown in figure 10.

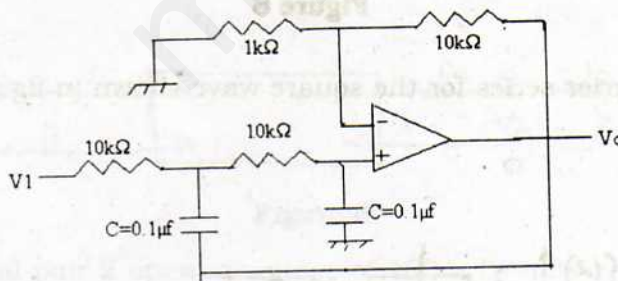


Figure 10

- c) Draw the circuit diagram of a first order high-pass active filter and find out the expression of the cut-off frequency.

5 + 6 + 4



11. a) State superposition theorem. For the network shown in figure 11, calculate current throughout the impedance $(3 + j4)$ ohm using superposition theorem.
- b) In the given circuit of figure 12, find the reading of the voltmeter V. Interchange the current source and voltmeter and verify the Reciprocity theorem.

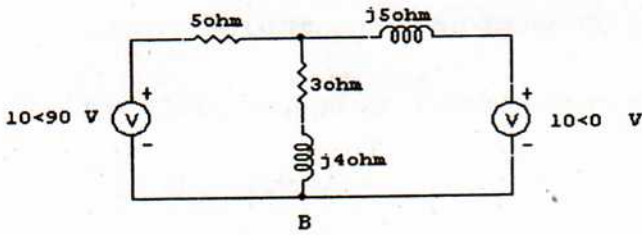


Figure 11

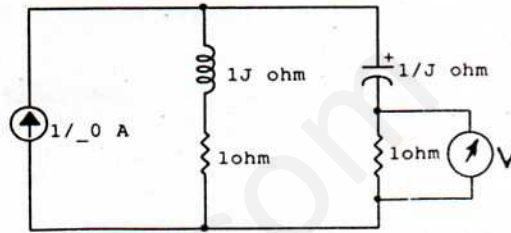


Figure 12

(2 + 6) + 7

END