

## Seventh Semester Examination – 2006

### ADVANCED ELECTRONICS CIRCUITS

Full Marks : 70

Time : 3 Hours


Answer Question No. 1 which is compulsory and any five from the remaining questions.

The figures in the right-hand margin indicate marks for the questions.


1. Answer the following questions : 2×10
- (a) Why active filters are preferred over passive filters ?
  - (b) Define the 3-dB cut-off frequency of a filter.
  - (c) What are the modes of operation of a 555 timer ?
  - (d) Distinguish between a first order and a second order filter.

P.T.O.

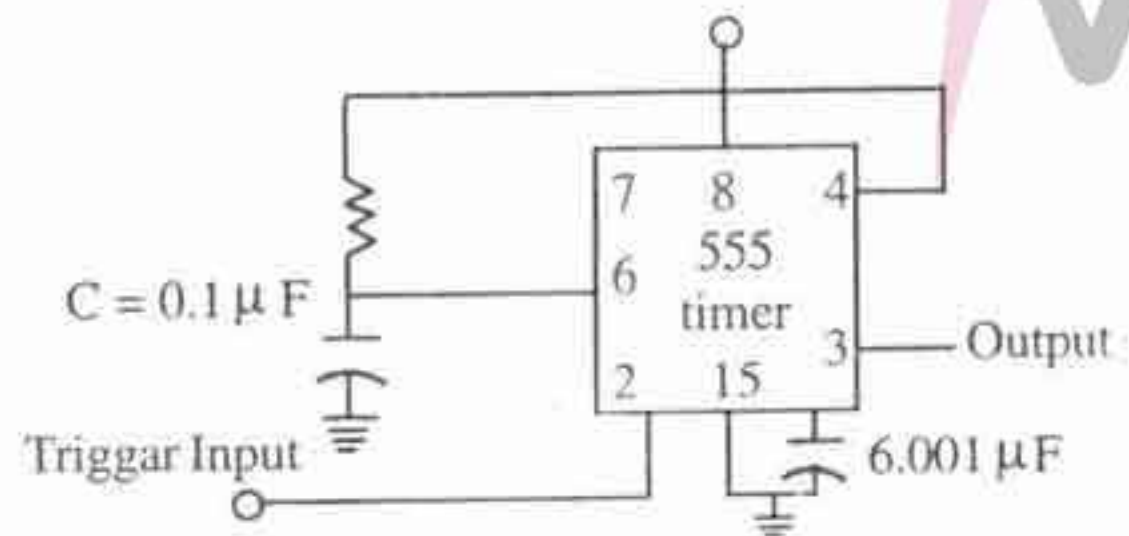- (e) Distinguish between astable, bistable and monostable multivibrators.
- (f) What is done to change the state of a bistable multivibrator?
- (g) What is the output of a UJT oscillator?
- (h) An OPAMP has a slew rate of  $5V/\mu s$ . What is the largest sine wave output voltage possible at a frequency of 1 MHz?
- (i) Determine the period of the output waveform for the circuit of figure shown, when triggered by a negative pulse?



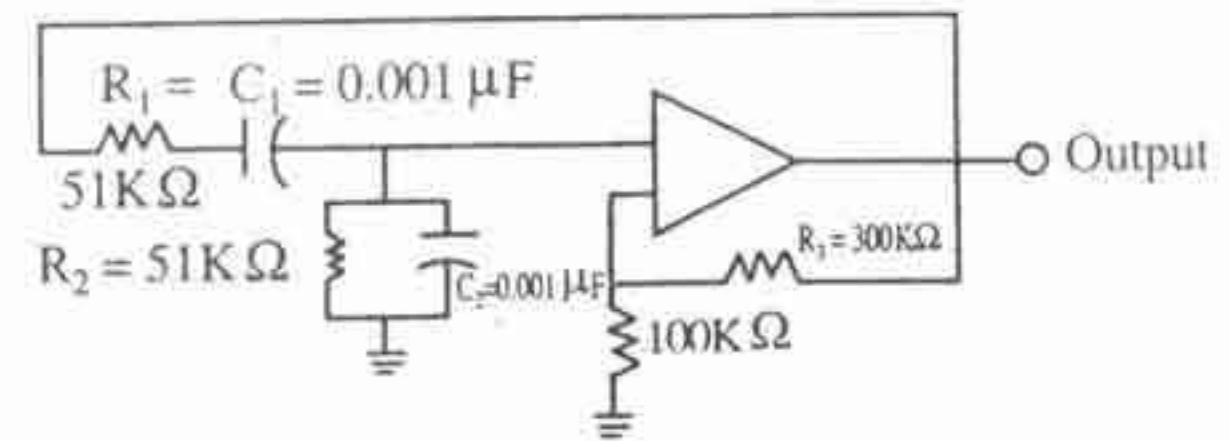- (j) What is the resonant frequency of the Wien bridge oscillator shown in figure?



2. (a) Draw the internal circuit of a 555 timer and write a brief note on it. 5
- (b) What is a voltage-controlled oscillator? Give two applications that require a VCO. 5
3. (a) Design a second-order low pass filter at a high cut-off frequency of 1 kHz. Draw the frequency response of the filter. 5
- (b) Describe with a circuit diagram the operation of a Wien bridge oscillator. Find an expression for the frequency of oscillation. 5
4. (a) What is an instrumentation amplifier? Give three applications of the instrumentation amplifier. 5
- (b) Give the circuit diagram for an opamp which acts as a voltage follower. 5



5. (a) Draw the block diagram for a phase-locked loop system (PLL). 5

(b) Design an astable multivibrator to give a square wave output at 100KHz. The transistors to be used have  $h_{fe} = 50$  and 6 volt dc supply is available. 5

6. (a) With the help of a circuit diagram explain the operation of a UJT relaxation oscillator. Sketch the waveforms at base1, base2 and emitter. 6

(b) Derive the expression for frequency of oscillations. 4

7. Write notes on : ...power of knowledge 5x2

(a) Phase-Locked Loops and their applications

(b) Schmitt trigger circuit, its operation and application.