



ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2007

CIRCUIT THEORY & NETWORKS

SEMESTER - 3

Time : 3 Hours]

(EIE)

[Full Marks : 70

GROUP - A

(Multiple Choice Type Questions)


1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

- i) A four terminal network constitute a
 - a) one port network
 - b) two port network
 - c) four port network
 - d) none of these.

- ii) A capacitor C at time $t = 0 +$ with zero initial charge acts as a
 - a) short circuit
 - b) open circuit
 - c) current source
 - d) voltage source.

- iii) Kirchoff's law fail in case of
 - a) Linear networks
 - b) Non-linear networks
 - c) Dual networks
 - d) Distributed parameter networks.

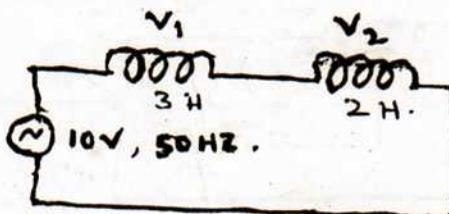- iv) The voltages v_1 & v_2 in the given circuit are
 - a) 6v, 4v
 - b) 4v, 6v
 - c) 5v each
 - d) none of these.





v) It is given that $Z_1 = (2 + j3) \Omega$ & $Z_2 = (6 + j3) \Omega$, Then $|Z_1 + Z_2|$ is

a) 10Ω

b) 14Ω

c) 11Ω

d) none of these.

vi) The phasor combination of resistive power & reactive power is called

a) true power

b) apparent power

c) reactor power

d) average power.

vii) The node method of circuit analysis is based on

a) KVL & ohm's law

b) KCL & kVL

c) KCL, kVL & ohm's law

d) KCL & ohm's law.

viii) Maximum power transfer occurs at a

a) 100% efficiency

b) 50% efficiency

c) 25% efficiency

d) 75% efficiency.

ix) Transient current in a RLC circuit is oscillatory when

a) $R = 2\sqrt{\frac{L}{C}}$

b) $R = 0$

c) $C = R > 2\sqrt{\frac{L}{C}}$

d) $R < 2\sqrt{\frac{L}{C}}$.


x) Two inductors are connected as shown in the following fig. What is the value of the effective inductance of the combination ?

a) 8 H

b) 4 H

c) 10 H

d) 6 H.

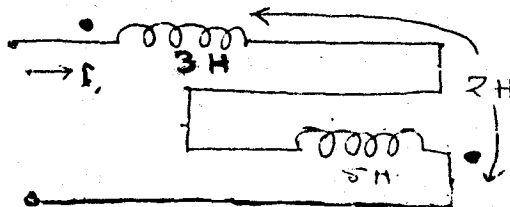




xi) What is the phase angle between inductor current & the applied voltage in a parallel RL circuit ?

- a) 0°
- b) 45°
- c) 90°
- d) 30°.

xii) Thevenin's equivalent resistance of the given circuit is

- a) 2Ω
- b) 0Ω
- c) 1Ω
- d) ∞.

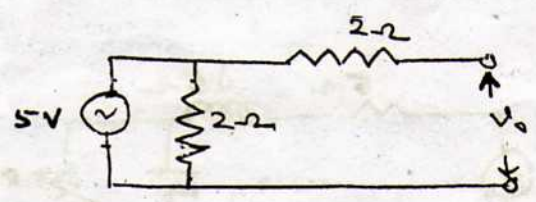


GROUP - B

(Short Answer Type Questions)

Answer any three of the following.

3 × 5 = 15

2. Determine the value of I_x & V_x .

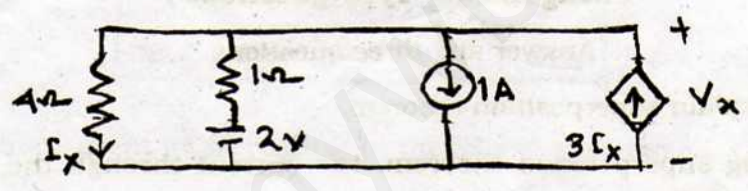


3. a) What is linear time invariant system ?

b) What is impulse response ?


c) The response of a system is given by $y(t) = c \times (t) + x^3(t)$. State whether the system is time-invariant as time-variant.

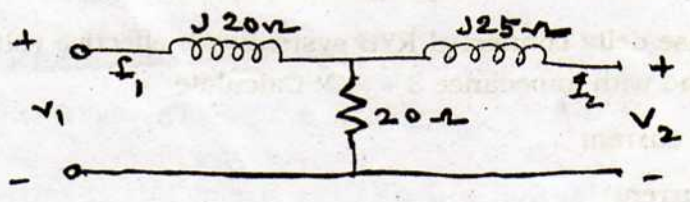4. Determine the Z-parameter of the network shown in the fig. Is it a reciprocal network ?






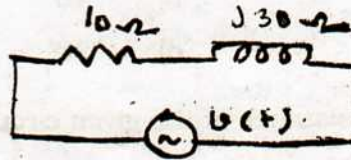5. In the circuit shown below, a voltage $v(t) = 50 \sin(\omega t + 30^\circ)$ is applied. Determine the true power, reactive power & power factor.



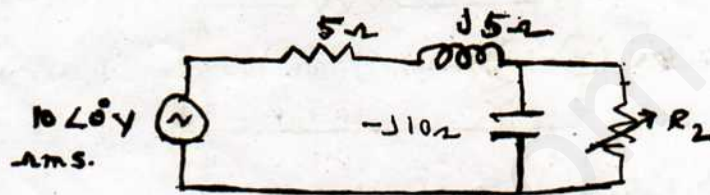6. In the network shown below, find R_L which will dissipate maximum power. Determine also maximum power.




GROUP - C

(Long Answer Type Questions)

Answer any *three* questions.

3 × 15 = 45

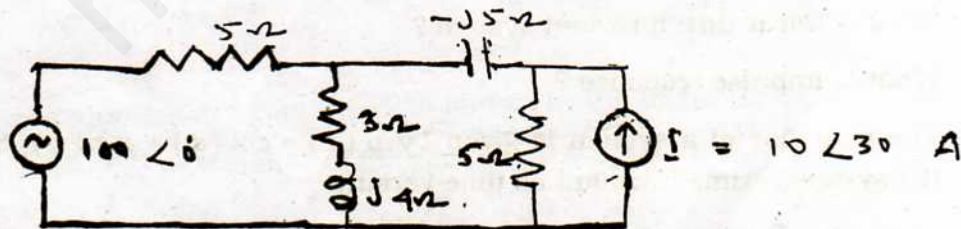7. a) State & explain superposition theorem.
 b) Find using superposition theorem, the current through the capacitor having reactions $-j5 \Omega$.




5 + 10

8. a) Describe the method of measuring reactive power.
 b) A three phase delta connected RYB system with effective voltage of 400 V, has a balanced load with impedance $3 + j4 \Omega$. Calculate
 i) phase current
 ii) line current
 iii) power in each phase.




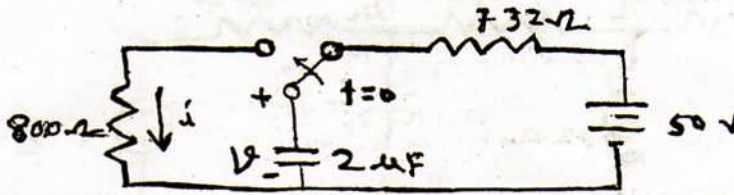- c) Determine $V(0^+)$, $i(0^+)$, $i(2 \text{ ms})$ for the following circuit :




5 + 5 + 5

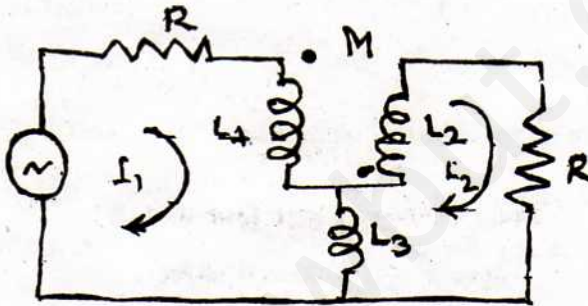9. a) Determine for a two-port network the condition of reciprocity & condition of symmetry in terms of h -parameters.
 b) Draw the voltage phases & current phases of a series R-L circuit. Draw also the impedance triangle.
 c) Find the ratio of I_1 & I_2 for the following circuit :



5 + 5 + 5

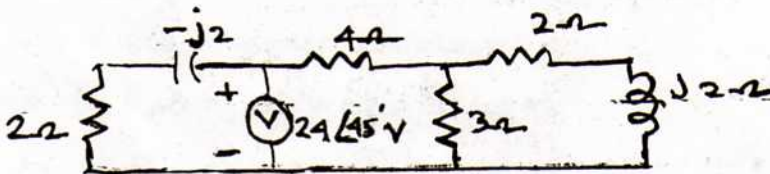10. a) Determine current in 3Ω resistor in the following figure :




- b) Find two elements of a series circuit having current $i = 4.24 \cos(5000t + 45^\circ) \text{ A}$, power 180 w & power factor 0.8 lagging.
 c) An RLC series circuit has $R = 100\Omega$, $L = 500 \text{ mH}$ & $C = 40 \mu\text{F}$. Calculate resonant, lower & upper half power frequency.

8 + 4 + 3



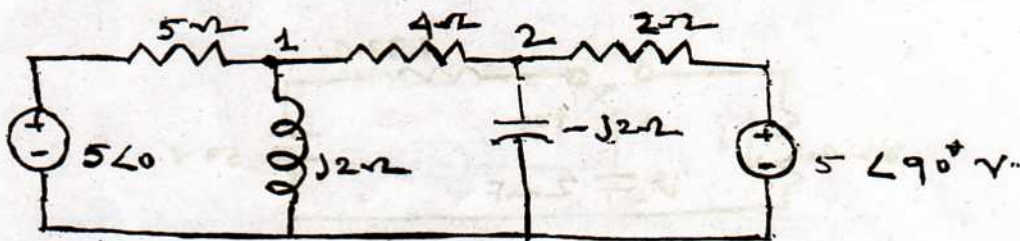11. a) For the network shown, determine the node voltages.



- b) Determine the step response of series R-L-C circuit. Draw the wave forms of the response.
- c) Determine Q factor of a series R-L-C circuit. 5 + 7 + 3

=====
END