

**DiplETE – ET (NEW SCHEME) – Code: DE57****Subject: NETWORKS AND TRANSMISSION LINES**

Time: 3 Hours

**DECEMBER 2009**

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. If  $V_{th}$  and  $R_{th}$  are the thevenin's voltage and resistance,  $R_L$  is the load resistance then thevenin's equivalent circuit consists of

- (A) series combination of  $R_{th}$  and  $V_{th}$   
 (B) series combination of  $R_{th}$ ,  $V_{th}$  and  $R_L$   
 (C) parallel combination of  $R_{th}$ ,  $V_{th}$  and  $R_L$   
 (D) parallel combination of  $R_{th}$  and  $V_{th}$

b. The laplace transfer of shifted unit step function  $f(t) = u(t - a)$  is given by

- (A)  $\frac{a}{s + a}$  (B)  $e^{-as} \left(\frac{1}{s}\right)$   
 (C)  $\frac{1}{s + a}$  (D) None of the above.

c. In z parameter representation if  $z_{21} = z_{12}$  then the network is

- (A) bilateral (B) symmetrical  
 (C) balanced (D) inverse (reciprocal)

d. The characteristic impedance of a distortionless line is

- (A) real (B) inductive  
 (C) capacitive (D) complex

e. For a prototype lowpass filter, the phase constant  $\beta$  in the attenuation band is

- (A)  $\alpha$  (B)  $\pi$   
 (C)  $\frac{\pi}{2}$  (D) 0

f. In a series resonant circuit, the resonant frequency will be

- (A) geometric mean of half power frequencies.  
 (B) sum of half power frequencies.

- (C) arithmetic mean of half power frequencies.  
 (D) difference of half power frequencies.

g. One neper is equal to

- (A) 0.8686 db                      (B) 8.686 db  
 (C) 86.86 db                      (D) 19.686 db

h. Thevenin's theorem is valid for networks containing only

- (A) reactive elements              (B) non linear elements  
 (C) linear elements                (D) bilateral network

i. VSWR on short circuited lossless line is given by:

- (A) 0                                  (B)  $\infty$   
 (C) Unity                              (D) None of above

j. Attenuators have

- (A) attenuation and phase constant    (B) gain only  
 (C) attenuation constant                (D) gain and phase constant

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

**Q.2** a. Explain in detail different types of network elements. **(8)**

b. A current of 5A flows through a parallel combination of resistive network of  $20\Omega$  &  $30\Omega$ . Find the

- (i) Power observed in the resistor.  
 (ii) Energy dissipated in the resistor/minute.  
 (iii) Charge flow through the resistor/minute.  
 (iv) Net resistance. **(8)**

**Q.3** a. State superposition and maximum power transfer theorem. **(4+4)**

b. Use Millman's theorem to determine the voltage  $V_s$  of the network shown in Fig.1 given that  $V_R = 230\angle 0^\circ V$ ,

$$V_Y = 230\angle -120^\circ V,$$

$$V_B = 230\angle 120^\circ V. \quad \text{(8)}$$

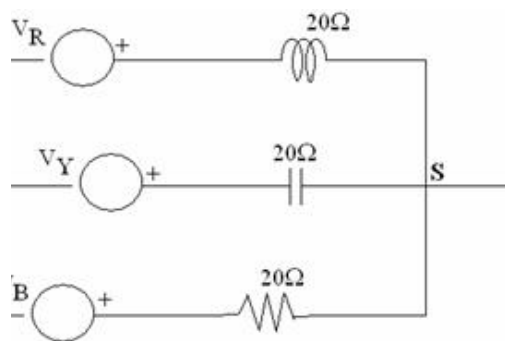


Fig.1

(iii) L

includes  $4\mu\text{F}$  capacitor and a resistance of  $16\Omega$ . If the bandwidth is  $500\text{ rad/sec}$ ,

(ii) Q

(8)

b. A two branch antiresonant circuit contains  $L = 0.4\text{H}$ ,  $C = 40\mu\text{F}$ . The resonance is to be achieved by variation of  $R_L$  and  $R_C$ . Calculate the resonant frequency for the following cases:

(i)  $R_L = 120\Omega$   $R_C = 80\Omega$ (ii)  $R_L = 80\Omega$   $R_C = 0$ (iii)  $R_L = R_C = 100\Omega$ 

(8)

**Q.5** a. State and prove convolution theorem (Integral).

(8)

b. Derive an expression for Laplace transform of an impulse function.

(8)

**Q.6** a. Define and derive expressions for

(i) Characteristic impedance.

(ii) Propagation constant.

(iii) Attenuation and phase constants of a transmission line in terms of primary constants.

(iv) Velocity of propagation.

(8)

b. A certain telephone cable without loading has the following constants/Km  $R = 25\Omega$ ,  $L = 0.6\text{MH}$   $C = 0.04\mu\text{F}$  &  $G$  is negligible. The loading coils of inductance  $45\text{ mH}$  and resistance  $20\Omega$  are now placed at intervals of  $1\text{ Km}$ . Calculate the attenuation/Km of loaded cable at  $1000\text{H}$  and the highest frequency of transmission.

(8)

**Q.7** a. What is meant by impedance matching in transmission lines? Discuss briefly different impedance matching elements used.

(8)

b. The terminating load of 4HF of transmission lines  $z_o = 50\angle 0^\circ\Omega$  working at  $300\text{ MHz}$  is  $50 + j50\Omega$ . Calculate VSWR and the position of the voltage minimum nearest to the load.

(8)

**Q.8** a. Derive an expression for design impedance of a symmetrical T attenuation.

(8)

b. Derive an *m-derived T section low pass filter* having cutoff frequency  $f_c = 1000\text{Hz}$ , Characteristics impedance  $R = 600\Omega$  & frequency of infinite attenuation  $f_\infty = 1050\text{Hz}$ .

(8)

**Q.9** a. Derive the expression for ABCD parameters in terms of Y parameters.

(8)

b. For the given bridge T network, find the driving point admittance  $Y_{11}$  and transfer admittance  $Y_{21}$  with a  $2\Omega$  load resistor connected across port 2.

(8)

