

Computer Organisation and

Architecture

2008 May

Technology BCA

Semester 2

University Exam

Mangalore University

UNIT-II

4. a. What are NAND and NOR gates? Explain their functionality with logic diagram and truth table.
 b. Simplify the Boolean function.
 $F(x,y,z) = \sum (0,2,4,5,6)$
 c. Implement the following function with NAND gate.
 $F(x,y,z) = \sum (0,6)$ (5+5+5)

OR

5. a. What are minterms and maxterms? Explain with example.
 b. Obtain the simplified expression in
 i) Sum of products
 ii) Product of sums for the expression
 $x'z' + y'z' + yz' + xyz$
 c. State and prove the theorems of Boolean Algebra. (3+6+6)

UNIT-III

6. a. Explain state diagram and state table.
 b. Design mod 6 counter using JK flip-flop.
 c. Explain 2 bit magnitude Comparator. (4+6+5)

OR

7. a. Explain the working of D flip-flop using NAND Gate.
 b. Explain a 4-bit ripple counter.
 c. Design a 3-bit counter using T Flip Flop. (5+5+5)

UNIT-IV

8. a. With a circuit diagram explain the working of a BCD adder.
 b. Explain construction of ALU.
 c. Perform the following arithmetic operation using 1's and 2's operation:
 56-48 (5+5+5)

OR

9. a. Explain 4 bit parallel adder using full adder.
 b. Perform the following arithmetic operation using 9's and 10's Complement form. Verify using ordinary calculation.
 i) 967-532 ii) 899-48
 c. Explain shift operation with a suitable logic diagram. (5+5+5)

* * *