
g. Standard unit capacitance value C_g for $5\ \mu\text{m}$ MOS transistor is _____.

(A) 0.0005 pF
(C) 0.01 pF

(B) 0.04 pF
(D) 0.02 pF

h. Overall delay fd for nMOS cascaded inverter driven by large capacitive load is _____.

(A) $3.5\ eN\ \tau$
(C) $1.5\ eN\ \tau$

(B) $4.5\ eN\ \tau$
(D) $2.5\ eN\ \tau$

i. Gate Area A_g is scaled by _____.

(A) $1/\alpha$
(C) $1/\alpha^2$

(B) $1/\beta$
(D) $1/\beta^2$

j. In constant field scaling model _____.


(A) $\alpha = \frac{1}{\beta}$
(C) $\beta = \alpha$

(B) $\beta = 1$
(D) $\alpha = 1$

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. With neat diagram explain the working of enhancement mode nMOS transistor. (8)
b. Design the inverter using CMOS logic. Explain its characteristics also. (8)
- Q.3** a. Derive an expression for I_{ds} in non saturated and saturated region. (10)
b. What is body effect? Explain briefly how threshold voltage V_t will be affected by body effect. (6)
- Q.4** a. Obtain pull up to pull down ratio for a nMOS inverter driven through one or more pass transistor. (10)
b. Explain the working of MOSFET. (6)
- Q.5** a. Write λ based design rules for wires and transistor. (8)
b. Define sheet resistance and standard capacitance for a feature size transistor. (8)
- Q.6** a. Derive an expression for total delay for N-cascaded inverters driving a large capacitive load. (8)

- b. Two nMOS inverters are cascaded to drive a capacitive load $C_L = 16C_g$ as shown in Fig.1. Calculate pair delay in terms of τ . (8)

 

Inverter 1

$$\begin{aligned} L_{pu1} &= 16 \lambda \\ W_{pu1} &= 2 \lambda \\ L_{pd1} &= 2 \lambda \\ W_{pd1} &= 2 \lambda \end{aligned}$$

Inverter 2

$$\begin{aligned} L_{pu2} &= 2 \lambda \\ W_{pu2} &= 2 \lambda \\ L_{pd2} &= 2 \lambda \\ W_{pd2} &= 8 \lambda \end{aligned}$$

Fig. 1

- Q.7** a. Obtain scaling factor for the following:
 (i) Parasitic capacitance (ii) Channel resistance (iii) Gate delay
 (iv) Saturation current (8)
- b. Design a two-line to four-line decoder circuit to the mask layout level and determine its boundary box. (8)
- Q.8** a. Design two input NOR gate using CMOS. (6)
- b. Write an example of an inverter showing that the power dissipation decreases at the expense of area. (10)
- Q.9** a. Write a note on design styles in VLSI. (6)
- b. Obtain test-vector for the Fig.2, using sensitised path based testing. (10)

 


Fig.2