

Code :R5100406

## B.Tech I Year (R05) Supplementary Examinations, May 2011

## NETWORK ANALYSIS

(Common to Electronics &amp; Communication Engineering, Electronics &amp; Instrumentation Engineering, Biomedical Engineering, Electronics &amp; Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions  
All questions carry equal marks  
\*\*\*\*\*

- State and Explain Kirchoff's Laws.
  - Derive the expression for energy stored in an ideal capacitor.
  - Find the value of R and the current flowing through it when the branch AD carries no current. (Figure 1)

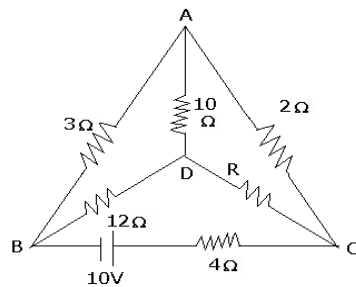


Figure 1:

- Explain the Dot Convention for mutually coupled coils.
  - Derive the Expression for coefficient coupling between pair of magnetically coupled coils.
  - Write the Loop Equations for the Coupled circuit shown in Figure 2.

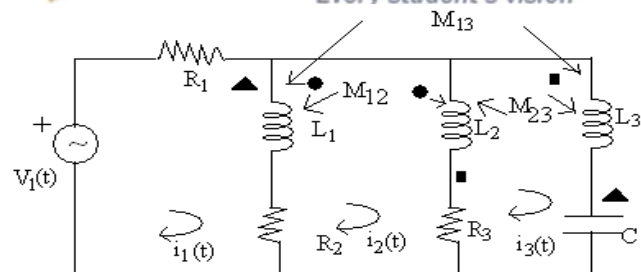


Figure 2:

- Derive the expression for "Band Width" in a series R-L-C circuit. Discuss the effect of Resistance of the circuit on Band Width.
  - In the circuit shown in Figure 3, the switch 's' is in position 1 for a long time and is moved to position 2 at  $t=0$ . Determine the expression for  $V_R(t)$  and  $V_C(t)$ .

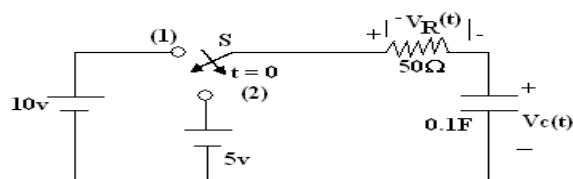


Figure 3:

- Determine the current  $i(t)$  in the network (Figure 4) shown using Laplace Transforms.
  - Define RMS value, Average value, Form factor & peak factor of a periodic quantity. Determine the above values for a full wave rectified sine wave.

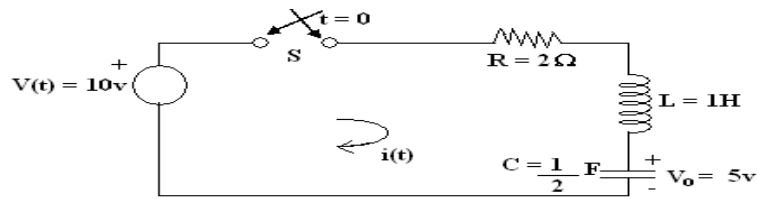


Figure 4:

5. (a) A heating element pure resistive rated for 450 watts, 110 V is to be worked from 220V, 50Hz main supply by connecting a series inductor. Calculate the value of the inductance needed?
- (b) A load consumes 100 watts at 0.8 p.f lagging. If the load voltage and current phasors are expressed as follows, evaluate A and B:  
 $V = (25 + jA)$  volts  
 $I = (B + j1)$  Amps.
6. (a) A typical two-port network is characterized by the equation  $2V_1 + 4I_2 = I_1$  and  $V_2 + 6V_1 = 8I_2$ . Determine the values of
  - i.  $y_{11}$
  - ii.  $z_{21}$  and
  - iii.  $h_{21}$
- (b) Obtain the input and output impedances of an amplifier having  $h_{11} = 2\Omega$ ;  $h_{12} = 1\Omega$ ;  $h_{21} = 5$  and  $h_{22} = 2\Omega$ , if it is driven by a source having an internal resistance of  $4\Omega$  and is terminated through a load which draws maximum power from the amplifier.
7. (a) Draw the circuit of symmetrical Bridged T-attenuator. Derive the design equations for the symmetrical Bridged T-attenuator.
- (b) Design symmetrical bridged T-attenuator with design impedance of  $300\Omega$  and attenuation of 60dB.
8. (a) Explain the variation of attenuation, phase shift and characteristic impedance of m derived low pass filter?
- (b) Design a low pass m derived T section having a cut off frequency of 2.5 KHz, a frequency of infinite attenuation 2.65 KHz and a design impedance of 600 ohm.

\*\*\*\*\*