

Total No. of Questions—12]

[Total No. of Printed Pages—4+2

**[3862]-171**

**S.E. (Instrumentation and Control) (First Sem.) EXAMINATION, 2010**

**FUNDAMENTALS OF INSTRUMENTATION**

**(2008 COURSE)**

**Time : Three Hours**

**Maximum Marks : 100**

**N.B. :—** (i) Answer *three* questions from Section I and *three* questions from Section II.

(ii) Answers to the two Sections should be written in separate answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Your answers will be valued as a whole.

(vi) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(vii) Assume suitable data, if necessary.

**SECTION I**

1. (a) Explain the requirement and contents of calibration certificate and calibration report in calibration process. [8]

(b) What is input, output impedance and loading effect in measurement systems ? [8]

P.T.O.

Or

2. (a) Explain the following terms : [8]

(i) Drift

(ii) Reproducibility

(iii) Dead zone

(iv) Hysteresis.

(b) A moving coil voltmeter has a uniform scale with 100 divisions. The full scale reading is 200 V and 1/10 of scale division can be estimated with fair degree of certainty. Determine the resolution of the instrument. [4]

(c) A 0.300 V voltmeter has an accuracy of +2% of full scale deflection. What would be the range of readings if true voltage is 30 V ? [4]

3. (a) Explain the construction and working of single phase induction type energymeter. [8]

(b) Design the Aryton (universal) shunt to provide an ammeter with current ranges of 1 A, 5 A and 10 A. A basic meter with internal resistance of 50  $\Omega$  and full scale deflection current of 1 mA is to be used. [8]

Or

4. (a) For the series type ohmmeter prove that : [8]

where,  $I_m$  is the current when measuring the unknown resistance  $R_x$ .

$I_{fs}$  is the full scale deflection current.

$R_h$  is the half scale deflection meter.

- (b) Explain how D.C. potentiometer can be used for calibration of voltmeter. [8]

5. (a) A resistance bridge has the configuration shown in Fig. 1, in which  $R_1 = 120.4 \text{ } \Omega$ ,  $R_2 = 119.0 \text{ } \Omega$  and  $R_3 = 119.7 \text{ } \Omega$  :

(i) What resistance must  $R_4$  have for balancing of the bridge?

(ii) If  $R_4$  has a value of  $121.2 \text{ } \Omega$  and if the input voltage is  $12 \text{ V d.c.}$ , what is the output voltage of the bridge, assuming it to be a voltage sensitive bridge. [8]

$$\frac{W}{S} = \frac{I_m}{I_{fs}} = \frac{R_h}{R_x + R_h},$$

Fig. 1

- (b) With the help of neat diagram derive the balancing condition in Hay's bridge and explain how it can be used for measurement of quality factor of a coil. [8]
- (c) Differentiate voltage and current sensitive bridges. [2]

*Or*

6. (a) The Schering bridge as shown in Fig. 2 balances under the following conditions : [10]

$$C_2 = 400 \text{ pf}, \quad R_4 = 10$$

$$R_3 = 1 \text{ kW}, \quad C_4 = 100 \text{ pf}$$

The bridge is driven by 1 kHz sine source. Find unknown capacitance  $C_1$  and its internal resistance  $r_1$ . Find the dissipation factor.



Fig. 2

- (b) Derive equation for sensitivity in Wheatstone bridge and show that the bridge sensitivity is maximum when ratio arm is equal to 1. [8]

## SECTION II

7. (a) Explain how phase can be measured using digital phase-meter. [8]  
(b) With the help of neat block diagram explain the working of DMM with typical specifications. [8]

*Or*

8. (a) List the advantages of Digital Instruments over analog instruments. [8]  
(b) Write a note on Digital Tachometer. [8]
9. (a) Explain dual trace and dual beam oscilloscope. [8]  
(b) How can phase and frequency be measured using X-Y mode of dual trace oscilloscope ? [8]  
(c) Explain Z-modulation in CRO. [2]

*Or*

10. (a) What is the role of a time base generator in CRO ? [8]

(b) An electrically deflected CRT has a final anode voltage of 2000 V and parallel deflecting plates 1.5 cm long and 5 mm apart. If the screen is 50 cm from the centre of deflecting plates, find : [8]

(i) beam speed

(ii) the deflection sensitivity of the tube

(iii) the deflection factor of the tube

(Mass of electron =  $9.1 \times 10^{-31}$  kg, Charge of electron =  $1.6 \times 10^{-19}$  C)

(c) In XY mode if the frequency of signal applied to X channel is 200 Hz and Y channel is 100 Hz, then draw the Lissajous pattern obtained on the CRT screen. [2]

11. (a) The chart speed of a recording instrument is 10 mm/s. If the time base of the recorded signal is 20 mm, what is the frequency of the recorded signal ? [8]

(b) How are triangular and sine waves generated in a function generator ? [8]

*Or*

12. (a) Explain different marking mechanism used in recorders. [8]

(b) Explain the difference between strip chart recorder and X-Y recorder. [8]