

Total No. of Questions : 12]

[Total No. of Pages : 4

P1535

[3762]-151

S.E. (Instrumentation)

FUNDAMENTALS OF INSTRUMENTATION

(2008)

Time : 3 Hours]

[Max. Marks : 100

Instructions to the candidates :

- 1) Answer 3 questions from Section I and 3 questions from Section II.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Assume suitable data, if necessary.


SECTION - I

Q1) a) Explain the following terms: [8]

- i) Precision and significant figures.
- ii) Fidelity.
- iii) Measuring lag.
- iv) Hysteresis.

b) It is desired to measure the value of current in 500 Ω resistor as shown in Fig.1 by connecting a 100 Ω ammeter. Find [8]

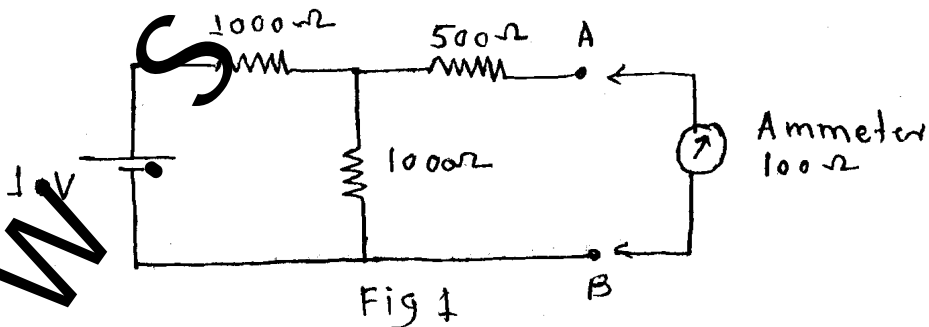- i) Actual value of current.
- ii) Measured value of current.
- iii) The percentage error in measurement and accuracy.



OR

P.T.O.

- Q2) a) Prove that, when shunt connected instrument is connected to circuit, the measured voltage is given by [8]

$$E_L = \frac{E_0}{1 + \frac{Z_0}{Z_L}}$$

where - E_L = Actual voltage measured.

Z_0 = Output impedance of circuit.

Z_L = Input impedance of circuit.

E_0 = Voltage at no load.

- b) Explain general documented procedure for calibration of equipment. [8]

- Q3) a) Sketch and describe the slide wire Potentiometer. Explain the process standardization. [8]

- b) Design a series type of ohm - meter the movement to be used requires 5mA for full scale deflection and has internal resistance of 50 Ω . The internal battery has a voltage of 3V. The desired value of half scale resistance 3000 Ω . Calculate the values of series and parallel resistances R_1 and R_2 . [8]

- c) Explain the function of swap many resistance. [2]


OR

- Q4) a) Explain the principle of working of moving Iron instruments. Explain the construction and working of attraction type and repulsion type of instruments. [8]

- b) Design an Ayrton shunt to provide an ammeter with current ranges of 1A, 5A and 10A. D'Arsonval movement with internal resistance of 1K Ω and full scale deflection current of 10mA is used. [8]

- c) A basic D'Arsonval movement has a full scale deflection current of 100 μ A. It is used as voltmeter. Calculate sensitivity of voltmeter. [2]

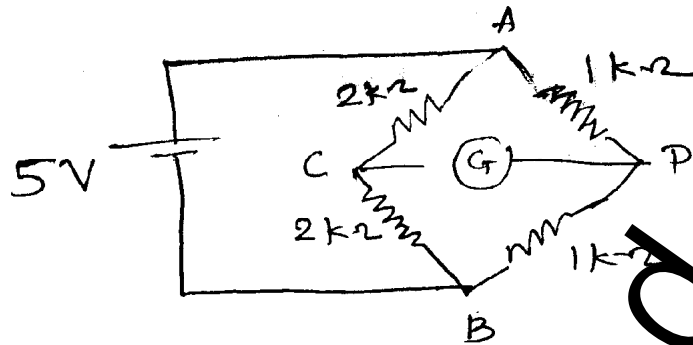- Q5) a) Derive an expression to find unknown frequency using Wein bridge.[8]
- b) As shown in circuit below of wheatstone bridge, the battery voltage is 5V with negligible internal resistance. The galvanometer has current sensitivity of $10\text{mm}/\mu\text{A}$ and internal resistance of $100\ \Omega$. Calculate the deflection of galvanometer caused by $15\ \Omega$ unbalance in Arm BC. [8]



OR

- Q6) a) Derive the balancing condition in Kelvin double bridge. [8]
- b) Derive the equation for measuring dissipation factor & unknown capacitance using Schering bridge. [8]

SECTION - II

- Q7) a) With the help of neat diagram, explain the construction and working of Digital Tachometer. [8]
- b) Write a short note on digital kilo-watt Hour meter. [8]

OR

- Q8) a) Explain how the distance is measured using Digital ultrasound meter.[8]
- b) Write a short note on Digital thermometer. [8]

- Q9) a) Explain amplitude, frequency, phase difference and unknown frequency is measured in dual trace oscilloscope. [8]
- b) Explain the difference between dual mode & X-Y mode of dual trace oscilloscope. Also explain the Alt & Chop mode of dual trace oscilloscope. [8]
- c) Explain how intensity knob controls the brightness of image in CRO.[2]

OR

- Q10)**a) Write the functions of various front Panel control of CRO. [8]
b) With the help of neat diagram explain the working of Digital Storage Oscilloscope. [8]
c) Write typical specifications of CRO. [2]

- Q11)**a) Explain with help of neat diagram concept of virtual instrumentation.[8]
b) Write a short note on potentiometric recorder. [8]

OR

- Q12)**a) Explain with help of neat diagram working of function generators. [8]
b) Explain the working of galvanometric type of recorders. [8]

