

Reg. No. \_\_\_\_\_

# Karunya University

(Karunya Institute of Technology and Sciences)

(Declared as Deemed to be University under Sec.3 of the UGC Act, 1956)

## End Semester Examination – April/May 2010

Subject Title: Solid State Circuits - II

Time : 3 hours

Subject Code: EC206

Maximum Marks: 100

### Answer ALL questions

#### PART – A (10 x 1 = 10 MARKS)

- \_\_\_\_\_ filter is one in which at very high frequencies, capacitor acts almost as a short circuit.
- Name any two important non sinusoidal waveforms in pulse circuitry.
- A bistable circuit is one which can be induced to make an \_\_\_\_\_ from one state to the other by means of external excitation.
- Define LTP in the Schmitt trigger circuit.
- \_\_\_\_\_ circuit has one stable state and one quasi stable state.
- The transition time may be reduced by introducing small \_\_\_\_\_ in parallel with the coupling resistors  $R_1$ , of the binary.
- Define constant current charging.
- Which one of the following is more efficient:  
a. Vacuum tube television sweep (or) b. Transistor television sweep.
- What is meant by multihar?
- Define sampling gate.

#### PART – B (5 x 3 = 15 MARKS)

- Under certain conditions, high pass RC circuit can act like a Differentiator. Justify.
- Give the applications of Schmitt trigger.
- Differentiate monostable multivibrators and Bistable multivibrators.
- Define displacement error and transmission error.
- Mention any three applications of Blocking Oscillator.

#### PART – C (5 x 15 = 75 MARKS)

- a. Explain the response of high pass RC circuit for a square input when  $\tau \ll T$  and  $\tau \gg T$ .  
(where  $\tau$  - time constant). (8)  
b. Neatly sketch the ramp response of low pass RC circuit. (7)  
(OR)
- What is an attenuator? Draw and explain the response of an attenuator to a step input.
- Explain the operation of self biased transistor binary with neat diagram. Draw its input and output waveforms.  
(OR)
- Calculate the stable state currents and voltages for the flip flop circuit (a) shown below, consisting of two cross-coupled inverter circuits whose parameter values are given in figure (b). Assume that the transistor have a minimum  $h_{FE}$  value of 20.

[P.T.O]

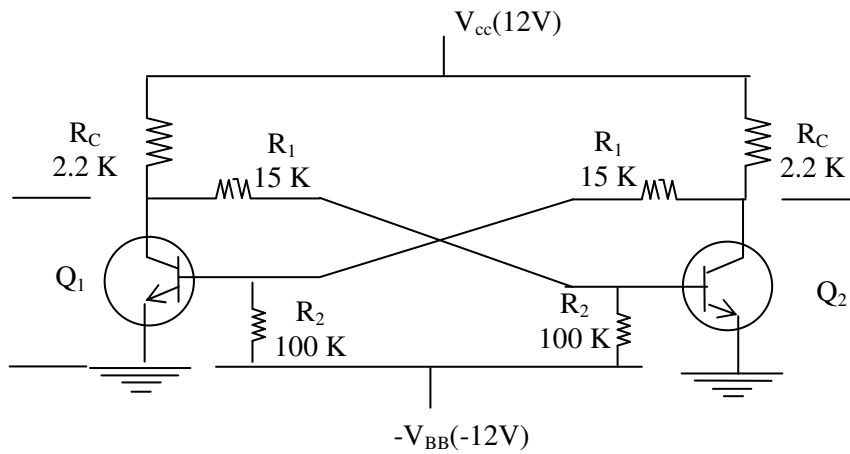


Fig. (a) Flip Flop circuit


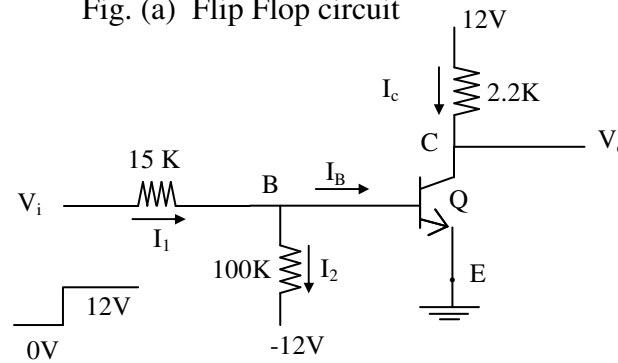


Fig. (b) Interior Circuit

20. Draw the circuit and explain the operation of emitter coupled monostable multivibrator. Also draw its waveforms.

(OR)

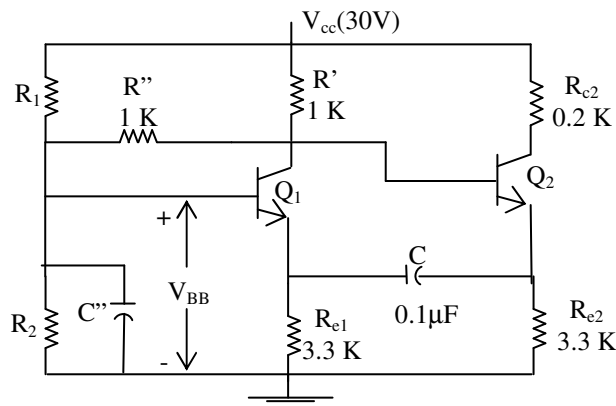21. In the following circuit,  $V_{cc} = 30V$ ,  $R_2 = 2R_1 \ll R''$ ,  $C = 0.1\mu F$ ,  $R_{c2} = 0.2k$ ,  $R' = R'' = 1K$  and  $R_{e1} = R_{e2} = 3.3K$ . Calculate (a) Draw and mention the voltage levels of the waveforms and (b) the frequency of oscillations. Assume Silicon transistors with  $h_{FE} = 30$ .



22. What are the general features of sweep signal? Discuss in detail.

(OR)

23. Discuss in detail, the block diagram of a time base system using transistor.

24. With neat diagram, explain the operation of transistor based bidirectional linear gate.

(OR)

25. Explain the operation of astable transistor blocking oscillator (Diode – Controlled) with neat diagrams.