

Reg. No. _____

Karunya University

(Karunya Institute of Technology and Sciences)

(Declared as Deemed to be University under Sec.3 of the UGC Act, 1956)

End Semester Examination – November/December 2010

Subject Title : **SOLID STATE CIRCUITS - II**

Time : 3 hours

Subject Code: **EC206**

Maximum Marks: 100

Answer ALL questions

PART – A (10 x 1 = 10 MARKS)

1. What is time constant of a circuit?
2. What is double ended clipping?
3. What is a quasi stable state?
4. What is symmetrical triggering?
5. Mention an application of monostable multivibrator.
6. What is a V to f converter?
7. Why are time base generators called sweep circuits?
8. What is the advantage of Miller integrator over Bootstrap circuit?
9. What is a unidirectional sampling gate?
10. What do monostable and astable blocking oscillators generate?

PART – B (5 x 3 = 15 MARKS)

11. Draw the circuit and output waveforms of a shunt clipper which clips above a reference level.
12. Define UTP and LTP of a Schmitt trigger circuit. How can they be varied?
13. Explain a method of triggering a monostable multivibrator.
14. Mention three different methods of generating a time base waveforms.
15. List the various applications of a blocking oscillator.

PART – C (5 x 15 = 75 MARKS)

16. a. Explain the operation of a low pass RC circuit. Describe with necessary equations and diagrams its response to a square wave input. (9)
b. Calculate the rise time, time constant and the time to charge fully of a RC circuit with $R = 50 \text{ k}\Omega$ and capacitor $C = 500\text{pF}$. (6)
(OR)
17. a. Explain with circuit diagram the operation of a positive clamper. (8)
b. Draw a circuit to transmit the part of a sine wave that lies between - 3V to + 6V. (7)
18. a. Explain with a circuit diagram, the operation of a Schmitt trigger. (8)
b. Explain how it can be used as a sine to square wave converter. (7)
(OR)
19. a. Describe with a circuit diagram the functioning of a fixed bias bistable multivibrator. (10)
b. Write a note on the commutating capacitors used. (5)
20. With the help of a circuit diagram and waveforms, explain the working of an emitter coupled monostable multivibrator.
(OR)
21. Explain the working of a collector coupled astable multivibrator. Obtain an expression for frequency of oscillation of the circuit.
22. Describe the working of a simple transistor current time base generator.

[P.T.O]

(OR)

23. Explain the basic principle of a Miller time base generator and explain the working of a transistor Miller time base generator.

24. Describe the working of a bidirectional sampling gate using transistors.

(OR)

25. With the help of a circuit diagram and waveforms, explain the working of a triggered transistor monostable blocking oscillator.