

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech (ECE)/SEM-4/EC-402/2010**

**2010**

## **DIGITAL ELECTRONIC CIRCUITS**

**Time Allotted : 3 Hours**

**Full Marks : 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

### **GROUP - A ( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :  $10 \times 1 = 10$

i) A message bit is 010101. We are using even parity generator. So the parity bit added to the message bit is

- a) 0                          b) 1  
c) 0 & 1                      d) none of these.

ii) What is the decimal equivalent code for the following canonical ?

$$P(X, Y, Z) = (X + Y + Z') (X + Y' + Z') (X + Y + Z) (X' + Y + Z') \\ (X' + Y' + Z')$$

- a)  $m_1 + m_2 + m_3 + m_4$     b)  $m_1 + m_2 + m_4 + m_5$   
c)  $m_1 + m_3 + m_4 + m_5$     d) none of these.

- iii) If  $(128)_{10} = (1003)_b$ , the possible base  $b$  is
- a) 3
  - b) 4
  - c) 5
  - d) 6.
- iv) The logical expression  $y = \sum m(0, 3, 6, 7, 10, 12, 15)$  is equivalent to
- a)  $y = \prod M(0, 3, 6, 7, 10, 12, 15)$
  - b)  $\prod M(1, 2, 4, 5, 8, 9, 11, 13, 14)$
  - c)  $\sum m(1, 2, 4, 5, 8, 9, 11, 13, 14)$
  - d)  $y = \sum m(0, 3, 6, 7, 10, 12, 15)$ .
- v) The Sop form of logical expression is most suitable for designing logic circuits using only
- a) XOR gates
  - b) AND gates
  - c) NAND gates
  - d) NOR gates.
- vi) Which of the following flip-flops is used as latch ?
- a) JK flip-flop
  - b) D flip-flop
  - c) RS flip-flop
  - d) T flip-flop.
- vii) The fraction  $0.68_{10}$  is equal to
- a)  $0.010101_2$
  - b)  $0.101_2$
  - c)  $0.10101_2$
  - d)  $0.10111_2$ .

viii) The resolution of a 12-bit D/A converter using a binary ladder with + 10V as the full scale output will be

- a) 2.44 mV
- b) 3.50 mV
- c) 4.32 mV
- d) 5.12 mV.


ix) The initial state of MOD 16 down counter is 0110. The state after 37 clock pulse will be

- a) 0000
- b) 0110
- c) 0101
- d) 0001.


x) In a D type latch Enable i/p is HIGH,  $D = 1$ . The o/p will be

- a) 0
- b) 1
- c) don't care
- d) blocked.

 xi) The frequency of the pulse at point A is



 - a) 10 kHz
- b) 31.25 Hz
- c) 50 Hz
- d) 5 kHz.



The value of F is

- a) A XOR B
- b) A XNOR C
- c) A XOR C
- d) B XNOR C.

xiii) Largest negative number that can be represented by 8-bit word length in 2's complement system is

- a) - 255
- b) - 128
- c) - 127
- d) - 256.

xiv) The logic family that gives fastest switching is

- a) CMOS
- b) ECL
- c) Schottky TTL
- d) DTL.

**GROUP - B**  
**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. Draw a BCD adder circuit to add two BCD numbers maximum up to 9. The output of this adder should also be in BCD.
3. Design a full subtractor circuit using multiplexer.
4. Construct a 2-bit comparator using only decoder.
5. a) Define the following terms related with digital IC :
  - i) Noise margin
  - ii) Propagation delay
  - iii) Fan-in & Fan-out.b) Write down the characteristic equation of JK & D Flip-flops.  $3 + 2$
6. What is the main difference between a latch and a flip-flop ?

**GROUP - C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Write down the differences between combinational logic circuit & sequential logic circuit.

- b) Design a MOD 14 asynchronous UP/DOWN counter with JK flip-flop.  $3 + 12$

8. a) With the help of necessary circuit diagram explain the operation Ramp type ADC.

- b) A 6-bit R-2R ladder type DAC has reference voltage of 6.5 V.

Find :

i) resolution in % & volt

ii) the full scale voltage

iii) the o/p for the i/p 011100.  $10 + 2 + 1 + 2$

9. a) Discuss the totem pole output configuration of TTL logic family.

- b) Design a combinational circuit that accepts a BCD as i/p and generates XS3 as an o/p using ROM.

- c) Design & explain the operation of a 4-bit universal register.  $5 + 5 + 5$

10. a) Write down the excitation table of JK and D flip-flops and derive the excitation equation for these two flip-flops.
- b) Design a full subtractor using full adder module and NOT gates.
- c) Design a full subtractor using 4 to 1 MUX.  $6 + 3 + 6$
11. Write short notes on any three of the following :  $3 \times 5$
- a) Priority encoder
  - b) Even parity generator and checker
  - c) PLD
  - d) Johnson counter
  - e) Parallel in serial out ( PISO ) shift register.