

DIPLOMA IN NAUTICAL SCIENCE

Term-End Examination

June, 2007

BNA-013 : ELECTRICITY AND ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note :

- (i) *Non-programmable scientific calculator is allowed.*
- (ii) *Attempt **three** questions from each section in all.*
- (iii) *Questions no. 1 and 5 are **compulsory**.*

SECTION A (Electricity)

1. (a) Explain principle, construction and working of a transformer. Briefly explain step-up and step-down transformer. 10
- (b) A step-down transformer is used on 220 V supply to provide a current of 5 amp to a 60 watts bulb. If the secondary has 24 turns, find the number of turns in the primary and the current that flows in it. 5

*Attempt any **two** from the following three questions.*

2. (a) Define the following terms: 5

- (i) Watt
- (ii) emf
- (iii) Temperature coefficient of resistance
- (iv) Average value of resistance
- (v) Form factor
- (b) If the rms current in 50 Hz sinusoidal a.c. is 10 amp, determine 5
 - (i) Peak value of alternating current
 - (ii) Average value of alternating current
 - (iii) Form factor
 - (iv) The value of current $1/150$ sec. after it was zero
- 3. (a) Explain briefly construction and working of an A.C. generator. 5
- (b) If a copper wire is stretched to make it 15% longer, what is the percentage change in its resistance ? 5
- 4. (a) State and explain Kirchhoff's Current Law. Why Kirchhoff's Current Law is called as "Law of Conservation of Charge" ? 5
- (b) What is the force on a wire of length 0.015 m carrying current 0.75 amp, placed inside a long, straight solenoid near its centre and making an angle of 30° with the axis of the solenoid ? The number of turns per unit length of the solenoid is 20 and it carries a current of 0.3 amp. 5

SECTION B (Electronics)

5. (a) Explain V – I characteristics of a junction diode. 10
- (b) A tungsten wire of unknown composition emits 0.3 amp/cm^2 at a temperature of 2100°K . Find the work function of tungsten filament.
(Given : $A = 60.2 \text{ amp/cm}^2/\text{K}^2$) 5

Attempt any **two** from the following three questions.

6. (a) Explain briefly common emitter amplifier with necessary circuit diagram. 5
- (b) A tuned collector oscillator operates at 2.2 MHz frequency. At what frequency will it work if its tuned circuit capacitance is reduced by 50% ? 5
7. (a) How can zener diode be used as voltage stabilizer ? Explain with necessary circuit diagram. 5
- (b) A full wave rectifier uses two diodes of forward resistance 20Ω each. The transformer rms secondary voltage from centre tap to each end of secondary is 30 V and load resistance is 980Ω . Find
- (i) d.c. current
 - (ii) rms current
 - (iii) efficiency of rectification 5

8. Write short notes on any **two** of the following : $5 \times 2 = 10$

- (i) Need for modulation
- (ii) Capacitor filter
- (iii) Half adder
- (iv) Loop antenna
- (v) Kirchhoff's voltage law