

C13-R3: DIGITAL SYSTEM DESIGN

NOTE:

1. Answer question 1 and any FOUR questions from 2 to 7.
2. Parts of the same question should be answered together and in the same sequence.

Time: 3 Hours

Total Marks: 100

1.

- a) What is multiplexer? Justify whether a multiplexer is sufficient to realize any Boolean function.
- b) Simplify the following Boolean expression, and also obtain the simplified expression in POSs form.
$$F = (C+D)' + A'CD' + AB'C' + A'B'CD + ACD'$$
- c) Realize a 3-input XOR gate with the help of 2-input NAND gates only.
- d) Relatively compare the advantages and disadvantages of synchronous counter and asynchronous counter.
- e) Differentiate demultiplexer from decoder.
- f) What is ripple counter? "Ripple counter is also known as divided-by- n counter." - Explain.
- g) Obtain a clocked T flip-flop using a clocked D flip-flop as basic unit.

(7x4)

2.

- a) Draw a logic circuit of a 4-bit shift register with the help of JK flip-flops and multiplexers having the facilities of (i) parallel loading, (ii) right shifting, (iii) left shifting, and (iv) no change. Clearly state how are the facilities achieved.
- b) Design a clocked JK flip-flop using only NAND gates.
- c) Define race problem. What do you mean by race-around condition? Devise a mechanism to resolve it and clearly state how it operates.

(6+6+6)

3.

- a) State Shannon's Expansion Theorem, and prove it.
- b) Define minterm and maxterm. Give an example of each. State their significance, and explain why they are so called.
- c) Suppose a decade counter is used to count down from 9 through 0. Design a combinational circuit, using only basic gates, that is to be appended after the decade counter, so that the overall circuitry behaves like a down counter.

(6+6+6)

4.

- a) Prove that NAND and NOR gates are universal logic gates.
- b) Describe the general structure of CMOS logic circuit. Obtain the transistor level circuit of CMOS 3-input OR gate.
- c) Design a CMOS circuit for the full adder, where (i) A_n , B_n , and C_n are three input variables, (ii) Output carry C_{n+1} is a function of A_n , B_n , and C_n , and (iii) Output sum S_n is a function of A_n , B_n , C_n , and C_{n+1} .

(4+6+8)

5.

- a) A synchronous counter with four JK flip-flops has the following connections.

$$J_A = K_A = 1,$$

$$J_B = Q_A \cdot Q_D', \quad K_B = Q_A,$$

$$J_C = K_C = Q_A \cdot Q_B,$$

$$J_D = Q_A \cdot Q_B \cdot Q_C, \quad \text{and } K_D = Q_A$$

Determine the modulus, n of the counter, and draw the output waveforms of the same.

- b) Realize the CMOS circuit with its structural specification as given below. The circuit consists of four transistors in series, two consecutive pMOS transistors Q_1 and Q_2 with the source of Q_1 as V_{DD} , two consecutive nMOS transistors Q_3 and Q_4 with the source of Q_4 as grounded, and the output at the common drain of Q_2 and Q_3 . In addition, the gates of Q_1 and Q_4 are common to input 1, whereas the gates of Q_2 and Q_3 are complementary to each other, with the gate of Q_2 as input 2.
- c) Draw the circuit diagram of a three-input totem-pole output TTL NAND gate. State with justification whether two or more totem-pole outputs can be wire-ANDed.

(9+5+4)

6.

- a) Design a serial two's complementer circuit using JK flip-flop as the basic memory element.
- b) What is PLD? Write a short note on PLA folding.
- c) Mention the advantages and disadvantages of Gate Array design style over Custom (or Semi-Custom) design style, in designing VLSI chips.

(7+5+6)

7.

- a) Construct a sequence generator to produce the sequence 11010110.
- b) Design a synchronous counter using JK flip-flops to count the sequence:
"1-3-15-5-8-2-0-12-6-9"
- c) Write a short note on Data flow modeling of VHDL.

(6+8+4)