

### C13-R3: DIGITAL SYSTEM DESIGN

#### NOTE:

1. Answer question 1 and any FOUR questions from 2 to 7.
2. Parts of the same question should be answered together and in the same sequence.

Time: 3 Hours

Total Marks: 100

1.

- a) The following calculation was performed by a particular breed of unusually intelligent chicken. If the radix  $r$  used by the chicken corresponds to its total number of toes, how many toes does the chicken have on each foot?  
$$((35)_r + (24)_r) \times (21)_r = (1501)_r$$
- b) Prove that the dual of the exclusive-OR is also its complement.
- c) Design a combinational circuit that multiplies by 5 an input decimal digit represented in BCD. The output is also in BCD. Show that the outputs can be obtained from the input lines without using any logic gates.
- d) Define programmable Array Logic (PALs). How are they characterized?
- e) In VHDL, there are two types of delay that can be used for modelling behaviour. Taking a suitable example, explain each of them in brief.
- f) Datapaths provide connections between components in the system and are classified according to different features. Explain each feature of the datapath in brief.
- g) Which are the programmable elements of FPGA module? Explain the functions of each of them in brief.

(7x4)

2.

- a) Implement the four Boolean functions listed using three half-adder circuits

$$D = A \oplus B \oplus C$$

$$E = \overline{A}BC + A\overline{B}C$$

$$F = A\overline{B}\overline{C} + (\overline{A} + \overline{B})C$$

$$G = ABC$$

- b) A combinational circuit is specified by the following three Boolean functions:

$$F_1 = \overline{X + Y} + XY\overline{Z}$$

$$F_2 = \overline{X + Y} + \overline{X}YZ$$

$$F_3 = XYZ + \overline{X + Y}$$

Design the circuit with a decoder and external OR gates.

- c) Design a synchronous mod-6 counter whose counting sequence is 000, 010, 011, 110, 101, 001, 000 etc. Use clocked JK flip-flops.

(4+4+10)

3.

- a) Find a logic diagram representing minimum 2-level logic needed to implement the VHDL dataflow description give below. Note that complemented inputs are available.

-- Combinational Circuit 2: Dataflow VHDL Description

- **library** ieee;

**use** ieee. std\_logic\_1164. **all**;

**entity** comb\_ckt\_2 **is**

**port** (a, b, c, d, a\_n, c\_n, d\_n: **in** std\_logic;


f, g: **out** std\_logic);

-- a\_n, b\_n, .. are complements of a, b, ..., respectively.

**end** comb\_ckt\_2;

```
architecture dataflow_1 of comb_ckt_2 is  
begin  
f <= b and (a or (a_n and c)) or (b_n and c and d_n);  
g <= b and (c or (a_n and c_n)) or (c_n and d_n);  
end dataflow_1;
```

 - b) Write a dataflow description for the circuit in Figure given below by using the Boolean equation for the output F.



(9+9)

4.

- a) Simulate the 4 x 1 MUX using Behavioral Style Modeling.

- b) For the following expressions:

$$f_1(x, y, z) = \sum m(1, 2, 4, 5, 7)$$

$$f_2(x, y, z) = \sum m(0, 1, 3, 5, 7)$$

Illustrate the use of PAL to realize combinational logic.

(9+9)

5.

- a) A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:

$$D_A = \overline{X}Y + XA \quad D_B = \overline{X}B + XA \quad Z = XB$$

- Draw the logic diagram of the circuit.
- Derive the state table
- Derive the state diagram

- b) A one-digit BCD adder using FPGA module is to be designed. Write high-level specifications of the system. Draw a scheme that uses two binary adders. Show the steps only for FPGA implementation.

(9+9)

6.

- a) ROM modules can be classified according to the way that their contents (the values of the constant bit-vectors) are set. Explain this classification and discuss the advantages and disadvantages of each of them.

- b) Consider sequential system described by the following tabular representation (the combination  $x_1x_0 = 00$  never appears, so it is considered a don't care case):

Input:  $\underline{x} = (x_1, x_0), x_i \in \{0, 1\}$

Output:  $z \in \{0, 1\}$

State:  $\underline{y} = (y_1, y_0), y_i \in \{0, 1\}$

Function: The transition and output function are

PS	$x_1x_0$		
$y_1y_0$	01	10	11
00	01,0	10,1	10,0
01	00,0	11,1	11,0
10	11,0	10,0	00,1

11      |      10,0      00,0      11,1

Show a ROM-based implementation of this system, including ROM contents.

**(8+10)**

**7.**

- a) ASM (Algorithmic State Machine) is a controller for the logic design of a digital system and is regarded as a hardware algorithm. Show the general model of an ASM and explain the working of each functional block.
- b) Consider a design example of a parallel (unsigned) 4-bit binary multiplier.
  - i) Draw a possible system architecture diagram for the binary multiplier, showing different components, which are required for the design.
  - ii) Mention the signals associated with its controller and draw an ASM chart for the same.

**(6+12)**