

**AMIETE – ET (OLD SCHEME)**

Code: AE27

Subject: DIGITAL HARDWARE DESIGN

Time: 3 Hours

Max. Marks: 100

**DECEMBER 2009****NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2x10)**

a. The outputs of a system at any time are determined from present inputs and previous stored values in \_\_\_\_\_.

- (A) Combinational system  
 (B) Sequential system  
 (C) RTL system  
 (D) None of above

b. Modeling a digital design as a set of components and interconnections is done in \_\_\_\_\_.

- (A) Data flow design                      (B) Behavioural design  
 (C) Mixed style design                      (D) Structural design

c. The Boolean algebra expression  $(x + x')y =$

- (A) x    (B) y  
 (C) x+y    (D)  $x' + y$

d. In \_\_\_\_\_ state machine, output is a function of \_\_\_\_\_ and \_\_\_\_\_.

- (A) Mealy, present-state, external inputs  
 (B) Moore, present-state, external inputs  
 (C) Mealy, next-state, external inputs  
 (D) Moore, next-state, external inputs

e. A Programmable Array Logic (PAL) has

- (A) Hardwired AND array and a programmable OR array  
 (B) Hardwired OR array and a programmable AND array  
 (C) Programmable AND array and a programmable OR array  
 (D) Hardwired AND array and a hardwired OR array

f. What is value of base r if  $(121)_r = (144)_8$  ?

- (A) 7    (B) 8

(C) 9

(D) 10


g. The circuit shown in Fig. 1 detects the following sequence

(A) 0001

(B) 0111

(C) 0101

(D) 1111

 


h. The threshold element shown in Fig.2, realises the switching function, where  $Y = f(x_1, x_2, x_3)$

(A)  $Y = \Sigma (1, 2, 3, 6, 7)$

(B)  $Y = \Sigma (2, 3, 7)$

(C)  $Y = \Sigma (1, 2, 4, 5)$

(D)  $Y = \Sigma (2, 5, 6, 7)$

 

i. A modulo-P twisted-tail ring counter uses

(A) P binary variable

(B) 2P binary variable

(C) P/2 binary variable

(D) None of the above

j. Typical uses of shifters include

(A) Removal of the leading (or trailing) bits of a vector

(B) Performing multiplication or division by a power of two.

(C) Extracting a subvector from a bit-vector

(D) All the above

**Answer any FIVE Questions out of EIGHT Questions.**

**Each question carries 16 marks.**

**Q.2** a. Use the tabulation procedure to generate the set of prime implicants and to obtain *all* minimal expressions for the following function:

$$f(w, x, y) = \Sigma (1, 5, 6, 12, 13, 14) + \Sigma \phi (2, 4) \tag{9}$$

b. Find whether the function

$$f(w, x, y, z) = \Sigma (0, 1, 3, 5, 8, 10, 11, 12, 13, 15) \text{ is symmetric and if so express the function in symmetric notation.} \tag{7}$$

**Q.3** a. Explain the following:-

- (1) FPGAs  
 (2) Shift registers  
 (3) Priority encoder (9)
- b. Using a ROM, implement a system that converts from BCD to Seven segments. (7)
- Q.4** a. Implement the following function with NAND gates:-  
 $f(x, y, z) = \sum (0, 6)$  (6)
- b. Explain features of Computer Aided Design Tools. (4)
- c. Explain how functional decomposition is done. Give an example. (6)
- Q.5** a. Explain identification and realization of threshold functions. (5)
- b. Give an example of data sub system and control sub system. (7)
- c. Explain explicit sequencing and implicit sequencing used in microinstruction sequencing. (4)
- Q.6** a. Explain critical race and non-critical race used in asynchronous sequential machines. (5)
- b. Explain limitations of finite state machines. (3)
- c. Draw the ASM chart and state diagram for the synchronous circuit, which has enable input E, clock and outputs A, B, C. (8)
- (i) If E= 1, on every rising edge of the clock code on output A, B, and C changes from 000 → 011 → 101 → 111 → 000 and repeats.  
 (ii) If E= 0, then the circuit holds present state.
- Q.7** a. Write short notes on:- (8)
- (i) Horizontal and vertical microinstruction format  
 (ii) Synchronous sequential machine and asynchronous sequential machine
- b. Draw the structure of microprogrammed controller and explain its functionality. (8)
- Q.8** a. Write VHDL code for the following:- (8)
- (i) 3×8 decoder  
 (ii) JK flip flop
- b. Draw the block diagram of Programmable Sequential Array (PSA) and explain various inputs and outputs. (4)
- c. Explain minimization of flow tables in synchronous sequential machines. (4)
- Q.9** a. Design full subtractor using structural modeling, in VHDL. (6)
- b. Mention various components used in VHDL design. (4)

c. Compare behavioural, structural and data flow models used in VHDL.

**(6)**