



- (A) present state and external inputs.
- (B) only present state.
- (C) only external inputs.
- (D) neither present state nor external inputs.

e. Which of the following is a unate function

- (A)  $x'z + x'y + w'z$
- (B)  $x'y + xy' + x'y'$
- (C)  $x'z + xz + yz'$
- (D)  $xz + yz' + xy'$


f. Fig. 2 is block diagram of a multiplier that multiplies two-bit binary numbers. How many output variables (x) are needed for it



- (A) 2
- (B) 4
- (C) 6
- (D) 8

g. The circuit shown in Fi

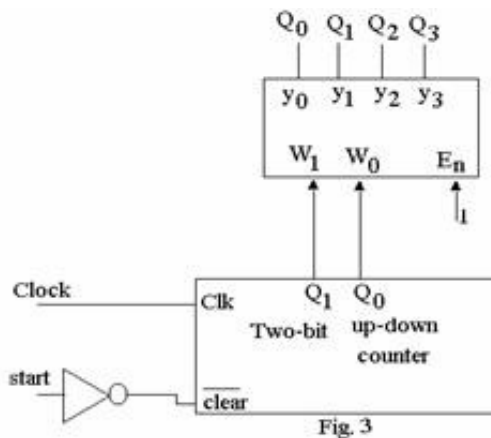- (A) 2-bit up down cc
- (B) 4-bit up down cc
- (C) 4-bit ring counter
- (D) 4-bit Johnson coi



h. Time  $t_1$  and  $t_2$  shown in Fig.4 respectively represent


- (A) set up and hold time.
- (B) hold and set up time.
- (C) rise and fall time.
- (D) fall and rise time.

i. Canonical sum of pr

- (A)  $pqs + pqs' + p$
- (C)  $pq's + pqs' + p$

j. An n-bit Johnson co

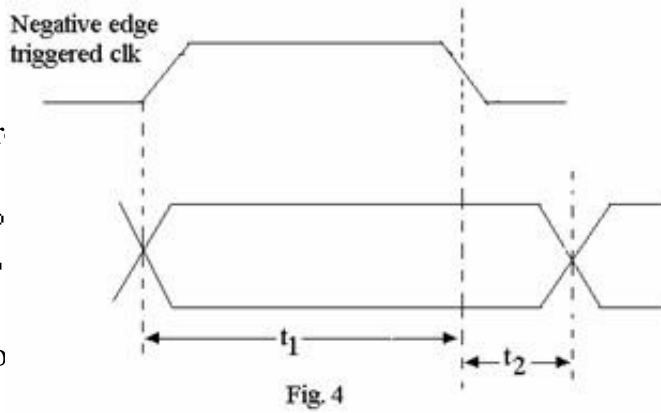- (A)  $\frac{n}{2}$ .
- (B)  $2n$ .
- (C)  $4n$ .
- (D)  $n$ .



**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

**Q.2** a. Derive a minimum-cost realisation of a four-variable function that is equal to 1 if exactly two or exactly three of its variables are equal to 1, otherwise it is equal to 0. (6)

b. A circuit with two outputs has to implement the following functions:

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 4, 6, 7, 9) + d(10, 11)$$

$$g(x_1, x_2, x_3, x_4) = \sum m(2, 4, 9, 10, 15) + d(0, 13, 14)$$

Design a minimum-cost circuit to complement the above function. Compare its cost with combined costs of two circuits that implement the functions f and g separately. Assume that inputs are available in both uncomplemented and complemented form. (10)

**Q.3** a. The function  $f(x_1, x_2, x_3, x_4, x_5) = \sum m(4, 7, 8, 11, 13, 14, 23, 27, 28, 29, 30)$  can be decomposed to the form  $F(\Phi(x_1, x_4, x_5), x_2, x_3)$ . Determine the function F and  $\Phi$ . (6)

b. Design a single digit BCD adder using an EPROM. Determine the minimum size (mxn bits) of the EPROM. (10)

**Q.4** a. Explain with the help of a suitable logic diagram the differences between a registered PAL and a GAL. (6)

b. Write a VHDL program for a  $4 \times 1$  multiplexer. (4)

c. Write a VHDL program for a 4 bit shift register. (6)

**Q.5** The output z of a fundamental, two-input sequential circuit changes from 0 to 1 only when  $x_2$

changes from 0 to 1 while  $x_1 = 1$ . Further, the output changes from 1 to 0 only when  $x_1$  changes from 1 to 0 while  $x_2 = 0$ .

- (i) Find a minimum row reduced flow table. (8)
- (ii) Show a valid assignment and write a set of hazard free excitation and output equations. (8)

**Q.6** a. Reduce the state table given below using equivalence class state reduction technique. (8)

Present State (PS)	Next State (NS), Output (Z)	
	x=0	x=1
s <sub>0</sub>	s <sub>3</sub> ,0	s <sub>1</sub> ,0
s <sub>1</sub>	s <sub>4</sub> ,0	s <sub>0</sub> ,1
s <sub>2</sub>	s <sub>6</sub> ,0	s <sub>5</sub> ,1
s <sub>3</sub>	s <sub>0</sub> ,1	s <sub>3</sub> 0
s <sub>4</sub>	s <sub>0</sub> ,1	s <sub>3</sub> 0
s <sub>5</sub>	s <sub>2</sub> ,0	s <sub>1</sub> 0
s <sub>6</sub>	s <sub>0</sub> ,1	s <sub>4</sub> 0

- b. Construct a Mealy state diagram that detects a serial input sequence of 10110. Overlapping of the patterns is possible. When the input pattern is detected, it causes output z to be asserted high. First write the flow table and then reduce it.

(8)

**Q.7** a. Find the reduced state table for the machine M given below: (8)

PS	NS, Z <sub>1</sub>			
	xy=00	xy=01	xy=10	xy=11
A	A, -	C, 1	E, 1	B, 1
B	E, 0	C, -	-, -	-, -
C	F, 0	F, 1	E, 0	-, -
D	-, -	E, 0	A, -	-, -
E	-, -	-, -	A, 0	D, 1
F	C, 0	-, -	B, 0	C, 1

**Machine M**

- b. What is maximal compatibility? What is the difference between compatible states and maximal compatibility? (8)

**Q.8** a. For the two given Machines M<sub>1</sub> and M<sub>2</sub>, find a bigger machine M which is a serial combination

of  $M_1$  and  $M_2$ . (8)

PS	NS,Z	
	x=0	x=1
A	B, 0	C, 0
B	A, 1	C, 0
C	B, 1	A, 0

Machine M1

PS	NS,Z	
	y=0	y=1
a	a, 0	b, 1
b	b, 1	a, 1

Machine M2

b. Find the state assignment, by choosing self dependent subset, for the machine given below: (8)

PS	NS		Z
	x=0	x=1	
A	E	B	1
B	E	A	0
C	D	A	0
D	C	F	1
E	F	C	0
F	E	C	0

**Q.9** a. Write ASM chart for a machine which scans a 3 bit word and produces an output  $z_2$  when last two bits in consecutive 3 bit word are ones and second output  $z_1$  which identifies the start of each 3-bit word. Implement the machine using multiplexers. (6)

b. Explain the role of CAD Tools in digital system design. (6)

c. Write a brief note on a micro-programmed controller. (4)